

Application Note

1. TDPS1000E0E10 Half-Bridge Evaluation Board

1.1 Introduction

This half-bridge evaluation board provides the elements of a simple buck or boost converter for basic study of switching characteristics and efficiency achievable with Transphorm's 600V GaN power switches. In either buck or boost mode the circuit can be configured for synchronous rectification. Jumpers allow use of a single logic input or separate hi/lo inputs. The high-voltage input and output can operate at up to 400Vdc, with a power output of up to 1kW. The inductor provided is intended for efficient operation at 100kHz, although other inductors and other frequencies may be easily used.

 


Fig. 1. Half-Bridge Evaluation Board

1.2 TDPS1000E0E10 Input/output Specifications:

- High-voltage input/output: 400 Vdc maximum
- Auxiliary Supply (J1): 10V min, 18V max
- Logic inputs: nominal 0-5V;

for the pulse-generation circuit,	$V_{lo} < 1.5V, V_{hi} > 3.0V$
for direct connection to gate driver, SMA coaxial connectors	$V_{lo} < 0.8V, V_{hi} > 2.0V$
- Switching frequency: configuration dependent
 - lower limit determined by peak inductor current
 - upper limit determined by desired dead time and power dissipation
- Power dissipation in HEMTs is limited by maximum junction temperature. Refer to the TPH3006PS data sheet.

1.3 Circuit Description

The circuit comprises a simple half bridge featuring two TPH3006PS GaN power transistors, as indicated in the block diagram of Figure 2. Two high-voltage ports are provided which can serve as either input or output, depending on the configuration: boost or buck. In either case one transistor acts as the active power switch while the other carries the freewheeling current. The latter device may be enhanced, as a synchronous rectifier, or not. With GaN power transistors the reverse recovery charge is low and there is no need for additional freewheeling diodes. Two input connectors are provided which can be connected to sources of logic-level command signals for the hi/lo gate driver. Both inputs may be driven by off-board signal sources, or alternatively, a single signal source may be connected to an on-board pulse-generator circuit which generates the two non-overlapping pulses. Jumpers determine how the input signals are used.

An inductor is provided as a starting point for investigation. This is a 320uH toroid intended to demonstrate a reasonable compromise between size and efficiency for power up to 1kW at a switching frequency of 100kHz.

 


Figure 2: Functional Block Diagram


1.4 Using the board

The board can be used for evaluation of basic switching functionality in a variety of circuit configurations. It is not a complete circuit, but rather a building block. It can be used in steady-state DC/DC converter mode with output power up to 1kW. Depending on circuit configuration and desired operating temperature, forced air flow might be required at higher power levels.


1.5 Configurations

Figure 3 shows the basic power connections for buck and boost modes. For buck mode, the HVdc input (terminals J2,J3) is connected to the high-voltage supply and the output is taken from terminals J5 and J7. For boost mode the connections are reversed.

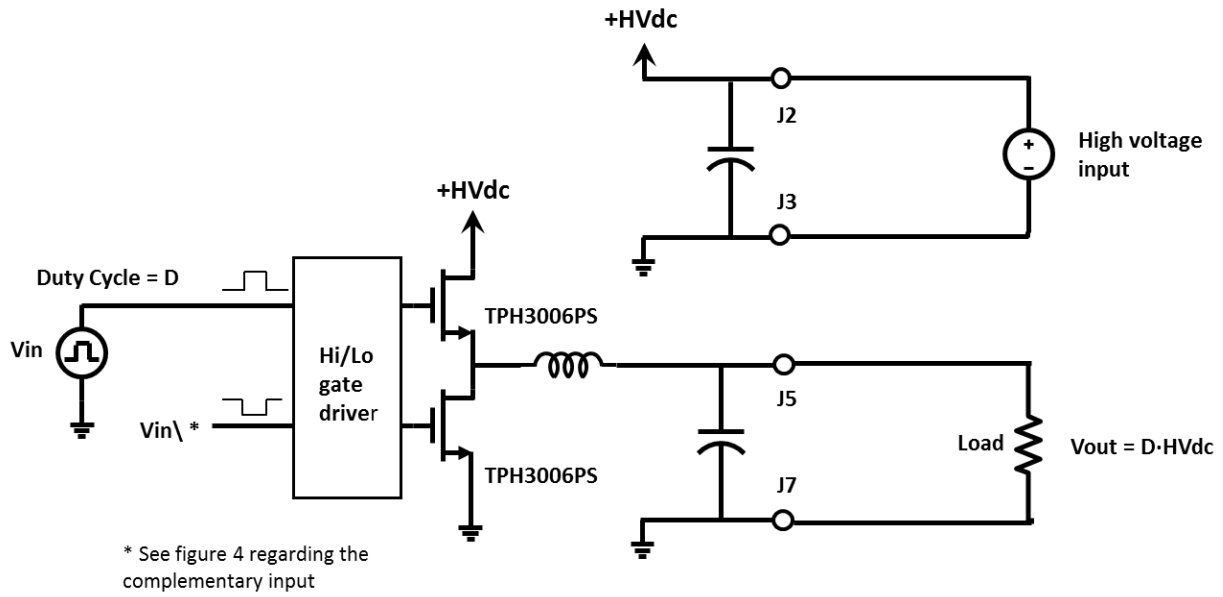Note that in boost mode a load must be connected. The load current affects the output voltage up to the transition from DCM to CCM. In buck mode the load may be an open circuit.



(a) Buck Mode

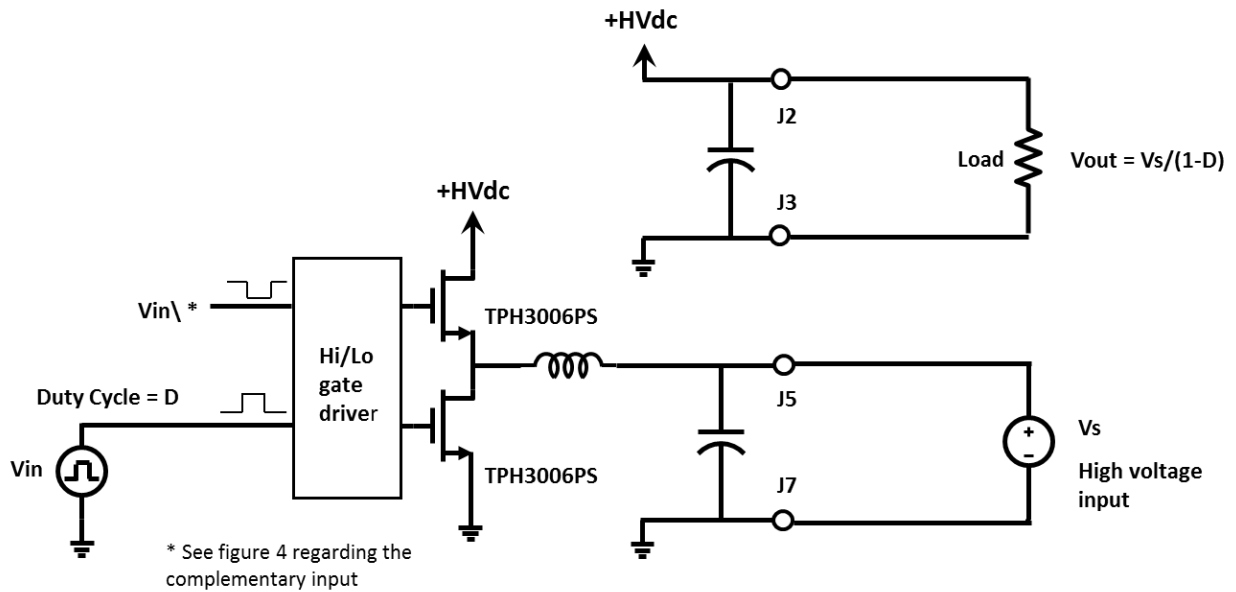


(b) Boost mode

Figure 3. Supply and Load connections for Buck (a) and Boost (b) configurations.

Figure 4 shows possible configurations for the gate-drive signals. In figure 4(a) a single input from an external signal source is used together with the on-board pulse generation circuit. J4 is used, J6 is left open circuit. Jumpers JP1 and JP2 are in the top position, as shown. If the high-side transistor is to be the active switch (e.g. buck mode), then the duty cycle of the input source should simply be set to the desired duty cycle (D). If the low-side transistor is to be the active switch (e.g. boost mode) the duty cycle of the input source should be set to (1-D), where D is the desired duty cycle of the low-side switch. This configuration results in synchronous rectification. If it is desired to let the device carrying the freewheeling current act as a diode, then the appropriate jumper should be placed so that the pull-down resistor is connected to the driver. Figure 4(b) shows a buck-mode configuration where the low-side device is not enhanced. Finally, figure 4(c) shows use of two external signal sources as inputs to the gate driver.

For any configuration an auxiliary supply voltage of 10V-18V must be supplied at connector J1.

Pull-down resistors R5 and R6 have a value of 4.99k. If a 50 ohm signal source is used and 50 ohm termination is desired, then R5 and R6 may be replaced (or paralleled) with 1206 size 50 ohm resistors.

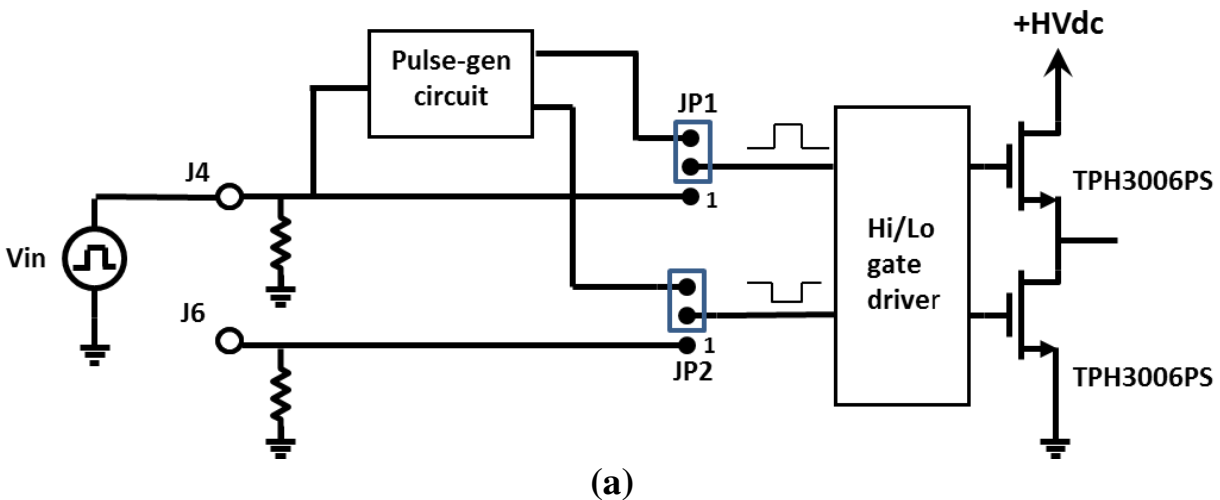

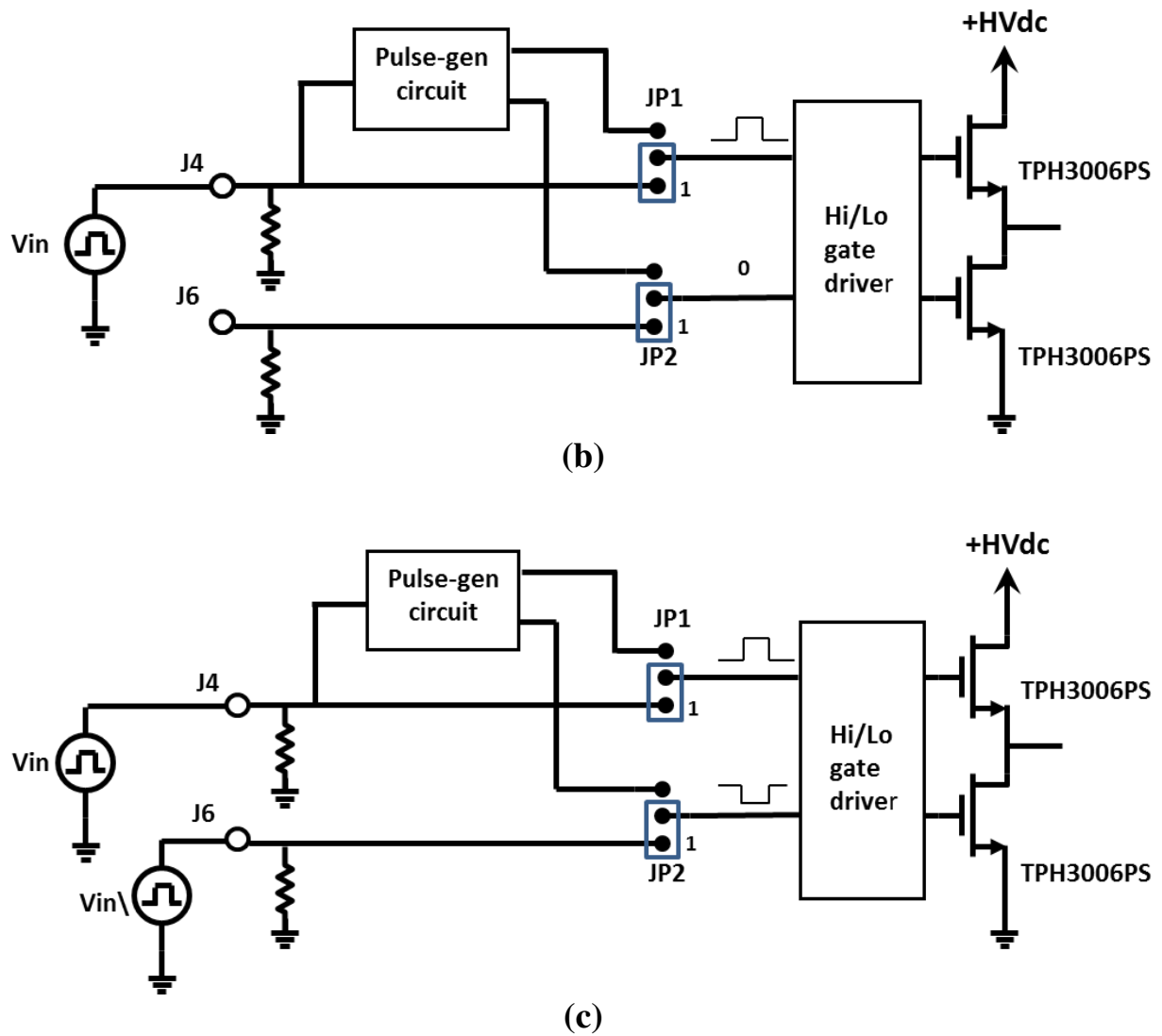


Figure 4: input configurations. (a) using a single source for either buck or boost mode (b) buck mode without synchronous rectification (c) using two signal sources

1.6 Deadtime control

The required form of the gate-drive signals is shown in Figure 5. The times marked A are the deadtimes when neither transistor is driven on. The deadtime must be greater than zero to avoid shoot-through currents. The Si8230BB gate drive chip ensures a minimum deadtime based on the value of resistor R7, connected to the DT input. The deadtime in ns is equal to the resistance

in kohm x 10: so the default value of 5.7k corresponds to 57ns. This will add to any deadtime already present in the input signals. The on-board pulse generator circuit, for example, creates deadtimes of about the 60ns. The resulting deadtime at the gate pins of Q1 and Q2 is about 120ns. Either shorting or removing R7 will reduce the deadtime to 60ns.

 


Figure 5: Non-overlapping gate pulses


1.7 Design details

The detailed circuit schematic is included with this file as a pdf. The parts list follows in table 1.


Qty	Value	Package	ID	Manf	Manf P/N
1		529802B02 500G	HS1	Aavid Thermalloy	529802B02500G
1		74LVC1G17 DBV	U3	Texas Instruments	SN74LVC1G17DBVR
1		DIODE-DO- 214AC	D1	Fairchild	ES1J
2	2.2uF 450V	ECW- FD2W225J	C18	Panasonic	ECW-FD2W225J
2	120ohm	FB0603	FB1, FB2	TDK	MMZ1608Q121B
1			J1	Molex	22-23-2021
2		JP2E	JP1, JP2	FCI	68001-403HLF
4		KEYSTONE_ 7691	J2, J3, J5, J7	Keystone	7691
1		LT3082	U1	Linear Technology	LT3082EST#PBF
1	320uH	TVH49164A	L1	CWS	Mag-Inc 77083 core; 63 turns AWG18
1	.1u	C-EUC1812	C7	Kemet	C1812V104KDRACTU
7	.1u	C-USC0603	C10, C11, C12, C14, C20, C21, C22	AVX	06033C104JAT2A
3	.1u	C-USC2225K	C8, C16, C17	Vishay	VJ2225Y104KXGAT

1	5.76k	R-US_R0603	R7	Yageo	RC0603FR-075K76L
1	0	R-US_R1206	R9	Panasonic	ERJ-8GEY0R00V
1	10	R-US_R0805	R4	Panasonic	ERJ-6GEYJ100V
2	100pF	C-USC0603	C19, C23	AVX	06035A101FAT2A
1	10MEG	R-US_R1206	R3	Stackpole	HVCB1206FKC10M0
2	10u	C-EUC0805	C13, C15	Kemet	C0805C106M4PACTU
2	1k	R-US_R0603	R8, R10	Yageo	RC0603FR-071KL
1	1u	C-EUC0805	C2	Yageo	CC0805ZRY5V8BB105
1	2.2u	C-EUC0805	C3	TDK	C2012X5R1E225K125AC
1	0.68uF 630V	B32922C36 84M	C9	EPCOS	B32922C3684M
1	22u	C-USC1206	C1	TDK	C3225X7R1C226K250AC
3	4.7n	C-EUC1206	C4, C5, C6	Kemet	C1206C472KDRACTU
3	4.99k	R-US_R1206	R1, R5, R6	Stackpole	RMCF1206FT4K99
1	499k	R-US_R1206	R2	Stackpole	RMCF1206FT499K
2	74AHC1G86DBV	74AHC1G86 DBV	U4, U5	Texas Instruments	SN74AHC1G86DBVR
2	BAT54W	BAT54W	D2, D3	NXP	BAT54W
2	BU-SMA-G	BU-SMA-G	J4, J6	Molex	731000114
1	SI8230	SI8230	U2	Silicon Labs	SI8230BB-B-IS1
2	TPH3006PS	TPH_TO220 VERT_TRI	Q1, Q2	Transphorm	TPH3006PS
2	TPSPAD1-13	TPSPAD1-13	TP1, TP3		(TP2, TP4, TP5 DNI)
1	Q1 insulator (high side)			Bergquist	SP2000-0.015-00-54
1	Q2 insulator (low side)			Aavid Thermalloy	53-77-9G


Table 1. Bill of Materials for the half-bridge Evaluation Board

 

(a) PCB: Top and Bottom Layers

 

(b) PCB: Inner Layer 2, Ground Plane

 

(c) PCB: Inner Layer 3: Power Plane

Figure 7: PCB layers

1.7 Probing

Plated-through holes labeled test points 4 and 5 (TP4, TP5) are provided for probing the switching waveform. In order to minimize inductance during measurement, the tip and the ground of the probe should be directly attached to the sensing points to minimize the sensing loop. For safe, reliable and accurate measurement, a scope probe tip may be directly soldered to TP4 and a short ground wire soldered to TP5. Figure 8 indicates an alternative which does not require soldering the probe tip.

WARNINGS:

There is no specific protection against over-current or over-voltage on this board.

If the on-board pulse generation circuit is used in boost mode, a zero input corresponds to 100% duty cycle for the active low-side switch.

 


Fig. 8. Low-inductance probing of fast, high-voltage signals

Efficiency has been measured for this circuit in boost mode with 200Vdc in and 400Vdc out, switching at 100kHz.

 


Figure 9: efficiency for a boost 200V:400V converter