

REF_5BR4780BZ_15W1

About this document

Scope and purpose

This document is a reference design for a 15 W non-isolated auxiliary power supply for an outdoor air-conditioner unit with the latest Infineon fifth-generation fixed-frequency (FF) CoolSET™ ICE5BR4780BZ. The power supply is designed with a universal input compatible with most geographic regions and three non-isolated outputs (12 V/800 m A, 15 V/150 mA and 5 v/300 mA), where 15 V output and 5 V output are supported by a linear regulator from an 18 V source and an 8 V source respectively.

Highlights of the auxiliary power supply for the invertized air-conditioner unit are:

- Tightly regulated output voltages, high efficiency under light load and low standby power
- Comprehensive CoolSET™ protection feature for a robust system
- Auto-restart protection scheme to minimize interruption and enhance end-user experience

Intended audience

This document is intended for power supply design engineers who are designing auxiliary power supplies for invertized air-conditioner units that are efficient, reliable and easy to design.

Table of contents

Abou	t this document	1
Table	e of contents	1
1	System introduction	3
2	Reference board design	5
3	Power supply specifications	
4	Circuit diagram	
5	Circuit description	
5.1	EMI filtering and line rectification	
5.2	Flyback converter power stage	
5.3	Control of flyback converter through fifth-generation FF CoolSET™ ICE5BR4780BZ	8
5.3.1	Current sensing	8
5.3.2	Feedback and compensation network	8
5.4	Unique features of the fifth-generation FF CoolSET™ ICE5BR4780BZ	9
5.4.1	Fast self-start-up and sustaining of V _{cc}	9
5.4.2	CCM, DCM operation with frequency reduction	9
5.4.3	Frequency jittering with modulated gate drive	9
5.4.4	System robustness and reliability through protection features	10
5.5	Clamper circuit	10
5.6	PCB design tips	10
5.7	EMI reduction tips	11



Table of contents

6	PCB layout	12
6.1	Top side	12
6.2	Bottom side	12
7	Bill of materials	13
8	Transformer specification	14
9	Measurement data and graphs	15
9.1	Efficiency curve	
9.2	Standby power	18
9.3	Line and load regulation	18
9.4	Maximum input power	19
9.5	Surge immunity (EN 61000-4-5)	19
9.6	Conducted emissions (EN 55022 class B)	20
9.7	Thermal measurement	21
9.8	18 V rail regulation (LDO input)	22
10	Waveforms and oscilloscope plots	23
10.1	Start-up at full load	23
10.2	Soft-start at full load	23
10.3	Drain and CS voltage at full load	24
10.4	Frequency jittering and modulated gate drive	24
10.5	Load-transient response	
10.6	Output ripple voltage at full load	
10.7	Output ripple voltage at ABM (minimum load)	
10.8	Entering ABM	
10.9	During ABM	
10.10	8	
10.11	55 - 1 - P	
10.12	2 Overload protection	28
11	Appendix A: Transformer design and spreadsheet [3]	29
12	Appendix B: WE transformer specification	36
13	References	37
Revis	sion history	38



System introduction

1 System introduction

With the growing household trend for internet-connected devices, the new generation of home appliances including air-conditioners are equipped with advanced features such as wireless control and monitoring capability, smart sensors and touch screen display. These can transform a static product into an interactive and intelligent home appliance, capable of adapting to the smart-home theme. Infineon has introduced the latest fifth-generation CoolSET™ to address this need in an efficient and cost-effective manner.

An auxiliary SMPS is needed to power the various modules and sensors, which typically operate from a stable DC voltage source. The Infineon CoolSET™ (as shown in **Figure 1**) forms the heart of the system, providing the necessary protection and AC-DC conversion from the mains to multiple regulated DC voltages to power the various blocks.

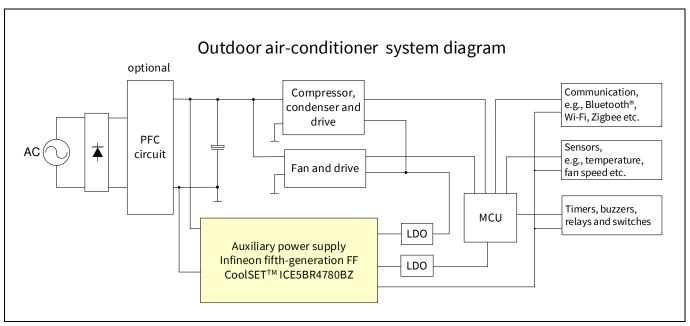


Figure 1 Simplified outdoor air-conditioner unit system block diagram

Table 1 lists the system requirements for an auxiliary power supply for an outdoor air-conditioner unit, and the corresponding Infineon solution is shown in the right-hand column.

Table 1 System requirements and Infineon solutions

	System requirement for invertized air-conditioner unit power supply	Infineon solution – ICE5BR4780BZ
1	High efficiency under light load and low standby power	Digital frequency reduction and active burst mode (ABM)
2	Robust system and protection features	Comprehensive CoolSET™ protection feature in DIP-7 package
3	Auto-restart protection scheme to minimize interruption and enhance end-user experience	All protections are in auto-restart

1.1 High efficiency under light load and low standby power

During typical air-conditioner operation, the power requirement fluctuates according to various use cases. However, in most cases where room temperature is already stabilized, both indoor and outdoor air-conditioner units will reside in an idle state, in which the loading toward the auxiliary power supply is low. It is crucial that



System introduction

the auxiliary power supply operates as efficiently as possible, because it will be in this particular state for most of the period. Under light-load conditions, losses incurred with the power switch are usually dominated by the switching operation. The choice of switching scheme and frequency play a crucial role in ensuring high conversion efficiency.

In this reference design, ICE5BR4780BZ was primarily chosen due to its frequency reduction switching scheme. Compared with a traditional FF flyback, the CoolSET™ reduces its switching frequency from medium to light load, thereby minimizing switching losses. Therefore, an efficiency of more than 80 percent is achievable under 25 percent loading conditions and nominal input voltages.

Simplified circuitry with good integration of power and protection 1.2 features

To relieve the designer of the complexity of PCB layout and circuit design, the CoolSET™ is a highly integrated device with both a controller and a HV MOSFET integrated into a single, space-saving DIP-7 package. This certainly helps the designer to reduce component count.

Auto-restart protection scheme to minimize interruption and enhance 1.3 end-user experience


For an invertized air-conditioner unit, it would be annoying to both the end user and the manufacturer if the system were to halt and latch after protection. Accessibility of the input AC plug may also be difficult; therefore, to minimize interruption, the CoolSET™ implements auto-restart mode for all protections.



Reference board design

2 Reference board design

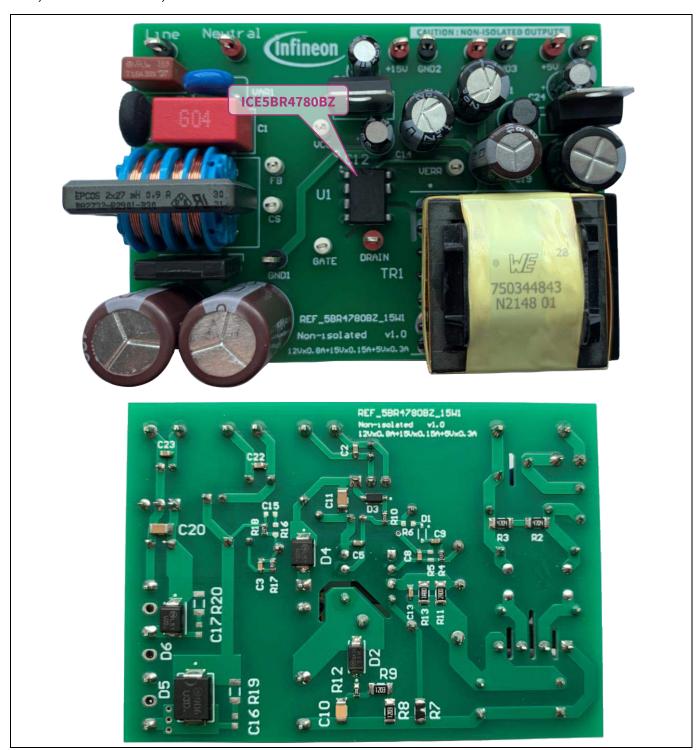This document provides complete design details including specifications, schematics, bill of materials (BOM), PCB layout and transformer design. Performance results pertaining to line/load regulation, efficiency, transient load, thermal conditions, conducted EMI scans and so on are also included.



REF_5BR4780BZ_15W1 Figure 2



Power supply specifications

Power supply specifications 3

The table below shows the minimum acceptance performance of the design at 25°C ambient temperature. Actual performance is listed in the measurements section.

Specifications of REF_5BR4780BZ_15W1 Table 2

Description	Symbol	Min.	Тур.	Max.	Units	Comments
Input						
Voltage	V _{IN}	85	_	264	V AC	2 wires (no P.E.)
Frequency	f _{LINE}	47	50/60	64	Hz	
Output						
Output voltage 1	V _{O1}	-	12	-	V	±1 percent
Output current 1	I _{O1}	-	_	0.8	Α	
Output voltage ripple 1	V_{RPP1}	-	_	60	mV	
Output voltage 2	V _{O2}	-	15	-	V	±1 percent
Output current 2	I _{O2}	-	-	0.15	Α	
Output voltage ripple 2	V_{RPP2}	-		50	mV	
Output voltage 3	V _{O3}	-	5	-	V	±1 percent
Output current 3	I ₀₃	-	-	0.3	Α	
Output voltage ripple 3	V_{RPP3}	-		50	mV	
Output power	P _{out}	-	13.35	-	W	
Output overcurrent protection	I _{OCP}	-		1.2	Α	12 V output
Start-up time	t_{start_up}	-	-	250	ms	
Environmental						
Conducted EMI			8		dB	Margin, CISPR 22 class B
Surge immunity						EN 61000-4-5
Differential mode			±1		kV	
PCBA dimension		80) x 57 x 26		mm³	LxWxH



Circuit diagram

4 Circuit diagram

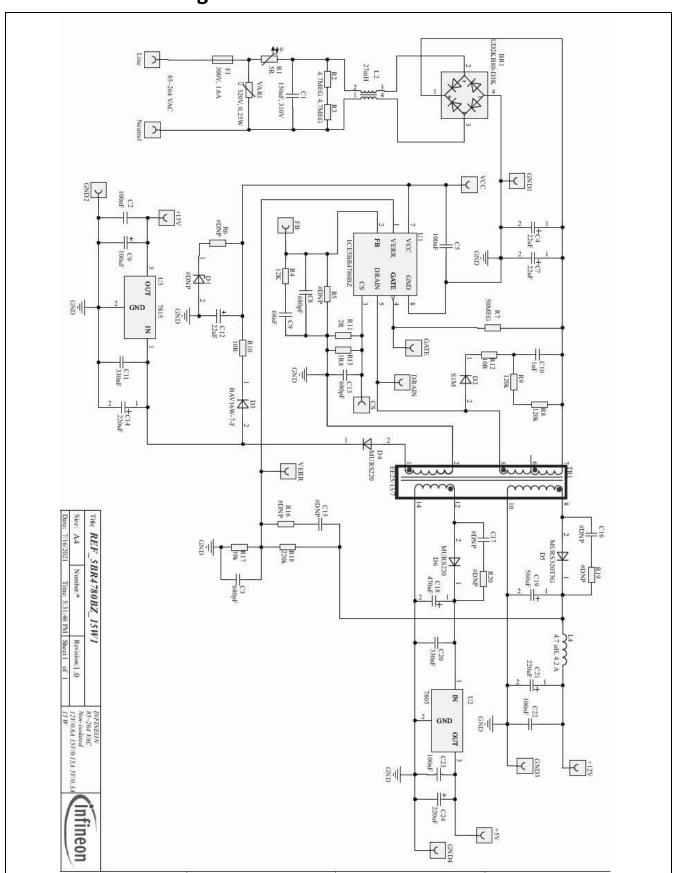


Figure 3 Schematic of REF_5BR4780BZ_15W1



Circuit description

5 Circuit description

In this section, the design circuit for the SMPS unit will be briefly described by the different functional blocks. For details of the design procedure and component selection for the flyback circuitry please refer to the IC design guide [2] and calculation tool [3].

5.1 EMI filtering and line rectification

The input of the power supply unit is taken from the AC power grid, which is in the range of 85 V AC ~ 264 V AC. The fuse F1 is directly connected to the input line to protect the system in case of excess current entering the system circuit due to any fault. Following is the varistor VAR1, which is connected across the input to absorb excessive energy during line-surge transient. The X-capacitor C1 and common-mode choke (CMC) L2 reduce the EMI noise. R2 and R3 serve as the X-capacitor discharge resistor. Thermistor R1 is in series with line to limit inrush current. The bridge rectifier BR1 rectifies the AC input into DC voltage, filtered by the bulk capacitor C4 and C7.

5.2 Flyback converter power stage

The flyback converter power stage consists of transformer TR1, CoolSET™, secondary rectification diodes D5 and D6, secondary output capacitors C18 and C19 and output filter inductor L4.

When the primary HV MOSFET turns on, energy is stored in the transformer. When it turns off, the stored energy is discharged to the output capacitors and into the output load.

Secondary winding is sandwiched between two layers of primary winding to reduce leakage inductance. This improves efficiency and reduces voltage spikes.

For the output rectification, lower forward voltage and ultra-fast recovery diodes can improve efficiency. Capacitor C19 stores the energy needed during output load jumps. LC filter L4/C21 reduces the high-frequency ripple voltage.

The 15 V output is from the 15 V low dropout (LDO) regulator (U3) with an input of 18 V. The 5 V output is from the 5 V LDO regulator (U2) with an input of 8 V. As such, these outputs would not be affected by cross-regulation. However, its input should be maintained within the operating range of the LDO.

5.3 Control of flyback converter through fifth-generation FF CoolSET™ ICE5BR4780BZ

5.3.1 Current sensing

The ICE5BR4780BZ is a current mode controller. The primary peak current is controlled cycle-by-cycle through the current sense (CS) resistors R11 and R13 in the CS pin (pin 3). Transformer saturation can be avoided through peak current limitation (PCL); therefore, the system is more protected and reliable.

5.3.2 Feedback and compensation network

Resistor R17 and R18 comprises a voltage divider, which is used to sense the V_{OUT} and directly feed back output signal to the error amplifier pin (pin 1) of U1, as it is a non-isolated design. A Type II compensation network C8, C9 and R4 is connected between the FB pin (pin 2) and GND pin (pin 8) of the U1 to stabilize the system.

The FB pin of ICE5BR4780BZ is a multifunction pin, which is used to select the entry burst power level (there are three levels available) through the resistor at the FB pin (R5) and also the burst-on/burst-off sense input during ABM.



Circuit description

5.4 Unique features of the fifth-generation FF CoolSET™ ICE5BR4780BZ

5.4.1 Fast self-start-up and sustaining of V_{cc}

The IC uses a cascode structure to fast-charge the V_{CC} capacitor. Pull-up resistors R7 connected to the GATE pin (pin 4) are used to initiate the start-up phase. At first, $I_{VCC_Charge1}$ is used to charge the V_{CC} capacitor from 0 V to V_{CC_SCP} . This is a protection which reduces the power dissipation of the power MOSFET during V_{CC} short-to-GND condition. Thereafter, a much higher charging current of $I_{VCC_Charge2}$ will charge the V_{CC} capacitor until the V_{CC_ON} is reached.

After start-up, the IC V_{CC} supply is usually sustained by the auxiliary winding of the transformer, which needs to support the V_{CC} to be above undervoltage lockout (UVLO) voltage (10 V typ.). In this reference board, the V_{CC} supply is tapped from the 18 V winding.

5.4.2 CCM, DCM operation with frequency reduction

ICE5BR4780BZ can be operated in either discontinuous conduction mode (DCM) or continuous conduction mode (CCM) with frequency-reduction features. This reference board is designed to operate in DCM at operating input voltage and load conditions. When the system is operating at high output load, the controller will switch at 65 kHz FF. In order to achieve a better efficiency between light load and medium load, frequency reduction is implemented as a function of V_{FB} , as shown in **Figure 4**. Switching frequency will not reduce further once the minimum switching frequency of 28 kHz is reached.

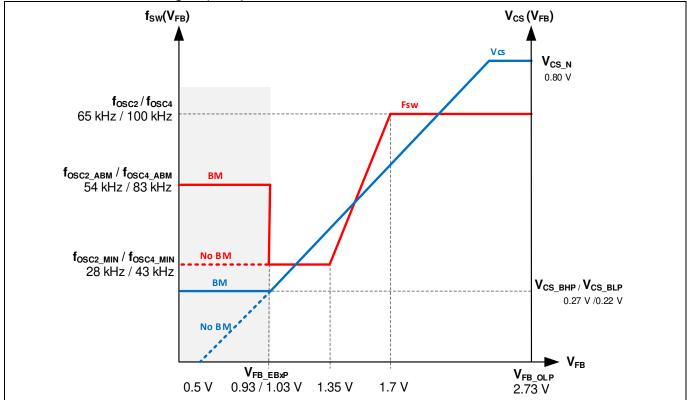


Figure 4 Frequency-reduction curve

5.4.3 Frequency jittering with modulated gate drive

The ICE5BR4780BZ has a frequency jittering feature with modulated gate drive to reduce the EMI noise. The jitter frequency is internally set at 65 kHz (±4 kHz), and the jitter period is 4 ms.



Circuit description

5.4.4 System robustness and reliability through protection features

Protection is one of the major factors in determining whether the system is safe and robust – therefore sufficient protection is necessary. ICE5BR4780BZ provides comprehensive protection to ensure the system is operating safely. This includes V_{CC} overvoltage (OV) and undervoltage (UV), overload, overtemperature and V_{CC} short-to-GND. When those faults are found, the system will enter into protection mode. Once the fault is removed, the system resumes normal operation. Protections and failure conditions are shown in the table below.

Table 3 Protection functions of ICE5BR4780BZ

Protection function	Failure condition	Protection mode
V _{cc} OV	V_{VCC} greater than V_{VCC_OVP}	Odd-skip auto-restart
V _{cc} UV	V_{VCC} less than V_{VCCoff}	Auto-restart
Overload	V_{FB} greater than V_{FB_OLP} and lasts for	Odd-skip auto-restart
	$t_{ extsf{FB_OLP_B}}$	
Overtemperature	T _J greater than 140°C (40°C hysteresis)	Non-switch auto-restart
V _{cc} short-to-GND	V_{VCC} less than V_{CC_SCP} , $I_{VCC_Charge1} \approx -0.2$ mA	Cannot start up
$(V_{VCC} = 0 \text{ V}, R_{startup} = 50 \text{ M}\Omega, V_{DRAIN} = 90 \text{ V})$		

5.5 Clamper circuit

A clamper network consisting of D2, C10 and R8, R9, R12 is used to reduce the switching voltage spikes across the drain of the integrated HV MOSFET of the CoolSET™, which are generated by the leakage inductance of the transformer TR1. This is a dissipative circuit; therefore, R8, R9 and C10 need to be fine-tuned depending on the voltage derating factor and efficiency requirement.

5.6 PCB design tips

For a good PCB design layout, there are several points to note.

The switching power loop needs to be as small as possible (see Figure 5). There are four power loops in the reference design; one on the HV side and three on the output side. The HV loop starts from the bulk capacitor C7 positive terminal, primary transformer winding, CoolSET™, CS resistors and back to the C7 negative terminal. The first output side loop (12 V output) starts at the transformer winding pin 8, output diode D5, output capacitor C19 and back to pin 10 of TR1. The second output loop (8 V output) starts at the transformer winding (pin 12 of TR1), output diode D6, output capacitor C18 and back to pin 14 of T1. The third output loop (18 V output) starts at the transformer winding (pin 2 of TR1), output diode D4, output capacitor C14 and back to pin 1 of T1.



Circuit description

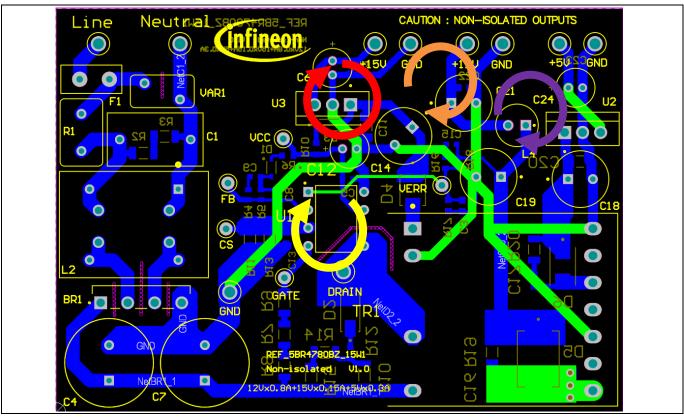


Figure 5 PCB layout tips

- Star-ground connection should be used to reduce high-frequency (HF) noise coupling that can affect the functional operation. The ground of the small-signal components should connect directly to the IC ground.
- Separating the HV components and LV components, e.g., by using a clamper circuit, can reduce the sparkover chance of the high energy surge during a lightning surge test.
- Make the PCB copper pour on the DRAIN pin of the MOSFET act as a heatsink.

5.7 EMI reduction tips

EMI compliance is always a challenge for the power supply designer. There are several critical points to consider in order to achieve a satisfactory EMI performance.


- A proper transformer design can significantly reduce EMI. Low leakage inductance can incur a low switching spike and HF noise. Interlaced winding technique is the most common practice to reduce leakage inductance. Winding shield, core shield and whole transformer shield are also some of the techniques used to reduce EMI.
- Input CMC and X-capacitor greatly reduce EMI, but this is costly and impractical especially for low-power applications.
- Short-switching power-loop design in the PCB (as described in section 5.6) can reduce radiated EMI due to the antenna effect.
- An output diode snubber circuit can reduce HF noise.
- Ferrite beads can reduce HF noise, especially on critical nodes such as the DRAIN pin, clamper diode and output diode terminals. There is no ferrite bead used in this design, as this can reduce the efficiency due to additional losses, especially on high-current terminals.



PCB layout

PCB layout 6

6.1 Top side

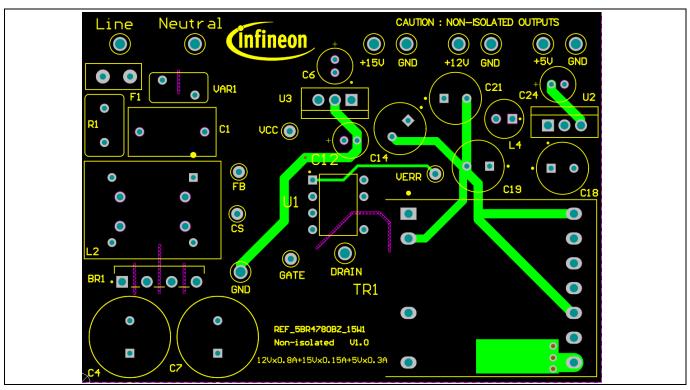

Top-side component legend Figure 6

6.2 **Bottom side**

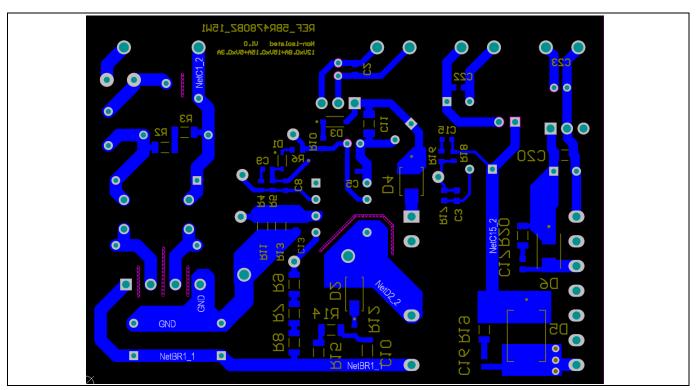


Figure 7 **Bottom-side copper and component legend**



Bill of materials

Bill of materials 7

Table 4 **BOM**

No.	Designator	Description	Part number	Manufacturer	Quantity
1	BR1	Bridge rectifiers 2 A 800 V	UD2KB80-7000	Shindengen	1
2	C1	Film capacitors 150 nF 310 V AC	890324023025	Würth Elektronik	1
3	C2, C5, C22, C23	MLCC – SMD/SMT 50 V 0.1 μF X7R 0603 10%			4
4	C4, C7	Aluminum capacitor 22 μF 20% 400 V radial	EKXG401ELL220MK20S	United Chemi-Con	2
5	C6, C24	Aluminum capacitor 100 μF 20% 25 V radial	25PX100MEFC5X11	Rubycon	2
6	C8	MLCC - SMD/SMT 0603 50 V 2200 pF 10%			1
7	C10	MLCC – SMD/SMT 500 V 1000 pF X7R 1206 10%			1
8	C9	MLCC - SMD/SMT 0603 50 V 68 nF 10%			1
9	C3, C13	MLCC - SMD/SMT 0603 50 V 680 pF 10%			2
10	C11, C20	MLCC - SMD/SMT 1206 50 V 330 nF 10%			2
11	C12	Aluminum capacitor 22 μF 20% 35 V radial	UVR1V220MDD	Nichicon	1
12	C14, C21	Aluminum capacitor 220 μF 20% 35 V radial	35ZLH220MEFCT78X11.5	Rubycon	2
13	C18	Aluminum capacitor 470 μF 20% 16 V radial	UHE1C471MPD	Nichicon	1
14	C19	Aluminum capacitor 560 μF 20% 25 V radial	25ZLJ560M8X20	Rubycon	1
15	D2	General-purpose diode 1 kV 1 A SMA	S1M		1
16	D3	General-purpose diode 100 V 150 mA SOD- 123	BAV16W-7-F	Diodes Inc	1
17	D4, D6	General-purpose diode 200 V 2 A SMB	MURS220T3G	ON Semiconductor	2
18	D5	General-purpose diode 200 V 3 A SMC	MURS320T3G	ON Semiconductor	1
19	F1	Time-lag fuse, 300 V, 1.6 A	36911600000	Littelfuse	1
20	L2	CMC 27 mH 900 mA 2LN TH	B82732R2901B030	TDK	1
21	L4	Inductor WE-TI, size 5075, 4.7 μH, 4.2 A	7447462047	Würth Elektronik	1
22	R1	ICL 5 Ω 20% 4.2 A 9.5 mm	B57235S0509M000	TDK Corporation	1
23	R2, R3	SMD resistor 4.7 mΩ 1% 1/4 W 1206			2
24	R4	SMD resistor 12 kΩ 1% 1/10 W 0603			1
25	R7	SMD resistor 50 m Ω 1% 300 mW 1206	CRHA1206AF50M0FKEF	Vishay	1
26	R8, R9	SMD resistor 120 k Ω 1% 1/4 W 1206			2
27	R10, R12	SMD resistor 10 Ω 1% 1/10 W 0603			2
28	R11	SMD resistor 2.0 Ω 1% 1/4 W 1206			1
29	R13	SMD resistor 2.2 Ω 1% 1/4 W 1206			1
30	R17	Resistor 39 kΩ 1% 1/10 W 0603			1
31	R18	Resistor 220 kΩ 1% 1/10 W 0603			1
32	TR1	EE25/13/7	750344843	Würth Elektronik	1
33	U1	FF 800 V CoolSET™	ICE5BR4780BZ	Infineon	1
34	U2	IC linear regulator 5 V 1.5 A TO220AB	L7805ABV	STMicroelectronics	1
35	U3	IC linear regulator 15 V 1.5 A TO220AB	L7815ABV	STMicroelectronics	1
36	VAR1	S07K320E2/320VAC/10%	B72207S2321K101	Epcos	1
37	+5 V, +12 V, +15 V, DRAIN, neutral	Test point THT, red	5010	Keystone	5
38	GND1, GND2, GND3, GND4, line	Test point THT, black	5011	Keystone	5
39	CS, FB, GATE, VERR, V _{CC}	Test point THT, white	5002	Keystone	5



Transformer specification

Transformer specification 8

Refer to Appendix A for transformer design and Appendix B for WE transformer specification.

Core name and material: EE25/13/7, TP4A (TDG)

Würth Elektronik bobbin: 070-6725 (14-pin, THT, horizontal version)

Primary inductance: $L_P = 926 \mu H (\pm 10 percent)$, measured between pin 5 and pin 7

Manufacturer and part number: Würth Elektronik Midcom (750344843) Rev.01

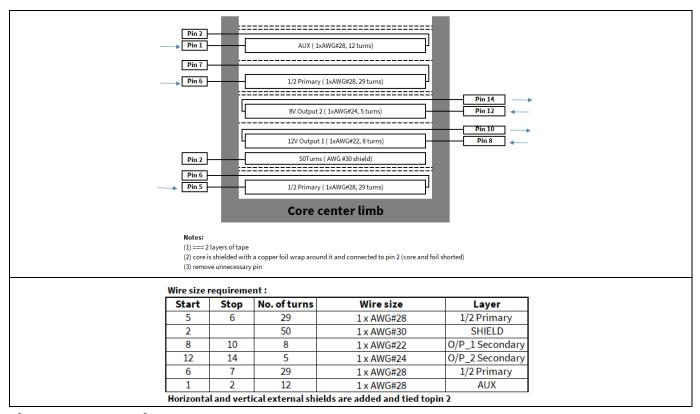


Figure 8 **Transformer structure**



Measurement data and graphs

9 Measurement data and graphs

Table 5 Electrical measurements

- 45(0 5												
Input (V AC/Hz)	P _{IN} (W)	V ₀₁ (V)	I ₀₁ (A)	V ₀₂ (V)	I ₀₂ (A)	V ₀₃ (V)	I ₀₃ (A)	P _{out} (W)	Efficiency (%)	Average efficiency (%)	OLP P _{IN} (W)	OLP Io1 (A)
	0.817	11.968	0.035	15.127	0.004	5.069	0.007	0.515				
	4.366	11.984	0.194	15.117	0.038	5.067	0.075	3.279	75.11			
85 V AC/ 60 Hz	8.728	11.984	0.395	15.105	0.079	5.066	0.150	6.687	76.61	75.50	22.69	1.12
00112	13.060	11.984	0.596	15.100	0.108	5.065	0.223	9.903	75.83	75.58		
	17.743	11.984	0.794	15.087	0.149	5.064	0.298	13.269	74.79			
	0.810	11.968	0.035	15.135	0.004	5.069	0.007	0.515				
	4.345	11.984	0.194	15.117	0.038	5.067	0.075	3.279	75.47		22.22	1.11
115 V AC/ 60 Hz	8.665	11.984	0.395	15.105	0.079	5.066	0.150	6.687	77.17			
00112	12.770	11.984	0.596	15.100	0.108	5.065	0.223	9.903	77.55	76.84		
	17.193	11.984	0.794	15.087	0.149	5.064	0.298	13.269	77.18			
	0.851	11.968	0.035	15.140	0.004	5.069	0.007	0.515				
	4.417	11.984	0.194	15.132	0.038	5.068	0.075	3.280	74.26			
230 V AC/ 50 Hz	8.703	11.984	0.395	15.127	0.079	5.067	0.150	6.689	76.86	76.64	21.71	1.11
001.12	12.749	11.984	0.596	15.097	0.108	5.065	0.223	9.902	77.67	76.64		
	17.060	11.984	0.794	15.090	0.149	5.064	0.298	13.270	77.78			
	0.871	11.968	0.035	15.135	0.004	5.069	0.007	0.515				
	4.496	11.984	0.194	15.130	0.038	5.068	0.075	3.280	72.95			
264 V AC/ 50 Hz	8.763	11.984	0.395	15.130	0.079	5.067	0.150	6.689	76.33	75.91	21.76	1.12
30	12.880	11.984	0.596	15.095	0.108	5.065	0.223	9.902	76.88			
	17.130	11.984	0.794	15.090	0.149	5.064	0.298	13.270	77.47			

Minimum load condition: 12 V/40 mA, 5 V/5 mA, 15 V/5 mA

25 percent load condition: 12 V/0.2 A, 5 V/75 mA, 15 V/38 mA $\,$

50 percent load condition: 12 V/0.4 A, 5 V/150 mA, 15 V/75 mA

75 percent load condition: 12 V/0.6 A, 5 V/225 mA, 15 V/113 mA

100 percent load condition: 12 V/0.8 A, 5 V/300 mA, 15 V/150 mA



Measurement data and graphs

Table 6 Efficiency and standby performance with a single output config

Input (V AC/Hz)	P _{IN} (W)	V ₀₁ (V)	I ₀₁ (A)	Р _{оит} (W)	Efficiency (%)	Average efficien (%)
	0.011	11.984	0.000	0.000		
	1.101	11.984	0.075	0.899	81.63	
85 V AC/	2.813	11.984	0.194	2.325	82.65	
60 Hz	5.642	11.984	0.395	4.734	83.90	22.00
	8.581	11.968	0.596	7.133	83.12	83.09
	11.495	11.968	0.794	9.503	82.67	
	0.013	11.984	0.000	0.000		
	1.089	11.984	0.075	0.899	82.53	
115 V AC/	2.741	11.984	0.194	2.325	84.82	
60 Hz	5.568	11.984	0.395	4.734	85.02	24.54
	8.451	11.968	0.596	7.133	84.40	84.54
	11.322	11.968	0.794	9.503	83.93	
	0.018	11.984	0.000	0.000		
	1.176	11.984	0.075	0.899	76.43	
230 V AC/	2.833	11.984	0.194	2.325	82.06	
50 Hz	5.711	11.984	0.395	4.734	82.89	22.00
	8.567	11.968	0.596	7.133	83.26	83.08
	11.300	11.968	0.794	9.503	84.09	
	0.025	11.984	0.000	0.000		
	1.218	11.984	0.075	0.899	73.79	
264 V AC/	2.876	11.984	0.194	2.325	80.84	
50 Hz	5.781	11.968	0.395	4.727	81.77	02.04
	8.640	11.968	0.596	7.133	82.56	82.04
	11.448	11.968	0.794	9.503	83.01	

Note:

Single-output (+12 V) configuration efficiency measurement was done by removing two LDO output circuits, and connecting +12 V output directly to the $V_{\rm CC}$ circuit; the actual board comes with LDO circuits. The overall circuit is not optimized for single-output configuration; the above efficiency data is for illustration only.



Measurement data and graphs

9.1 Efficiency curve

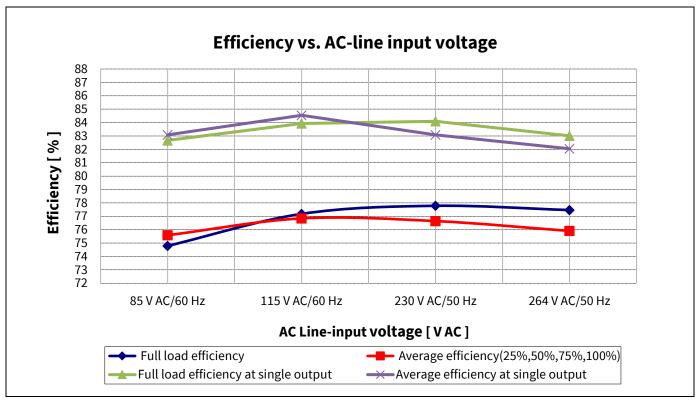


Figure 9 Efficiency vs. output load

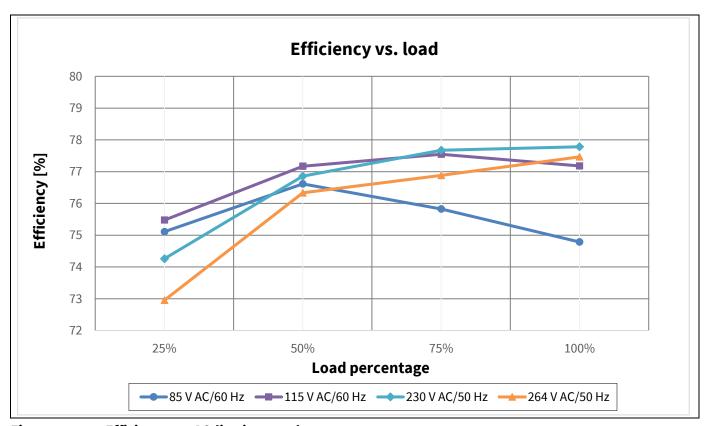


Figure 10 Efficiency vs. AC-line input voltage



Measurement data and graphs

9.2 Standby power

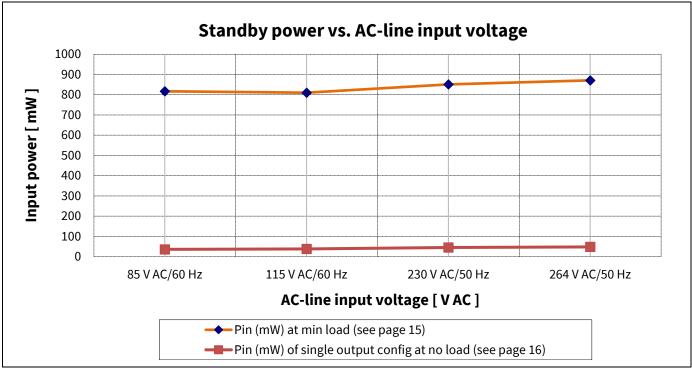


Figure 11 Standby power at minimum load vs. AC-line input voltage

9.3 Line and load regulation

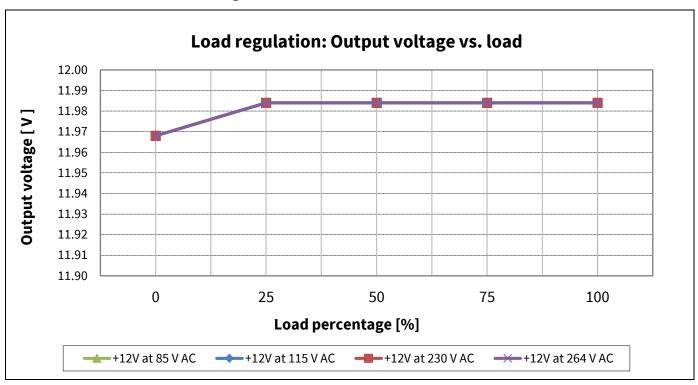


Figure 12 Output regulation vs. load at different AC-line input voltages



Measurement data and graphs

9.4 Maximum input power

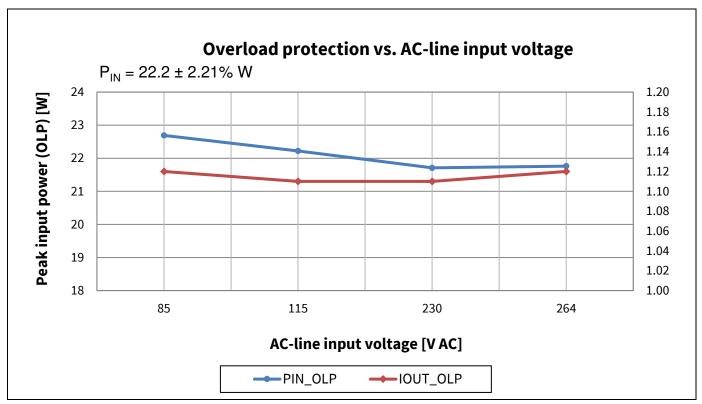


Figure 13 Maximum input power and output current (before overload protection) vs. AC-line input voltage

9.5 Surge immunity (EN 61000-4-5)

The reference board was subjected to surge immunity testing (±1 kV DM) according to EN 61000-4-5, at full load (resistive load). A test failure was defined as non-recoverable.

Table 7System surge immunity test result

Dossyintian	Test Level		Number of strikes				Tost result
Description	rest	Level	0°	90°	180°	270°	Test result
115/230 V AC	DM	±1 kV	3	3	3	3	Pass



Measurement data and graphs

Conducted emissions (EN 55022 class B) 9.6

The conducted EMI was measured by Schaffner (SMR4503) and followed the test standard of EN 55022 (CISPR 22) class B. The reference board was tested at full load (resistive load) at an input voltage of 115 V AC and 230 VAC.


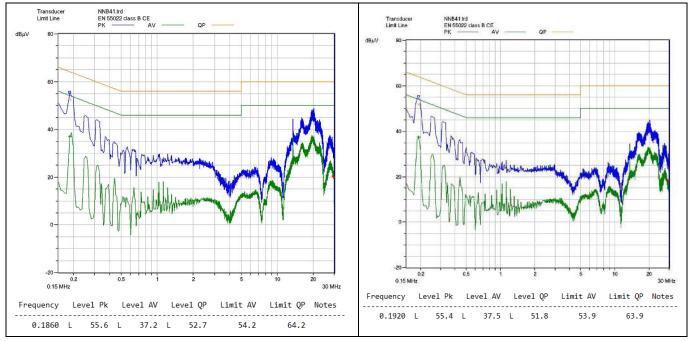


Figure 14 Conducted emissions at 115 V AC and full load on line (left) and neutral (right)

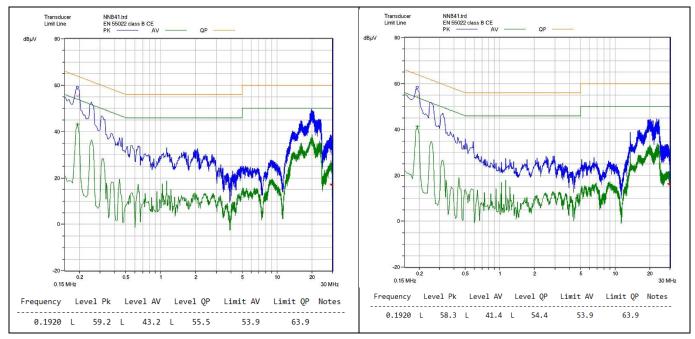

Conducted emissions at 230 V AC and full load on line (left) and neutral (right) Figure 15



Measurement data and graphs

9.7 Thermal measurement

Thermal measurement was done using an infrared thermography camera (FLIR-T62101) at an ambient temperature of 25°C taken after one hour running at full load. The temperature of the components was taken in an open-frame set-up.

Table 8 Thermal measurement of components (open-frame)

No.	Component	Temperature at 85 V AC (°C)	Temperature at 264 V AC (°C)
1	U1 (ICE5BR4780BZ)	75.8	72.3
2	TR1 (transformer)	52	56.5
3	BR1 (bridge diode)	51.5	39.1
4	D4 (15 V output diode)	62.3	62.1
5	D5 (12 V output diode)	79.1	81.6
6	D6 (5 V output diode)	67.6	69.8

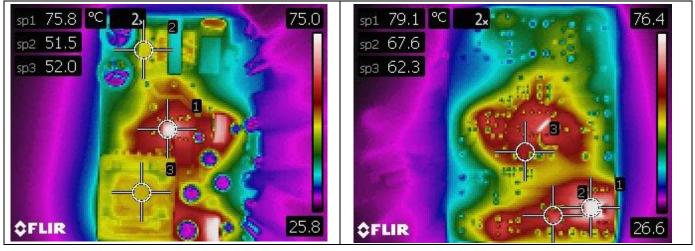


Figure 16 Top-layer (left) and bottom-layer (right) thermal image at 85 V AC input voltage

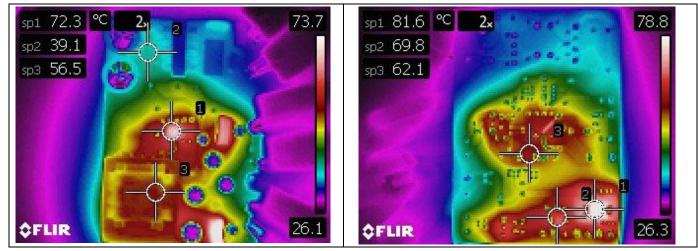


Figure 17 Top-layer (left) and bottom-layer (right) thermal image at 264 V AC input voltage



Measurement data and graphs

9.8 18 V rail regulation (LDO input)

As the 15 V output via a LDO is derived from the 18 V rail from the transformer which is also shared by the CoolSET™ V_{CC}, there are several design goals to achieve during normal operating conditions:

- Avoid V_{cc} UVLO (10 V typ.)
- Avoid V_{cc} OVP (25.5 V typ.)
- Meet the specification of the LDO: $(V_{OUT} + 1 \sim 2 \text{ V}) \leq V_{IN} \leq 30 \text{ V}$; load dependent

From the chart and table below, the 18 V rail is operating between 18.52 V and 21.77 V under different load combinations and line conditions, which is well within the design objectives outlined above.

Table 9 +18 V rail line and load regulation

Conditions	12 V/40 mA 5 V/0 A 15 V/0 A (V)	12 V/40 mA 5 V/5 mA 15 V/5 mA (V)	12 V/0.8 A 5 V/5 mA 15 V/5 mA (V)	12 V/0.8 A 5 V/0.3 A 15 V/0.15 A (V)
85 V AC/60 Hz	18.74	18.57	21.77	18.67
115 V AC/60 Hz	18.73	18.53	21.76	18.67
230 V AC/50 Hz	18.74	18.53	21.39	18.65
264 V AC/50 Hz	18.74	18.52	21.46	18.66

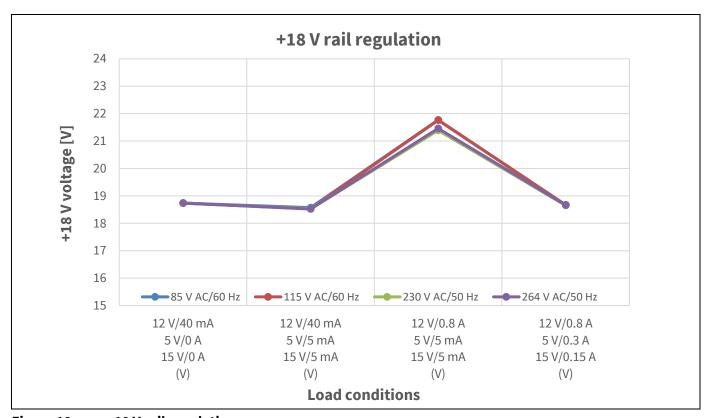


Figure 18 +18 V rail regulation



Waveforms and oscilloscope plots

Waveforms and oscilloscope plots 10

All waveforms and scope plots were recorded with a Teledyne LeCroy HDO4034 oscilloscope.

Start-up at full load 10.1

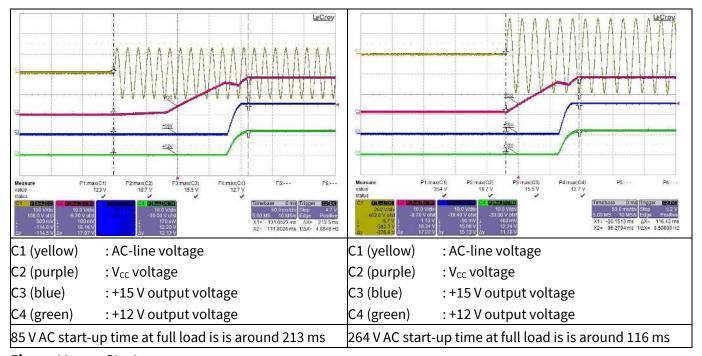


Figure 19 Start-up

Soft-start at full load 10.2


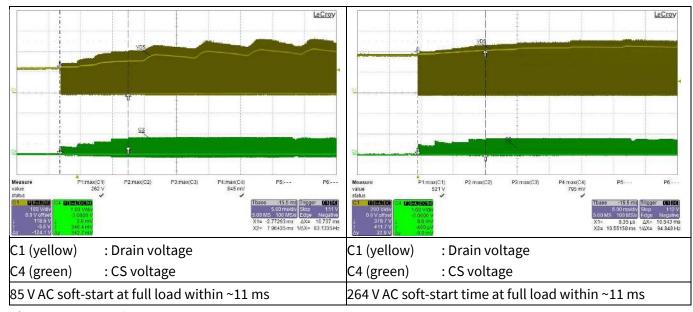


Figure 20 **Soft-start**

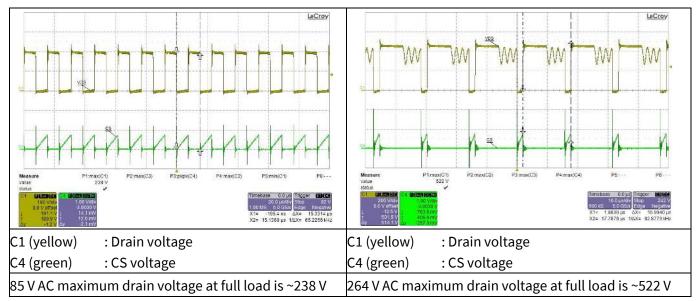

Waveforms and oscilloscope plots

Drain and CS voltage at full load 10.3



Drain and CS voltage Figure 21

Frequency jittering and modulated gate drive 10.4

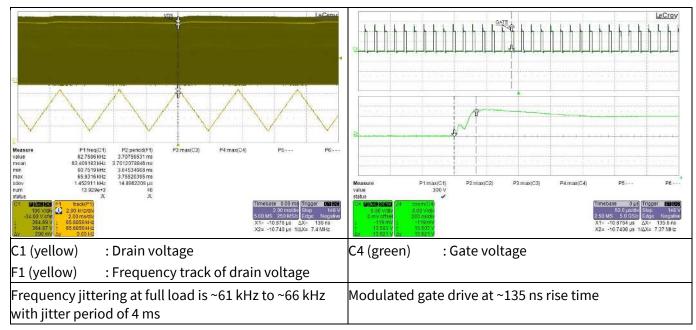


Figure 22 Frequency jittering and modulated gate drive



Waveforms and oscilloscope plots

10.5 Load-transient response


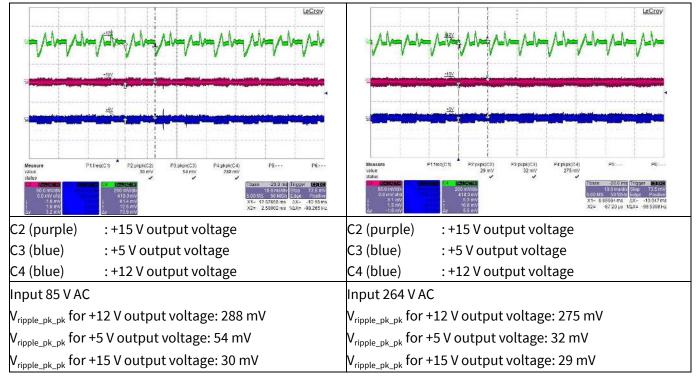


Figure 23 Load-transient response (+12 V output load change from 25 percent to 100 percent at 0.4 A/µs slew rate, 100 Hz, +15 V output and +5 V output load are fixed at full load; 20 MHz bandwidth and 10 μF electrolytic capacitor in parallel with 0.1 μF ceramic capacitor)

Output ripple voltage at full load 10.6

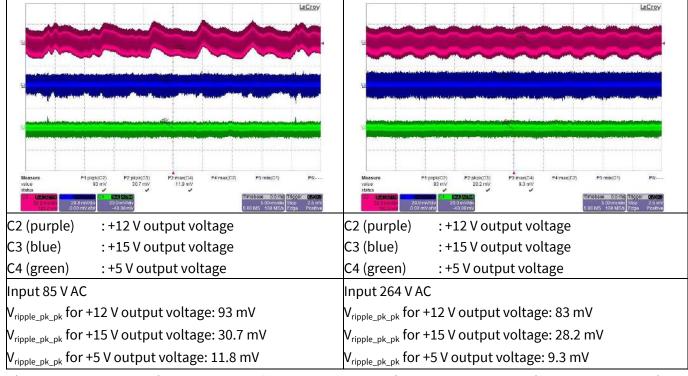


Output ripple voltage at full load. Probe terminals are decoupled with 10 μ F electrolytic Figure 24 and 0.1 µF ceramic capacitors. Oscilloscope is bandwidth filter limited to 20 MHz



Waveforms and oscilloscope plots

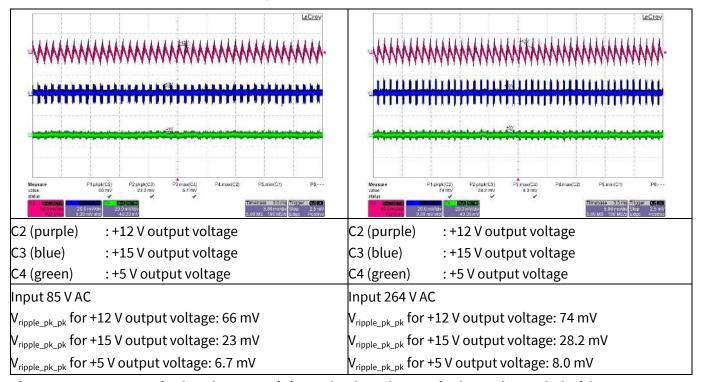Output ripple voltage at ABM (minimum load) 10.7



Output ripple voltage at minimum load. Probe terminals are decoupled with 10 µF Figure 25 electrolytic and 0.1 µF ceramic capacitors. Oscilloscope is bandwidth filter limited to 20 MHz

10.8 **Entering ABM**

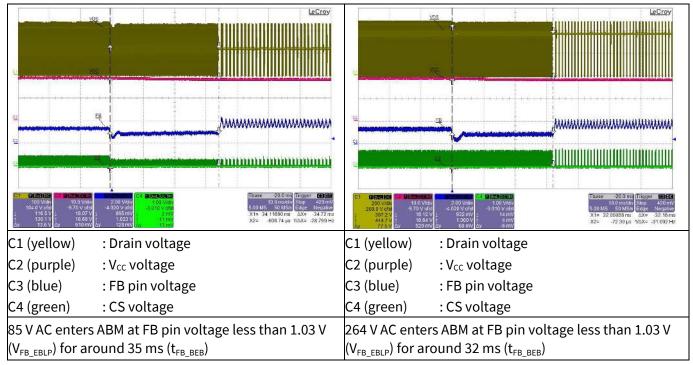


Figure 26 **Entering ABM**



Waveforms and oscilloscope plots

10.9 **During ABM**

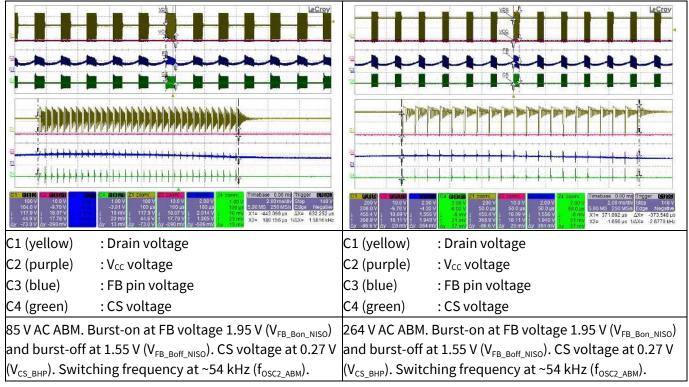


Figure 27 **During ABM**

10.10 **Leaving ABM**

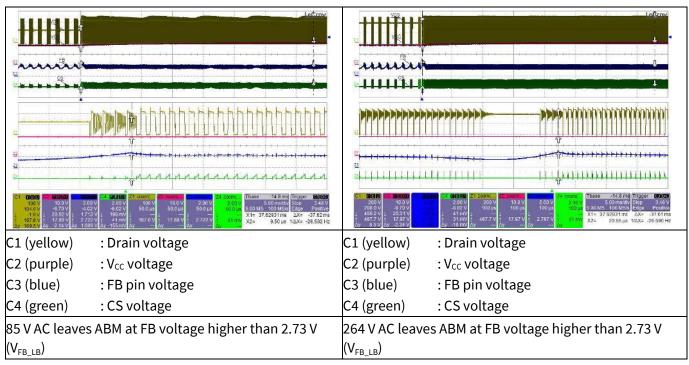


Figure 28 **Leaving ABM**



Waveforms and oscilloscope plots

10.11 **Vcc OV/UV protection**

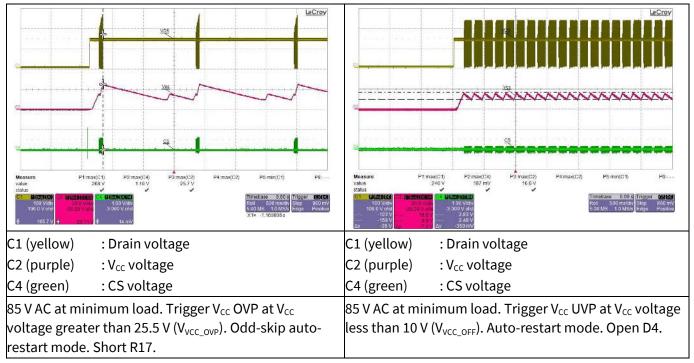


Figure 29 V_{cc} OV/UV protection

Overload protection 10.12

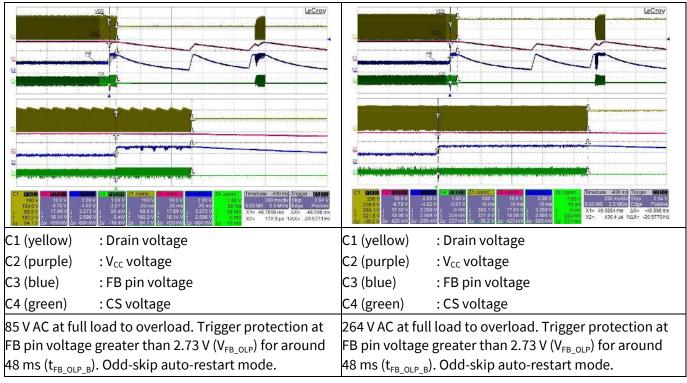


Figure 30 **Overload protection**



Appendix A: Transformer design and spreadsheet [3]

Appendix A: Transformer design and spreadsheet [3] 11

Calculation tool for FF flyback converter using fifth-generation CoolSET™ (version 1.1)

Project:	REF_5BR4780BZ_15W1
Application:	Aux for outdoor air-conditioner unit
CoolSET™:	ICE5BR4780BZ
Date:	7 December 2021
Revision:	V1.1

Notes:

Enter design variables in orange-colored cells

Read design results in green-colored cells

Equation numbers are according to the design guide

Component designators refer to the calculation tool

Select component values based on standard values available

Voltage/current rating does not include design margin, voltage spikes and transient currents In "Output regulation", only fill in either isolated or non-isolated, whichever is applicable							
111	output regui	Description	Eq.#	Parameter	Unit	Value	
Inpu	Input, output, CoolSET™ specs		-4."	- arameter	· · · · ·	ratuc	
	Line input	i e					
	Input	Minimum AC input voltage		V _{ACMin}	[V]	85	
	Input	Maximum AC input voltage		V _{ACMax}	[V]	264	
	Input	Line frequency		f _{AC}	[Hz]	60	
	Input	Bus capacitor DC ripple voltage		V _{DCRipple}	[V]	36	

Output 1	l specs
----------	---------

Input	Output voltage 1		V _{Out1}	[V]	12
Input	Output current 1		I _{Out1}	[A]	0.80
Input	Forward voltage of output diode 1		V _{FOut1}	[V]	0.6
Input	Output ripple voltage 1		V _{OutRipple1}	[V]	0.1
Result	Output power 1	Eq. 001	P _{Out1}	[W]	9.6
Result	Output load weight 1	Eq. 004	K _{L1}		0.65

Output 2 specs

Input	Output voltage 2		V _{Out2}	[V]	8
Input	Output current 2		I _{Out2}	[A]	0.3
Input	Forward voltage of output diode 2		V _{FOut2}	[V]	0.3
Input	Output ripple voltage 2		V _{OutRipple2}	[V]	0.5
Result	Output power 2	Eq. 002	P _{Out2}	[W]	2.4
Result	Output load weight 2	Eq. 005	K _{L2}		0.16

Auxiliary

Input	V _{CC} voltage		V _{Vcc}	[V]	18
Input	V _{CC} current			[A]	0.15
Input	Forward voltage of output diode 3		V _{FOut3}	[V]	0.4
Input	Forward voltage of V _{CC} diode (D2)		V _{F Vcc}	[V]	0.6
Result	Output power 3	Eq. 002	P _{Out2}	[W]	2.7

Power

Input	Efficiency		η		0.8
Result	Nominal output power	Eq. 003	PoutNom	[W]	14.70
Input	Maximum output power for overload protection		P _{OutMax}	[W]	15
Result	Maximum input power for overload protection	Eq. 006	P _{InMax}	[W]	18.75
Input	Minimum output power		PoutMin	[W]	1



Appendix A: Transformer design and spreadsheet [3]

Controller/CoolSET™

	Controller/CoolSET™			ICE5BR4780BZ
Input	Switching frequency	fs	[Hz]	65000
Input	Targeted max. drain source voltage	V _{DSMax}	[V]	700
Input	Max. ambient temperature	T _{amax}	[°C]	50

Diode bridge and input capacitor

Diode bridge

Input	Power factor		cosφ		0.6
Result	Maximum AC input current	Eq. 007	I _{ACRMS}	[A]	0.390
Result	Peak voltage at V _{ACMax}	Eq. 008	$V_{DCMaxPk}$	[V]	373.35

Input capacitor

Result	Peak voltage at V _{ACMin}	Eq. 009	V _{DCMinPk}	[V]	120.21
Result	Selected minimum DC input voltage	Eq. 010	$V_{DCMinSet}$	[V]	95.21
Result	Discharging time at each half-line cycle	Eq. 011	T _D	[ms]	6.59
Result	Required energy at discharging time of input capacitor	Eq. 012	W _{In}	[Ws]	0.13
Result	Calculated input capacitor	Eq. 013	C _{INCal}	[μF]	45.90
Input	Select input capacitor (C1)		Cin	[μF]	44
Result	Calculated minimum DC input voltage	Eq. 015	V _{DCMin}	[V]	94.14

Transformer design

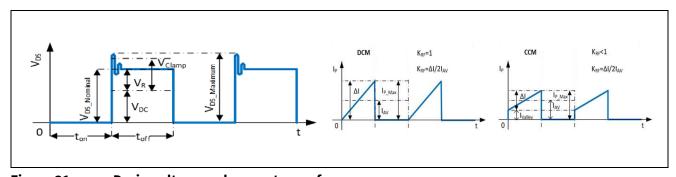


Figure 31 Drain voltage and current waveform

Primary inductance and winding currents

Input	Reflection voltage		V _{RSET}	[V]	96
Result	Maximum duty cycle	Eq. 016	D _{Max}		0.50
Input	Select current ripple factor		K _{RF}		1
Result	Primary inductance	Eq. 017	L _P	[H]	9.27E-04
Result	Primary turn-on average current	Eq. 018	I _{AV}	[A]	0.39
Result	Primary peak-to-peak current	Eq. 019	ΔΙ	[A]	0.79
Result	Primary peak current	Eq. 020	I _{PMax}	[A]	0.79
Result	Primary valley current	Eq. 021	I _{Valley}	[A]	0.00
Result	Primary RMS current	Eq. 022	I _{PRMS}	[A]	0.324

Select core type

Input	Select core type			2
Result	Core type			E25/13/7
Result	Core material			N87
Result	Maximum flux density	B _{Max}	[T]	0.3
Result	Cross-sectional area	A _e	[mm²]	52
Result	Bobbin width	BW	[mm]	15.6
Result	Winding cross-section	A _N	[mm²]	61
Result	Average length of turn	l _N	[mm]	50



Appendix A: Transformer design and spreadsheet [3]

Winding calculation

Result	Calculated minimum number of primary turns	Eq. 023	N _{PCal}	Turns	46.87
Input	Select number of primary turns		N _P	Turns	58
Result	Calculated number of secondary 1 turns	Eq. 024	N _{S1Cal}	Turns	7.61
Input	Select number of secondary 1 turns		N _{S1}	Turns	8
Result	Calculated number of secondary 2 turns	Eq. 025	N _{S2Cal}	Turns	5.01
Input	Select number of secondary 2 turns		N _{S2}	Turns	5
Result	Calculated number of auxiliary turns	Eq. 026	N _{VccCal}	Turns	11.75
Input	Select number of auxiliary turns		N _{Vcc}	Turns	12
Result	Calculated V _{CC} voltage	Eq. 027	V _{VccCal}	[V]	18.40

Post calculation

Result	Primary to secondary 1 turns ratio	Eq. 028	N _{PS1}		7.25
Result	Primary to secondary 2 turns ratio	Eq. 029	N _{PS2}		11.60
Result	Post-calculated reflected voltage	Eq. 030	V _{RPost}	[V]	91.35
Result	Post-calculated maximum duty cycle	Eq. 031	D _{MaxPost}		0.49
Result	Duty-cycle prime	Eq. 032	D _{Max} '		0.52
Result	Actual flux density	Eq. 033	B _{MaxAct}	[T]	0.242
Result	Maximum DC input voltage for CCM operation	Eq. 034	$V_{DCmaxCCM}$	[V]	99.09

Transformer winding design

Input	Margin according to safety standard		М	[mm]	0
Input	Copper space factor		f _{Cu}		0.4
Result	Effective bobbin window	Eq. 035	BW _E	[mm]	15.6
Result	Effective winding cross-section	Eq. 036	A _{Ne}	[mm²]	61.0
Input	Primary winding area factor		AF _{NP}		0.45
Input	Secondary 1 winding area factor		AF _{NS1}		0.30
Input	Secondary 2 winding area factor		AF _{NS2}		0.15
Input	Auxiliary winding area factor		AF _{NVcc}		0.10

Primary winding

Result	Calculated copper wire cross-sectional area	Eq. 037	A _{PCal}	[mm²]	0.1893
Result	Calculated maximum wire size	Eq. 038	AWG _{PCal}		24
Input	Select wire size		AWG _P		28
Input	Select number of parallel wire		nw _P		1
Result	Copper wire diameter	Eq. 039	d₽	[mm]	0.32
Result	Copper wire cross-sectional area	Eq. 040	A _P	[mm²]	0.0821
Result	Wire current density	Eq. 041	S _P	[A/mm ²]	3.94
Input	Insulation thickness		INS _P	[mm]	0.01
Result	Turns per layer	Eq. 042	NL_P	Turns/layer	45
Result	Number of layers	Eq. 043	Ln₽	Layers	2

Secondary 1 winding

Result	Calculated copper wire cross-sectional area	Eq. 044	A _{NS1Cal}	[mm²]	0.9150
Result	Calculated maximum wire size	Eq. 045	AWG _{S1Cal}		18
Input	Select wire size		AWG _{S1}		22
Input	Select number of parallel wire		nw _{S1}		1
Result	Copper wire diameter	Eq. 046	d _{S1}	[mm]	0.6465
Result	Copper wire cross-sectional area	Eq. 047	A _{S1}	[mm²]	0.3282
Result	Peak current	Eq. 048	I _{S1Max}	[A]	3.7355
Result	RMS current	Eq. 049	I _{S1RMS}	[A]	1.5557



Appendix A: Transformer design and spreadsheet [3]

Result	Wire current density	Eq. 050	S _{S1}	[A/mm ²]	4.74
Input	Insulation thickness		INS _{S1}	[mm]	0.02
Result	Turns per layer	Eq. 051	NL _{S1}	Turns/layer	8
Result	Number of layers	Eq. 052	Ln _{S1}	Layers	1

Secondary 2 winding

Result	Calculated copper wire cross-sectional area	Eq. 053	A _{NS2Cal}	[mm²]	0.7320
Result	Calculated maximum wire size	Eq. 054	AWG _{S2Cal}		19
Input	Select wire size		AWG _{S2}		24
Input	Select number of parallel wire		nw _{S2}		1
Result	Copper wire diameter	Eq. 055	d _{S2}	[mm]	0.5131
Result	Copper wire cross-sectional area	Eq. 056	A _{S2}	[mm²]	0.2068
Result	Peak current	Eq. 057	I _{S2Max}	[A]	1.4942
Result	RMS current	Eq. 058	I _{S2RMS}	[A]	0.6223
Result	Wire current density	Eq. 059	S _{S2}	[A/mm ²]	3.01
Input	Insulation thickness		INS _{S2}	[mm]	0.02
Result	Turns per layer	Eq. 060	NL _{S2}	Turns/layer	28
Result	Number of layers	Eq. 061	Ln _{S2}	Layers	1

RCD clamper and CS resistor

RCD clamper circuit

Input	Leakage inductance percentage		L _{LK%}	[%]	1
Result	Leakage inductance	Eq. 062	L _{LK}	[H]	9.27E-06
Result	Clamping voltage	Eq. 063	V _{Clamp}	[V]	235.30
Result	Calculated clamping capacitor	Eq. 064	C _{ClampCal}	[nF]	0.08
Input	Select clamping capacitor value (C2)		C _{clamp}	[nF]	1
Result	Calculated clamping resistor	Eq. 065	R _{clampCal}	[kΩ]	524.6
Input	Select clamping resistor value (R4)		R _{clamp}	[kΩ]	240

CS resistor

Input	CS threshold value from datasheet		V _{CS_N}	[V]	0.8
Result	Calculated CS resistor (R8A, R8B)	Eq. 066	R _{sense}	[Ω]	1.01

Output rectifier

Secondary 1 output rectifier

Secondar	y i output rectinei				
Result	Diode reverse voltage	Eq. 067	V _{RDiode1}	[V]	63.50
Result	Diode RMS current		I _{S 1RMS}	[A]	1.56
Input	Max. voltage undershoot at output capacitor		Δ V _{Out1}	[V]	0.5
Input	Number of clock periods		n _{cp1}		20
Result	Output capacitor ripple current	Eq. 068	I _{Ripple1}	[A]	1.33
Result	Calculated minimum output capacitor	Eq. 069	C _{Out1Cal}	[μF]	492
Input	Select output capacitor value (C152)		C _{Out1}	[μF]	560
Input	ESR (Z _{max}) value from datasheet at 100 kHz		R _{ESR1}	[Ω]	0.032
Input	Number of parallel capacitors		nc _{COut1}		1
Result	Zero frequency of output capacitor	Eq. 070	f _{ZCOut1}	[kHz]	8.88
Result	First-stage ripple voltage	Eq. 071	V _{Ripple1}	[V]	0.119535
Input	Select LC filter inductor value (L151)		L _{out1}	[μH]	4.7
Result	Calculated LC filter capacitor	Eq. 072	C _{LCCal1}	[μF]	68.3
Input	Select LC filter capacitor value (C153)		C _{LC1}	[μF]	220
Result	LC filter frequency	Eq. 073	f _{LC1}	[kHz]	4.95
Result	Second-stage ripple voltage	Eq. 074	V _{2ndRipple1}	[mV]	0.69



Appendix A: Transformer design and spreadsheet [3]

Result	Diode reverse voltage	Eq. 075	V _{RDiode2}	[V]	40.19
Result	Diode RMS current		I _{S2RMS}	[A]	0.62
Input	Max. voltage undershoot at output capacitor		∆ V _{Out1}	[V]	0.3
Input	Number of clock periods		n _{cp2}		20
Result	Output capacitor ripple current	Eq. 076	I _{Ripple2}	[A]	0.55
Result	Calculated minimum output capacitor	Eq. 077	C _{Out2Cal}	[μF]	308
Input	Select output capacitor value (C152)		C _{Out2}	[μF]	470
Input	ESR (Z _{max}) value from datasheet at 100 kHz		R _{ESR2}	[Ω]	0.032
Input	Number of parallel capacitors		nc _{COut2}		1
Result	Zero frequency of output capacitor	Eq 078	f _{ZCOut2}	[kHz]	10.58
Result	First stage ripple voltage	Eq 079	V _{Ripple2}	[V]	0.05

V_{cc} diode and capacitor

V_{CC} diode and capacitor

- 66	and capacitor				
Result	Auxiliary diode reverse voltage (D2)	Eq. 083	V _{RDiodeVCC}	[V]	95.65
Input	Soft-start time from datasheet		t _{ss}	[ms]	12
Input	I _{VCC,Charge3} from datasheet		I _{VCC_Charge3}	[mA]	3
Input	V _{CC} on-threshold		V _{VCC_ON}	[V]	16
Input	Vcc off-threshold		V _{VCC_OFF}	[V]	10
Result	Calculated V _{CC} capacitor	Eq. 084	Cvcccal	[μF]	6.00
Input	Select V _{CC} capacitor (C3)		C _{VCC}	[μF]	22
Input	V _{CC} short threshold from datasheet		V _{VCC_SCP}	[V]	1.1
Input	lvcc_charge1 from datasheet		I _{VCC_Charge1}	[mA]	0.2
Result	Start-up time	Eq. 085	t _{StartUp}	[ms]	230.267

Calculation of losses

Input diode bridge

Input	Diode bridge forward voltage		V_{FBR}	[V]	0.7
Result	Diode bridge power loss	Eq. 086	P _{DIN}	[W]	0.51

Transformer copper

Result	Primary winding copper resistance	Eq. 087	R _{PCu}	$[m\Omega]$	607.52
Result	Secondary 1 winding copper resistance	Eq. 088	R _{S1Cu}	$[m\Omega]$	20.96
Result	Secondary 2 winding copper resistance	Eq. 089	R _{S2Cu}	$[m\Omega]$	20.79
Result	Primary winding copper loss	Eq. 090	P _{PCu}	[mW]	63.64
Result	Secondary 1 winding copper loss	Eq. 091	P _{S1Cu}	[mW]	50.80
Result	Secondary 2 winding copper loss	Eq. 092	P _{S2Cu}	[mW]	8.06
Result	Total transformer copper loss	Eq. 093	P _{Cu}	[W]	0.1215

Output rectifier diode

Result	Secondary 1 diode loss	Eq. 094	P _{Diode1}	[W]	0.93
Result	Secondary 2 diode loss	Eq. 095	P _{Diode2}	[W]	0.19

RCD clamper circuit

Result	RCD clamper loss	Eq. 096	P _{Clamper}	[W]	0.26

CS resistor

Result CS resistor loss	Eq. 097 P	P _{CS} [W]	0.11
-------------------------	-----------	---------------------	------

MOSFET

Input	R _{DS(on)} from datasheet	$R_{DS(on)}$ at T_A = 125°C	[Ω]	8.69
Input	C _{o(er)} from datasheet	C _{o(er)}	[pF]	3
Input	External drain-to-source capacitance	C _{DS}	[pF]	0



Appendix A: Transformer design and spreadsheet [3]

Result	Switch-on loss at minimum AC input voltage	Eq. 098	Psonminac	[W]	0.0034
Result	Conduction loss at minimum AC input voltage	Eq. 099	PcondMinAC	[W]	0.9103
Result	Total MOSFET loss at minimum AC input voltage	Eq. 100	P _{MOSMinAC}	[W]	0.9137
Result	Switch-on loss at maximum AC input voltage	Eq. 101	P _{SONMaxAC}	[W]	0.0211
Result	Conduction loss at maximum AC input voltage	Eq. 102	PcondMaxAC	[W]	0.2295
Result	Total MOSFET loss at maximum AC input voltage	Eq. 103	P _{MOSMaxAC}	[W]	0.2506
Result	Total MOSFET loss (from minimum or maximum AC)		P _{MOS}	[W]	0.9137

Controller

Input	Controller current consumption		I _{VCC_Normal}	[mA]	1.7
Result	Controller loss	Eq. 104	P _{Ctrl}	[W]	0.0311

Efficiency after losses

Re	esult	Total power loss	Eq. 105	P _{Losses}	[W]	3.07
Re	esult	Post calculated efficiency	Eq. 106	η _{Post}	%	83.02%

CoolSET™/MOSFET temperature

CoolSET™/MOSFET temperature

Input	Enter thermal resistance junction-ambient (include copper pour)		R _{thJA_As}	[°K/W]	80.0
Result	Temperature rise	Eq. 107	ΔΤ	[°K]	73.1
Result	Junction temperature at T _{jmax}	Eq. 108	T _{jmax}	°C	123.1

Note: T_{jmax} was calculated by using maximum $R_{DS(on)}$ at 125°C with footprint copper area as heatsink, only for reference.

Output regulation (non-isolated)

	, ,				
Input	Error amplifier reference voltage		V _{ERR_REF}	[V]	1.8
Input	Weighted regulation factor of V _{Out1}		W ₁	%	100%
Input	Select voltage divider RO1 (R11)		R ₀₁	[kΩ]	39
Result	Calculated voltage divider RO2	Eq. 125	R _{02Cal}	[kΩ]	221.00
Input	Select voltage divider RO2 (R153)		R ₀₂	[kΩ]	220.0

Final design

Electrical

ical		
Minimum AC voltage	[V]	85
Maximum AC voltage	[V]	264
Maximum input current	[A]	0.22
Minimum DC voltage	[V]	96
Maximum DC voltage	[V]	373
Maximum output power	[W]	15.0
Output voltage 1	[V]	12.0
Output ripple voltage 1	[mV]	0.7
Output voltage 2	[V]	8.0
Output ripple voltage 2	[mV]	0.0
Transformer peak current	[A]	0.79
Maximum duty cycle		0.49
Reflected voltage	[V]	91
Copper losses	[W]	0.12
MOSFET losses	[W]	0.90
Sum losses	[W]	3.17
Efficiency	[Percent]	82.57%

Transformer

Core type		E25/13/7
Core material		N87
Effective core area	[mm²]	52
Maximum flux density	[mT]	242
Inductance	[μH]	924
Margin	[mm]	0
Primary turns	Turns	58
Primary copper wire size	AWG	28
Number of primary copper wires in parallel		1



Appendix A: Transformer design and spreadsheet [3]

Primary layers		Layer	2
Secondary 1 turns (N _{S1})		Turns	8
Secondary 1 copper wire size		AWG	22
Number of secondary 1 copper wires in parallel			1
Secondary 1 layers		Layer	1
Secondary 2 turns(N ₅₂)		Turns	5
Secondary 2 copper wire size		AWG	24
Number of secondary 2 copper wires in parallel			1
Secondary 2 layers		Layer	1
Auxiliary turns		Turns	12
Leakage inductance		[μH]	13.9
Components			
Input capacitor (C1)		[μF]	47.0
Secondary 1 output capacitor (C152)		[μF]	560.0
Secondary 1 output capacitor in parallel			1.0
Secondary 1 LC filter inductor (L151)		[μH]	4.7
Secondary 1 LC filter capacitor (C153)		[μF]	220.0
V _{CC} capacitor (C3)		[μF]	470.0
Sense resistor (R8A, R8B)		[Ω]	1.0
Clamping resistor (R4)		[k Ω]	0.0
Clamping capacitor (C2)		[nF]	0.0
High-side DC input voltage divider/resistor (R3A, R3B, R3C)		[M Ω]	22.0
Low-side DC input voltage divider/resistor (R7)		[k Ω]	1.01
Regulation components (non-isolated)			
Voltage divider (R11)	RO1	[kΩ]	39.0
Voltage divider (V _{Out1} sense) (R153)	RO2	[kΩ]	220.0



Appendix B: WE transformer specification

Appendix B: WE transformer specification 12

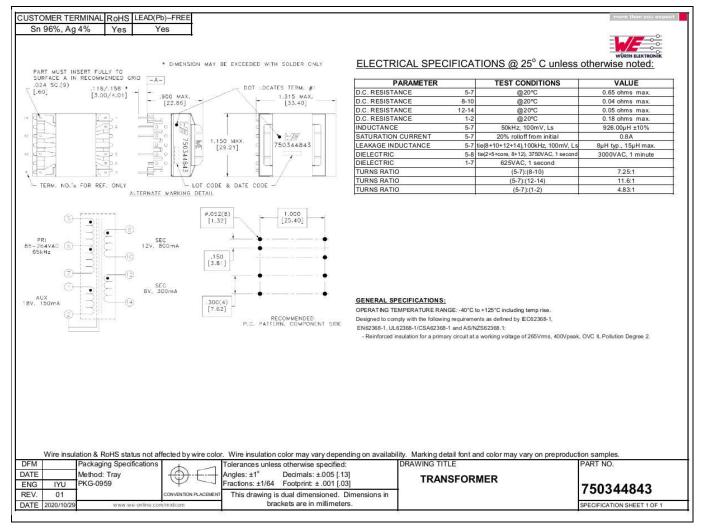


Figure 32 **WE transformer specification**



References

References **13**

- [1] Infineon Technologies AG: ICE5BR4780BZ Datasheet (V 1.0); 2022-02-22; ICE5BR4780BZ Datasheet
- [2] Infineon Technologies AG: 5th Generation Fixed-Frequency Design Guide (V 2.1); 2019-07-24; 5th **Generation Fixed-Frequency Design Guide**
- Infineon Technologies AG: Calculation tool for fixed-frequency flyback converter using fifth-generation [3] CoolSET™ (V 1.1); 2018-02-26; Calculation tool fixed-frequency CoolSET™ 5th generation – ICE5xRxxxxxZS



Revision history

Revision history

Document version	Date of release	Description of changes
V 1.0	2022-06-15	First release

Trademarks

All referenced product or service names and trademarks are the property of their respective owners.

Edition 2022-06-15
Published by
Infineon Technologies AG
81726 Munich, Germany

© 2022 Infineon Technologies AG. All Rights Reserved.

Do you have a question about this document?

Email: erratum@infineon.com

Document reference AN_2101_PL21_2105_093015

IMPORTANT NOTICE

The information contained in this application note is given as a hint for the implementation of the product only and shall in no event be regarded as a description or warranty of a certain functionality, condition or quality of the product. Before implementation of the product, the recipient of this application note must verify any function and other technical information given herein in the real application. Infineon Technologies hereby disclaims any and all warranties and liabilities of any kind (including without limitation warranties of non-infringement of intellectual property rights of any third party) with respect to any and all information given in this application note.

The data contained in this document is exclusively intended for technically trained staff. It is the responsibility of customer's technical departments to evaluate the suitability of the product for the intended application and the completeness of the product information given in this document with respect to such application.

For further information on the product, technology, delivery terms and conditions and prices please contact your nearest Infineon Technologies office (www.infineon.com).

WARNINGS

Due to technical requirements products may contain dangerous substances. For information on the types in question please contact your nearest Infineon Technologies office.

Except as otherwise explicitly approved by Infineon Technologies in a written document signed by authorized representatives of Infineon Technologies, Infineon Technologies' products may not be used in any applications where a failure of the product or any consequences of the use thereof can reasonably be expected to result in personal injury.