

# ***AN-1602 LMH7322 Dual Comparator Evaluation Board***

---

---

---

## **1 General Description**

This board is designed to demonstrate the LMH7322 dual comparator with RSPECL outputs. It will facilitate the evaluation of the LMH7322 in most of the possible configurations. There is one part containing two comparators mounted onto this board. The intention of this board is to demonstrate the conversion of an analog signal to a digital presentation at LVDS levels and to translate this LVDS signal to RSECL levels. The LATCH function can be evaluated using the two switches mounted on the edge of the board. Two test points located between the comparators allows checking the LVDS levels while the output signals are fed to two SMA connectors that feed the signals on a 50  $\Omega$  basis to any scope or analyzer. To demonstrate the hysteresis functionality both hysteresis resistors are mounted on header pins, which makes them changeable in a convenient manner. Only two supply voltages are needed to make this setup work. The positive supply is +2.5 V and the negative supply is –5.2 V.

## **2 Basic Operation**

The complete schematic consists of two comparators that show the conversion of analog to LVDS and LVDS to RSECL levels.

### **2.1 Input Conditions**

The input signal is connected to an SMA connector and feed to the non-inverting input of the first comparator. This is a DC path and referenced to ground by a 50  $\Omega$  (R3) resistor. The inverting input is also referenced to ground via a 50  $\Omega$  (R4) resistor. If no signal is present and both inputs are referenced to the same voltage, the comparator may oscillate if no precautions are taken. Adding a hysteresis resistor introduces a small voltage around the trip point, which prevents the input stage from continuously switching due to noise or other uncontrolled events. The hysteresis voltage can be varied by changing the resistor value connected to J3 (input stage) or J4 (output stage). The resistor can be varied between its extremes of being shorted or being open. Both situations are allowed. The short means that the highest hysteresis voltage is set and an open connection means that there is no hysteresis voltage set. This last situation means that there is the highest risk for oscillations if no signal or a very small signal is applied. It is desirable to use some hysteresis while working with very small and/ or low frequency signals.

### **2.2 The Latch Function**

Both comparators of the LMH7322 have a separate LATCH function, which means that every comparator can be activated or deactivated by a separate LATCH signal. Both latch functions use complementary signals and are connected to the two mini-switches (S1 and S2) situated on the border of the printed circuit board (PCB). If these switches are placed in the 'ON' state, the latch function is active and the outputs are frozen.

### 2.3 Output Configuration

The outputs of every comparator need to be biased with some current drawn from the Q or  $\bar{Q}$  pin. To activate these ECL configured outputs every output has a resistor connected to the most negative supply voltage. This assures that there is always a current flowing out of the pin. The higher the resistor value, the less current is drawn from the pin. Optimizing for high speed means the resistor should have a relatively low value causing a current of 10 to 20 mA to flow out of every pin. A standard termination of 50  $\Omega$  to the termination voltage of 2 V below the  $V_{CCO}$ , means that the output current for '1' is 18 mA and for '0' is 10 mA. The maximum output current per the output pin is about 40 mA or even more without damaging the device. This means that a system designer has a wide range to vary the bias resistor. Be aware that high resistor values result in slower response times of the comparator, but using values that are too low will also make the response times slower while raising the power consumption. The output signals are connected to SMA connectors via a coupling capacitor of 100 nF (C5 and C6) directly soldered onto the board. In parallel with this capacitor are two header sockets (J1 and J2) that can be used for a larger capacitor. This will lower the 3 dB point of the coupling capacitor and the 50  $\Omega$  output termination resistor present on any scope or analyzer. The 3 dB point using only the 100 nF capacitor is about 30 kHz. When placing a capacitor of 10  $\mu$ F in parallel with the 100 nF, the 3 dB point will be lowered to about 300 Hz. This AC connection is done for testing purposes only, because in this manner no external termination voltage is needed. The test board can now be tested by a direct connection to a scope or analyzer with a 50  $\Omega$  termination. If a DC connection is needed to analyze the board the two header sockets can be easily connected using a bended lead.

### 2.4 Layout Considerations

The setup of the PCB is simple and consists of a double sided PCB with a ground plane on the bottom side and the components and transmission lines on the top side.

### 2.5 Analog to LVDS Converter

The input transmission line is 50  $\Omega$  and is as short as possible. The LVDS output line from the analog to LVDS converter (the first comparator) is designed as a 100  $\Omega$  co-planar transmission line terminated with a 100  $\Omega$  termination resistor positioned as close as possible to the input of the LVDS to RSECL converter. Close to this termination resistor are two test points and two ground connections. This makes it possible to test the LVDS signals with a standard probe with a ground lead or with a special differential probe, which will give the best results. The power connections,  $V_{CCI}$  and  $V_{CCO}$ , are connected together and need a supply voltage of +2.5 V. The  $V_{EE}$  supply is -5.2 V and is not critical but is used because this is a standard ECL supply value.

### 2.6 LVDS TO RSECL Converter

The setup of the LVDS to RSECL converter (the second comparator) is roughly the same but has two different supplies for the  $V_{CCI}$  and  $V_{CCO}$ . This comparator has to produce (RS)ECL levels and therefore the  $V_{CCO}$  is connected to the ground, while the  $V_{EE}$  is connected to -5.2 V. Decoupling capacitors are always placed as close as possible to the appropriate pins. Every comparator has a resistor for setting the hysteresis voltage and this resistor is a standard resistor placed into two header sockets, which makes it easy to change its value.


### 2.7 External Connections

The connections for input and output signals are SMA connectors. The supply voltages are connected via a 3 pole MSTB connector.


### 3 Measurement Hints

For good high speed results, it is recommended that measurements are done via the SMA output connections. To obtain best results it is necessary to have terminated both outputs, otherwise reflections from one output will disturb the signal integrity on the other. If a probe is needed, be sure to connect via short leads and do not use the standard ground leads with alligator clips that are several inches long. These cause ringing while measuring pulsed signals and lead to the unwanted pick-up of spurious signals. The use of a differential probe is strongly recommended to view the real LVDS output signal, because of the probe's low parasitic capacitance and ease of use. Alternatively, it is possible to use two single probes and construct the LVDS signal by combining both signals.


### 4 Board Schematic

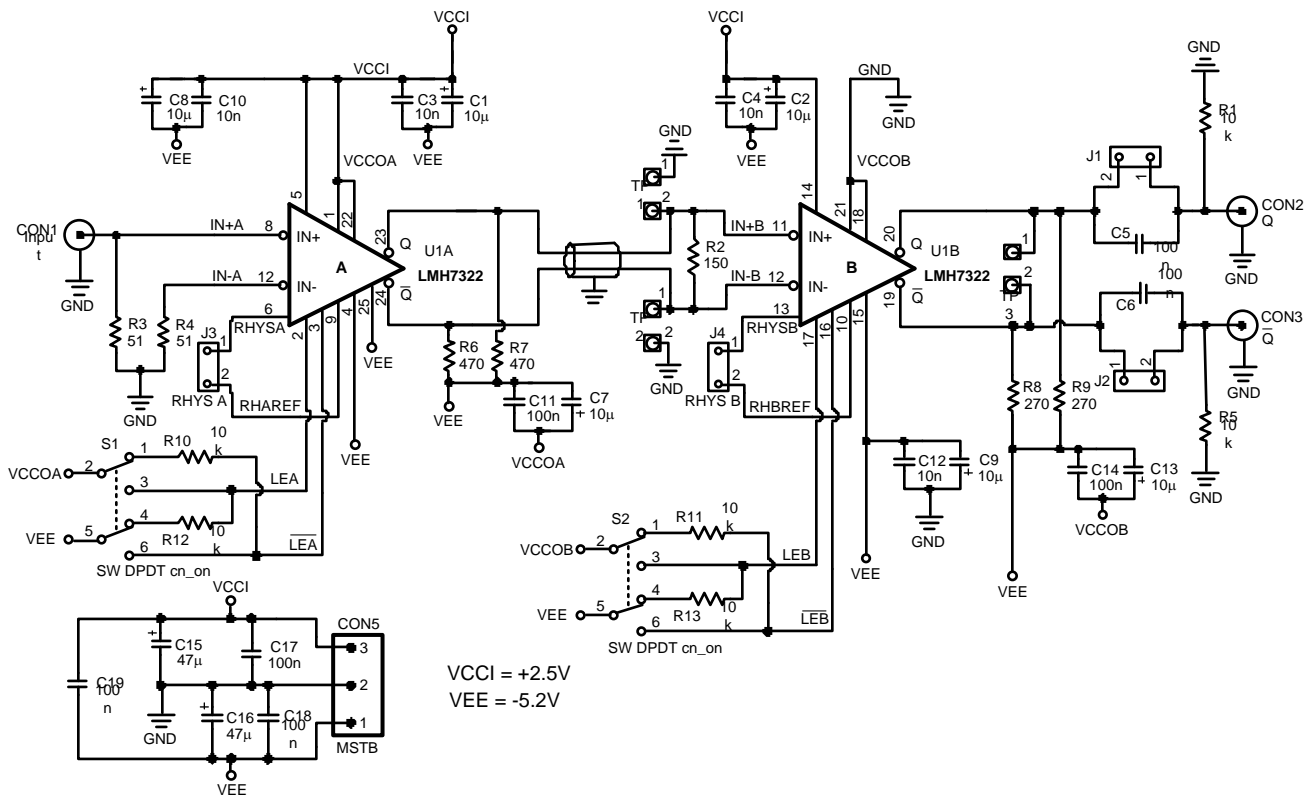

**5 Board Layout**

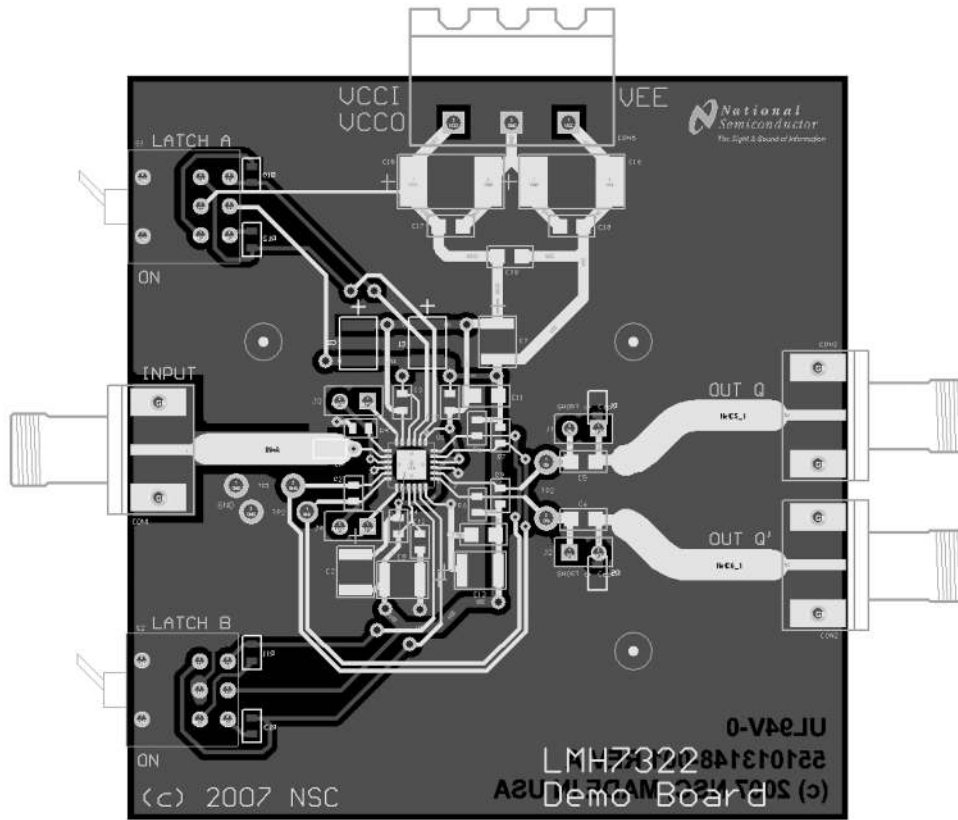

**Figure 1. PCB View**

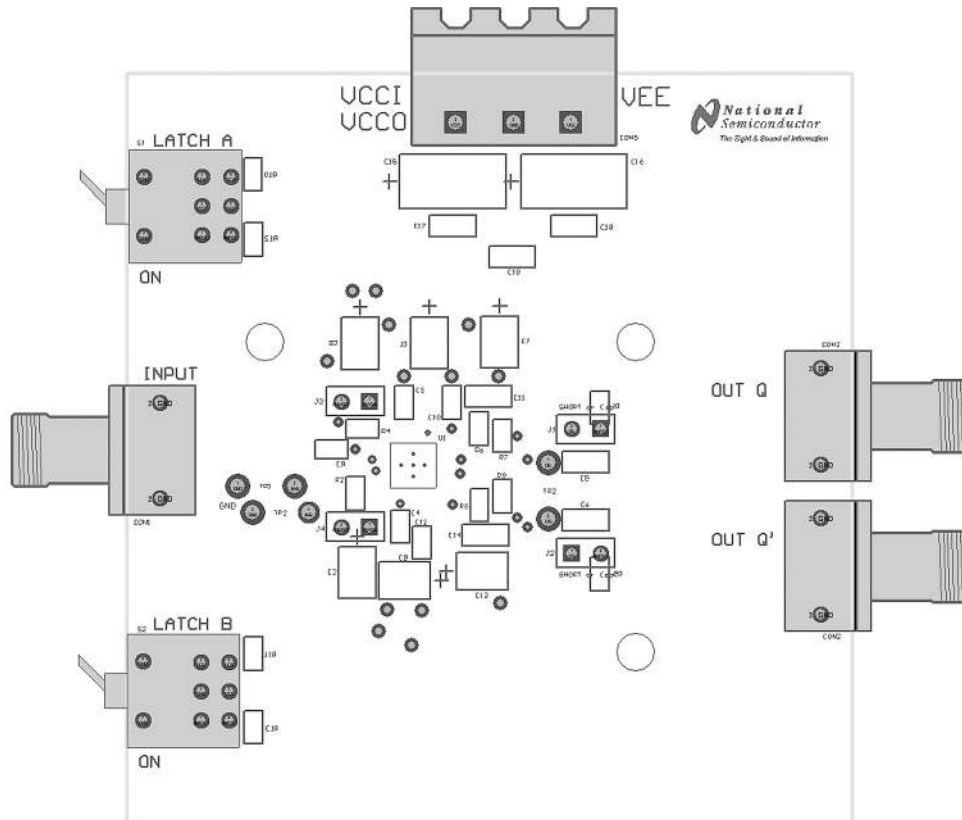

**Figure 2. Component View**

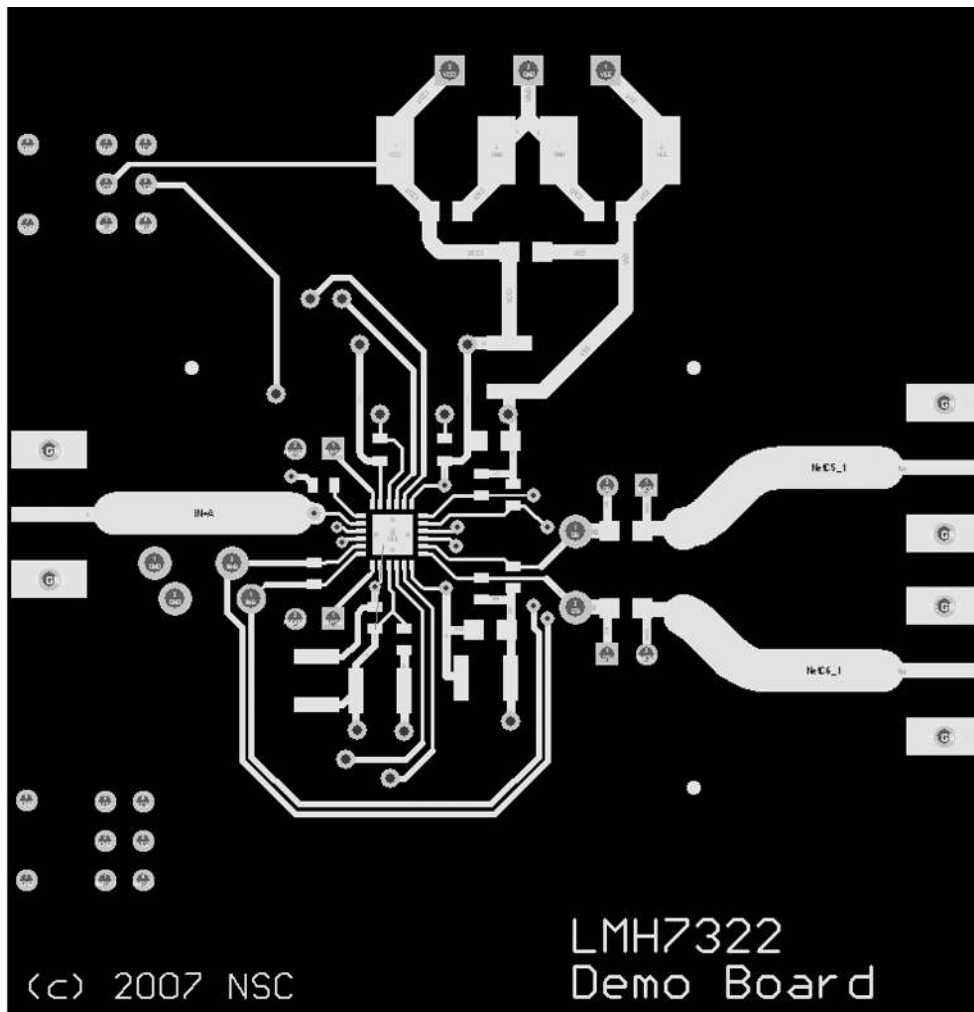


Figure 3. Component View

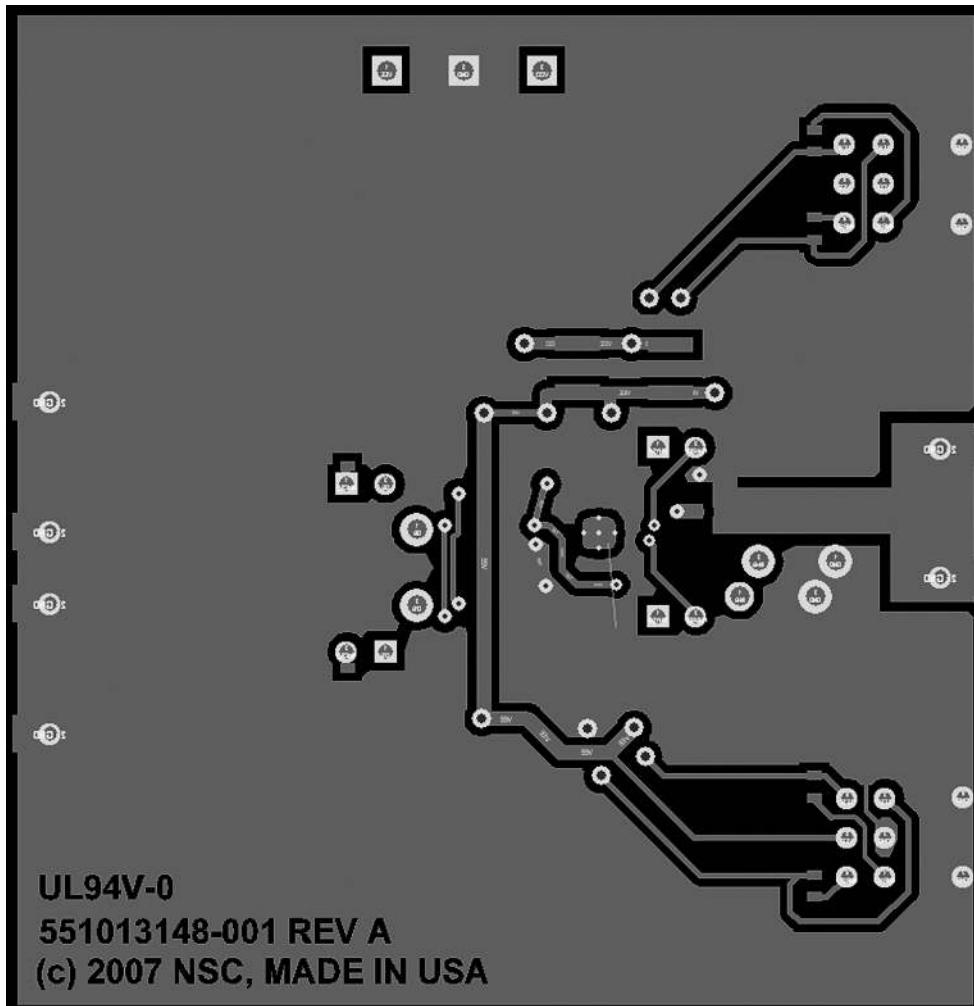


Figure 4. Tracks Bottom Side

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)