

VDSL

VDSL Over POTS

Solution Products



TBU-PL085-200-WH



TBU-CA085-500-WH



2020-42T-C4LF



B1250T

Design Kit



PN-DESIGNKIT-19

Objective

VDSL circuits are sometimes combined with Plain Old Telephone Service (POTS) circuits. This solution protects those communication ports against surge and power contact threats.

Solution

- 1 TBU[®] High-Speed Protector:
TBU-PL085-200-WH
- 1 TBU[®] High-Speed Protector:
TBU-CA085-500-WH
- 1 GDT: 2020-42T-C4LF
- 2 Telecom Fuses: B1250T

Compliance


GR-1089-CORE

Alternate Recommendations

Variations of this circuit are available depending on specific design constraints; contact your local Bourns technical representative for more information.

Benefit

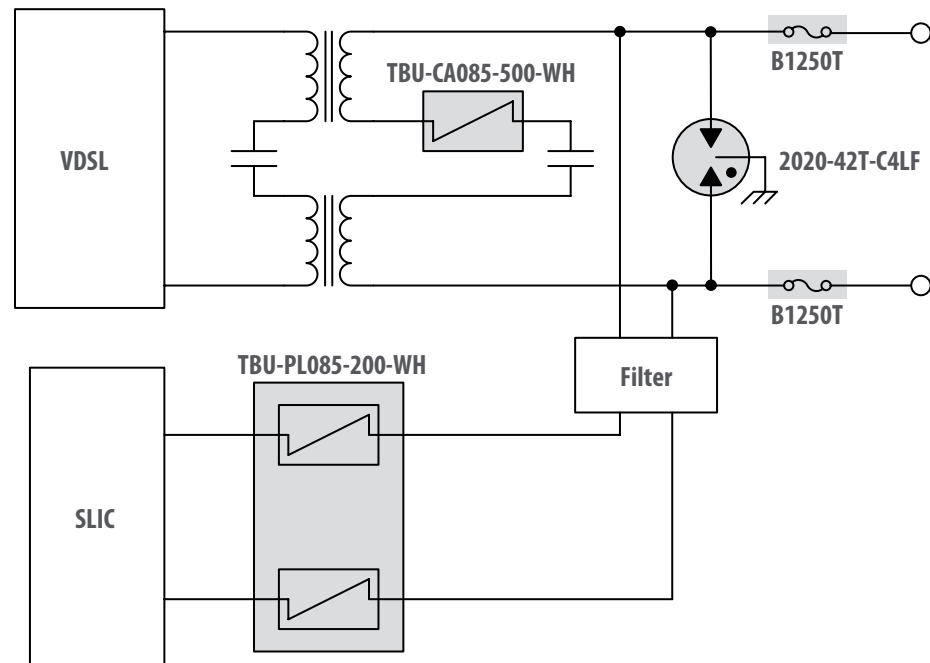This solution provides protection to the voice and data circuits without impairing the VDSL 30 MHz signal.



The schematic above illustrates the application protection and does not constitute the complete circuit design. Customers should verify actual device performance in their specific applications.