

## **AN-1397 LM2852X Demonstration Board**

---

---

---

### **1 Introduction**

This document describes the demonstration board for the LM2852X. The LM2852 is a 2A buck regulator belonging to Texas Instruments Simple Synchronous™ family. The LM2852 input voltage can range from 2.85 V to 5.5 V. Output voltages are factory set from 0.8 V to 3.3 V in 100mV increments. On-chip type-three compensation facilitates simple, low component count power supply design. Two frequency versions of the LM2852 are available: 500 kHz (LM2852Y) and 1500 kHz (LM2852X). The demonstration board for the LM2852X (1500 kHz version) is described in this document. A separate application note describes the LM2852Y. For detailed information regarding component selection, consult the device-specific data sheet.

### **2 $V_{IN}$ , GND and $V_{OUT}$**

Three solder terminals are provided for connections to  $V_{IN}$ , GND and  $V_{OUT}$ . The input voltage to the LM2852 is connected to two PVIN pins and an AVIN pin. PVIN is the supply connected to the output power switches; AVIN powers the controller logic of the regulator. The demonstration board includes filtering of the AVIN voltage using components  $R_F$  and  $C_F$ . The back side plane of the board is connected to ground through the solder terminal via as well as vias underneath the exposed DAP of the LM2852.

### **3 Enable (EN)**

The LM2852 enable pin is internally pulled up through a large resistance. The demonstration board includes a via connected to the EN line to facilitate soldering a jumper wire if application of an enable signal is desired.

### **4 $C_{IN}$ and $C_{INX}$**

The demonstration board provides two capacitor footprints for the input capacitance. The larger footprint holds the bulk of the capacitance, for example 47  $\mu$ F. Additional high frequency filtering may also be accomplished by adding a smaller capacitor –  $C_{INX}$ . A 1  $\mu$ F or 100 nF capacitor is commonly used for high frequency filtering.


### **5 $C_{SS}$**

The soft-start capacitor is used to control the startup behavior of the switching regulator. A 2.7 nF capacitor yields approximately a 3 ms startup time.

### **6 Output Filter - L, and $C_o$**

Since the LM2852 uses on-chip compensation, the output filter component values must be restricted to a certain range. The LM2852X is designed for ceramic output capacitors with ESR values below 10 m $\Omega$ . The recommended inductance and capacitance for standard input and output voltages are 1  $\mu$ H and 10  $\mu$ F.

## 7 Board Schematic

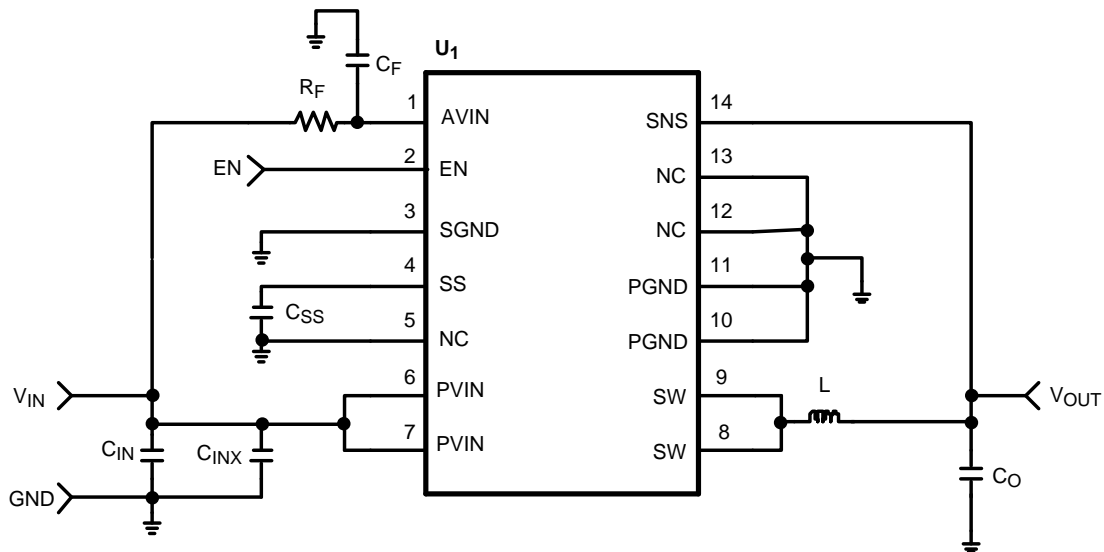

## 8 Bill of Materials (BOM) for 1500 kHz Solution (LM2852X)

**Table 1. Bill of Materials**

ID	Part Number	Type	Size	Parameters	Qty	Vendor
U <sub>1</sub>	LM2852XMXA-x.x	2A Buck	ETSSOP-14		1	NSC
L	DO1608C-102	Inductor		1 $\mu$ H	1	Coilcraft
C <sub>O</sub>	GRM31MR61A106KE19	Capacitor	1206	10 $\mu$ F/X5R/10 V	1	Murata
C <sub>IN</sub>	GRM31CR60J476M	Capacitor	1206	47 $\mu$ F/X5R/6.3 V	1	Murata
C <sub>INX</sub>	GRM188R61A105K	Capacitor	0603	1 $\mu$ F/X5R/10 V	1	Murata
C <sub>SS</sub>	VJ0603Y272KXXA	Capacitor	0603	2.7 nF $\pm$ 10%	1	Vishay-Vitramon
R <sub>F</sub>	CRCW060310R0F	Resistor	0603	10 $\Omega$ $\pm$ 10%	1	Vishay-Dale
C <sub>F</sub>	GRM188R61A105K	Capacitor	0603	1 $\mu$ F/X5R/10 V	1	Murata
	160-1026-02-05-00	Solder Terminals		Terminals for V <sub>IN</sub> , GND and V <sub>OUT</sub>	3	Wearnes

9 PCB Layouts: 835 (mil) X 850 (mil)

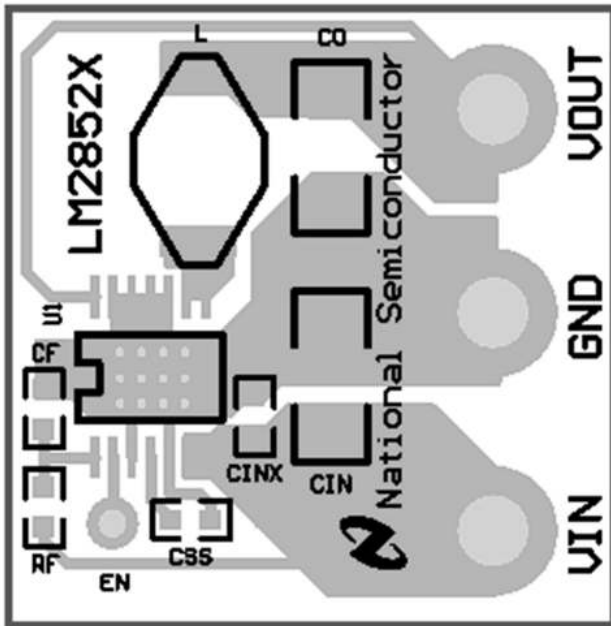


Figure 1. Top Layer

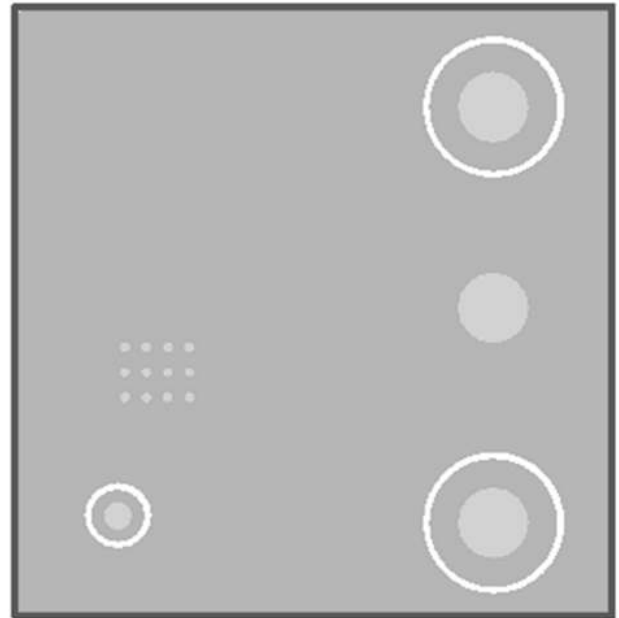


Figure 2. Bottom Layer

10 Efficiency Plot

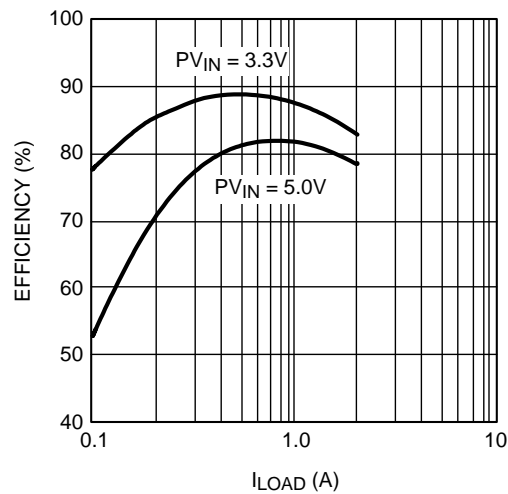


Figure 3. LM2852X Typical Efficiency for 2.5 V Output

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)