

AN-1867 EMIRR Evaluation Boards for LMV831/LMV832/LMV834

1 General Description

To demonstrate the EMI robustness of the LMV831/LMV832/LMV834 and to be able to measure the parameter EMIRR, three evaluation boards have been developed; one for each device. This document describes the evaluation boards and explains how to perform EMIRR measurements. Focus is on one of the input pins as those are most sensitive to EMI. Based on symmetry considerations, it can be expected that both inputs have the same EMIRR. For reasons of simplicity of the required schematic the measurement on the IN+ pin is selected. A detailed description on EMI and EMIRR for the other pins can be found in the *AN-1698 A Specification for EMI Hardened Operational Amplifiers Application Report (SNOA497)*.

To identify EMI robust op amps, a parameter is defined that quantitatively describes the EMI performance. A quantitative measure enables the comparison and the ranking of op amps on their EMI robustness. The definition of the parameter EMIRR is given by:

$$\text{EMIRR}_{V_{\text{RF_PEAK}}} = 20 \log \left(\frac{V_{\text{RF_PEAK}}}{\Delta V_{\text{OS}}} \right)$$

where $V_{\text{RF_PEAK}}$ is the amplitude of the applied unmodulated RF signal (V) and ΔV_{OS} is the resulting input-referred offset voltage shift (V).

2 Op Amp Configuration

To have best defined RF levels on the pin under test, no op amp feedback elements should be in the RF signal path. Therefore, the op amp is connected in an unity-gain configuration. This yields the lowest level of RF filtering due to a feedback network. Schematics and layouts are included in this application report.

3 Applying the RF Signal

Care needs to be taken in applying the RF signal to the pin under test. Signals up to a few GHz will be used, so the whole RF signal path needs to match the characteristic impedance of the RF generator. This requires proper coaxial cabling from the generator to the test board. On the test board a 50Ω stripline needs to be used to bring the RF signal as close as possible to the pin under test. In this case the stripline can be connected directly from the connector to the IN+ pin. A 50Ω termination at the pin under test is also required. For symmetry reasons this is done with two 100Ω resistors in parallel, one on each side of the strip line. Setting up the test environment with a 50Ω resistor close to the LMV831/LMV832/LMV834 ensures that the RF levels at the pin under test are well defined. This 50Ω resistor is also used to set the bias level of the IN+ pin to ground level. The DC measurements are taken at the output of the op amp. Since the op amp is in the unity gain configuration, the input referred offset voltage shift corresponds one-to-one to the measured output voltage shift.

4 Isolating the Other Pins

When the pin under test is tested, the other pins need to be decoupled for RF signals. This ensures that the obtained offset voltage shift is dominantly a result of coupling the RF signal to the pin under test. For this decoupling standard, SMD components can be used.

All trademarks are the property of their respective owners.

5 Layout Considerations

The layout of the evaluation board requires some attention. For decoupling the supply lines, it is suggested that 10 nF capacitors be placed as close as possible to the op amp. For single supply, place a capacitor between V^+ and V^- . For dual supplies, place one capacitor between V^+ and the board ground, and a second capacitor between ground and V^- . On the LMV831 evaluation board, the decoupling of the negative pin V^- is implemented by a capacitor between V^+ and V^- . This is done for easy routing and to keep connections to the pins short. Even with the LMV831/LMV832/LMV834's inherent hardening against EMI, it is still recommended to keep the input traces short and as far as possible from RF sources. Then the RF signals entering the chip are as low as possible, and the remaining EMI can be, almost, completely eliminated in the chip by the EMI reducing features of the LMV831/LMV832/LMV834.

6 Measurement Procedure

The measurement procedure is the same for all test circuits. To measure the input referred offset voltage shift needed for calculating the EMIRR, the following procedure can be used:

1. Measure V_{OUT} when the RF signal is off.
2. Measure V_{OUT} when the RF signal is on.
3. Translate measured V_{OUT} voltages to input referred voltages. Translation is one-to-one in this case since the gain is one in the IN+ test setup.
4. Subtract the two measured input referred voltages.
5. Verify if the offset shift is above the noise level of the op amp setup and the op amp is not saturated. If this is not the case choose another RF level and start the procedure again.
6. Calculate the EMIRR.
7. If needed, transform the results to an EMIRR based on a 100 mV_p RF signal.

7 Measurement Results

To show the sensitivity of the IN+ pin, two types of measurement results are presented using the LMV831 evaluation board:

- The EMIRR as a function of the frequency of the applied signal. The level of the signal is set to the standard level of 100 mV_p (-20 dBV_p).
- The EMIRR as a function of the level of the applied signal. The frequency is set to four typical values: 400 MHz, 900 MHz, 1.8 GHz, and 2.4 GHz.

7.1 EMIRR Vs. Frequency

[Figure 1](#) shows the EMIRR versus frequency for the various temperatures. The measurement is performed with a fixed RF level of -20 dBV_p and a varying RF signal frequency. The frequency range is 10 MHz to 10 GHz.

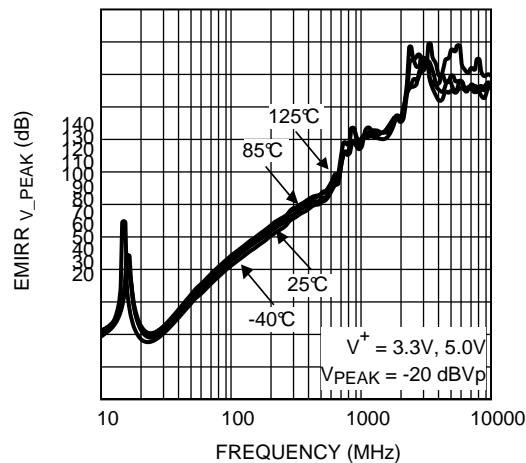


Figure 1. EMIRR vs. Frequency

7.2 EMIRR Vs. Power

Figure 2 shows the EMIRR as a function of power at four typical frequencies.

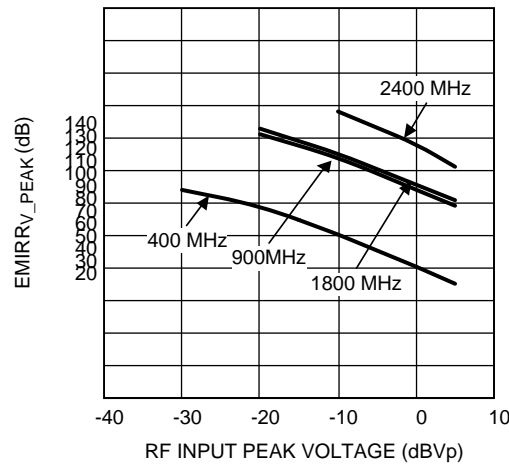


Figure 2. EMIRR vs. Power

In this figure two areas can be distinguished. At the left side of the figure, the EMIRR increases as a function of input level; whereas at the right side the EMIRR decreases as a function of the input level.

The left side of the figure is actually an artifact resulting from the limited accuracy of the measurement setup. For the relatively low input levels, the resulting offset voltage shift is well below the noise level. Thus, when calculating the EMIRR for that region, the ratio of the input level to the noise level is depicted. As the noise level is constant for the setup, an increasing EMIRR is obtained for increasing input signal level.

For the right side, the obtained offset-shift is well above the noise level. As the relation between offset voltage shift and RF input level is quadratic, the ratio as used in the EMIRR is inversely proportional to the RF input level, which is in line with the displayed slope of “-1”.

8 Bill Of Materials

The Bill of Materials (BOM) of the LMV831 evaluation board is given in [Table 1](#).

Table 1. LMV831 Bill Of Materials

Designator	Description	Comment
C1, C3	0603 Capacitor	100 pF
C2	0603 Capacitor	22 pF
C4, C5	Case_B Capacitor	10 μ F
P1	Connector	Banana
P2	Connector	SMA
P3	Connector	BNC
P4	Connector	Banana
P5	Connector	Banana
R1, R2	0603 Resistor	100 Ω
U1	SC70	LMV831

The Bill of Materials (BOM) of the LMV832 evaluation board is given in [Table 2](#).

Table 2. LMV832 Bill Of Materials

Designator	Description	Comment
C1, C2	0603 Capacitor	22 pF
C3, C4	0603 Capacitor	100 pF
C5, C6	Case_B Capacitor	10 μ F
P1, P2	Connector	SMA
P3, P4	Connector	BNC
P5	Connector	Banana
P6	Connector	Banana
P7	Connector	Banana
R1, R2, R3, R4	0603 Resistor	100 Ω
U1	MSOP	LMV832

The Bill of Materials (BOM) of the LMV834 evaluation board is given in [Table 3](#).

Table 3. LMV834 Bill Of Materials

Designator	Description	Comment
C1, C3	0603 Capacitor	100 pF
C2, C4	Case_B Capacitor	10 μ F
C5, C6, C7, C8	0603 Capacitor	22 pF
P1	Connector	Banana
P2	Connector	Banana
P3	Connector	Banana
P4, P5, P6, P7	Connector	SMA
P8, P9, P10, P11	Connector	BNC
R1, R2, R3, R4, R5, R6, R7, R8	0603 Resistor	100 Ω
U1	TSSOP	LMV834

9 LMV831 Evaluation Board

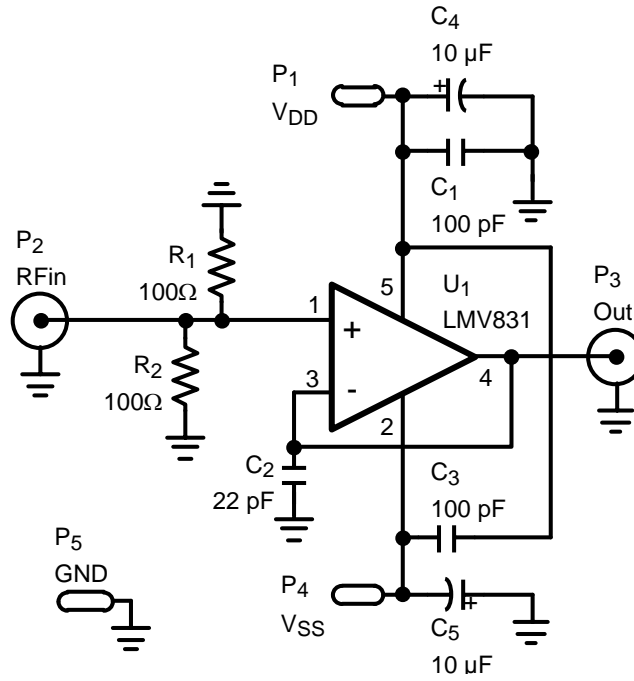


Figure 3. Schematic for LMV831, Coupling RF Signal to the IN+ Pin

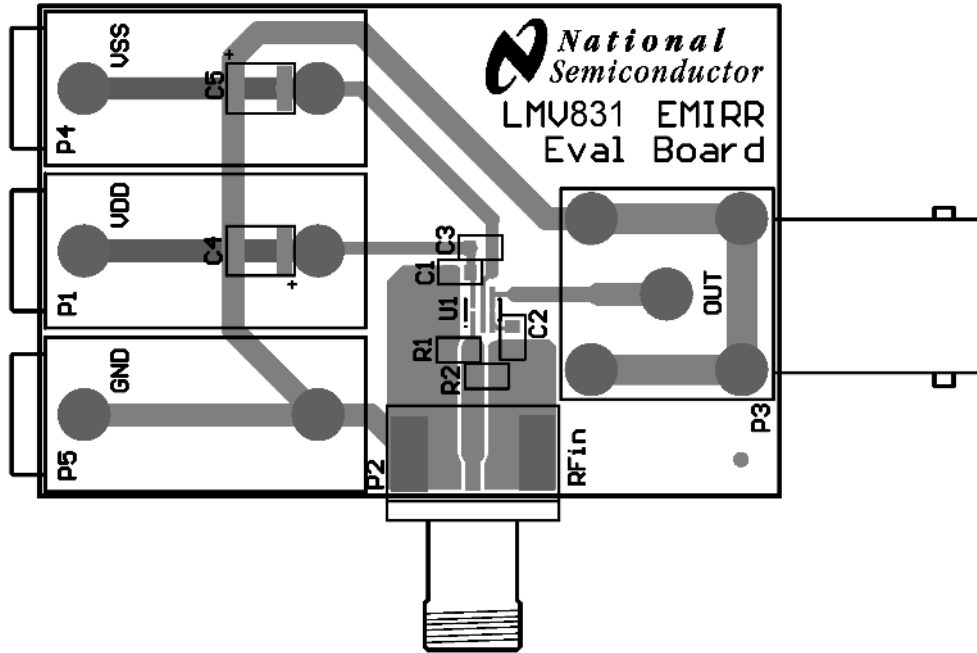


Figure 4. Layout for LMV831, All Layers

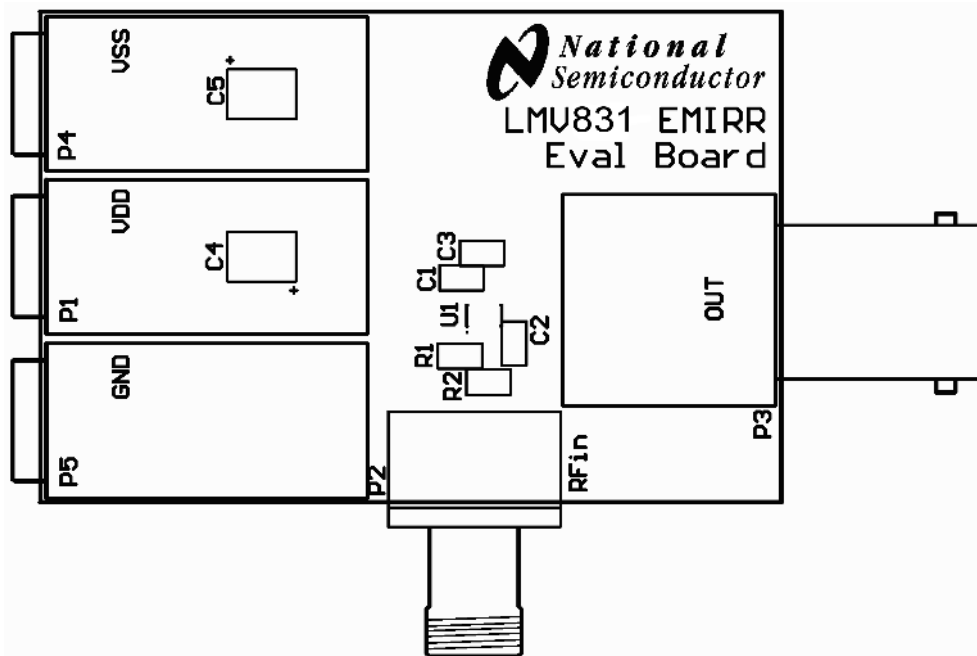


Figure 5. Layout for LMV831, Silk Screen

10 LMV832 Evaluation Board

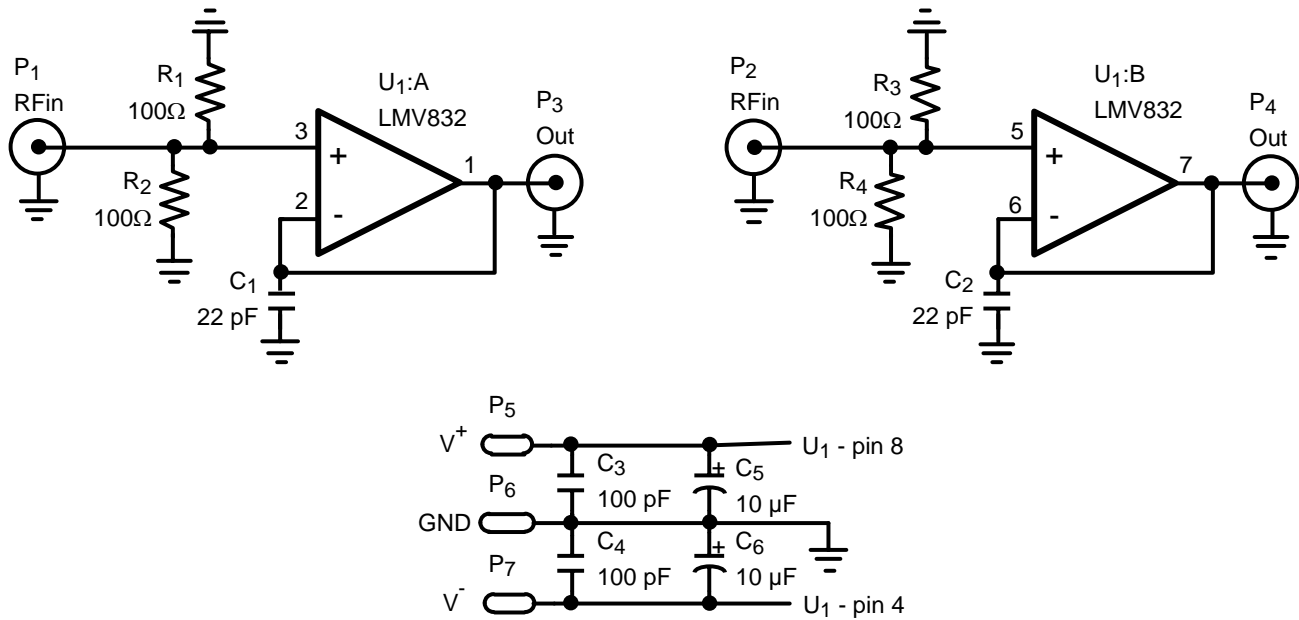


Figure 6. Schematic for LMV832, Coupling RF Signal to the IN+ Pin

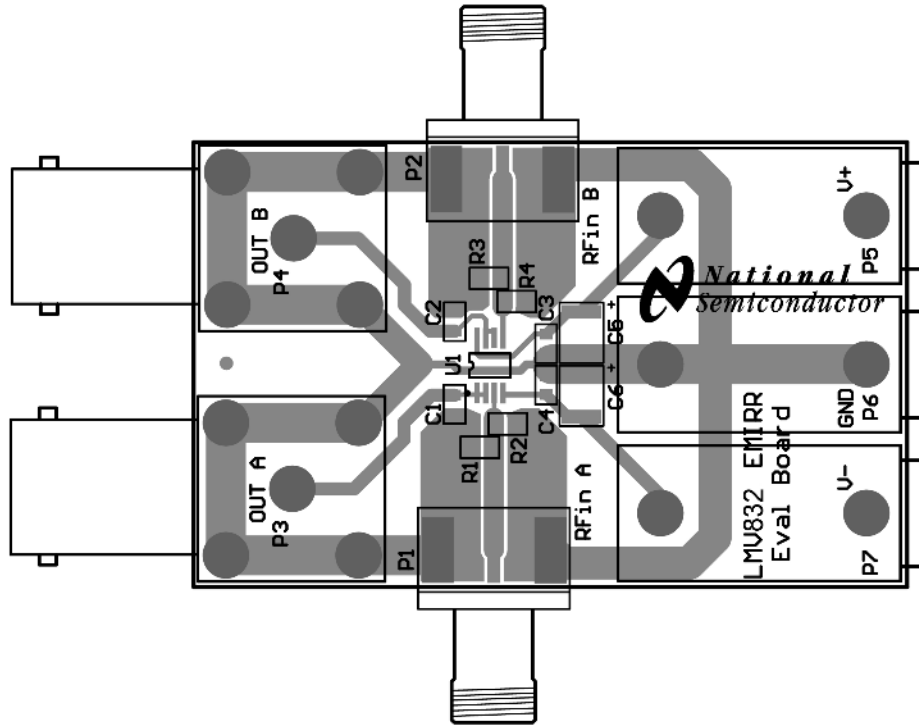


Figure 7. Layout for LMV832, All Layers

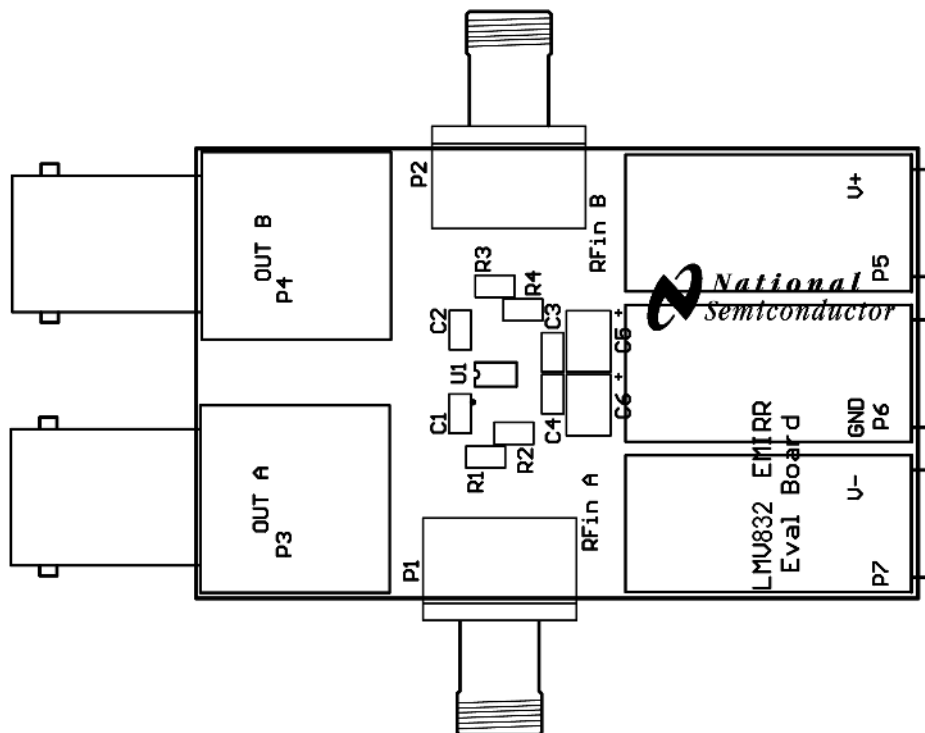


Figure 8. Layout for LMV832, Silk Screen

11 LMV834 Evaluation Board

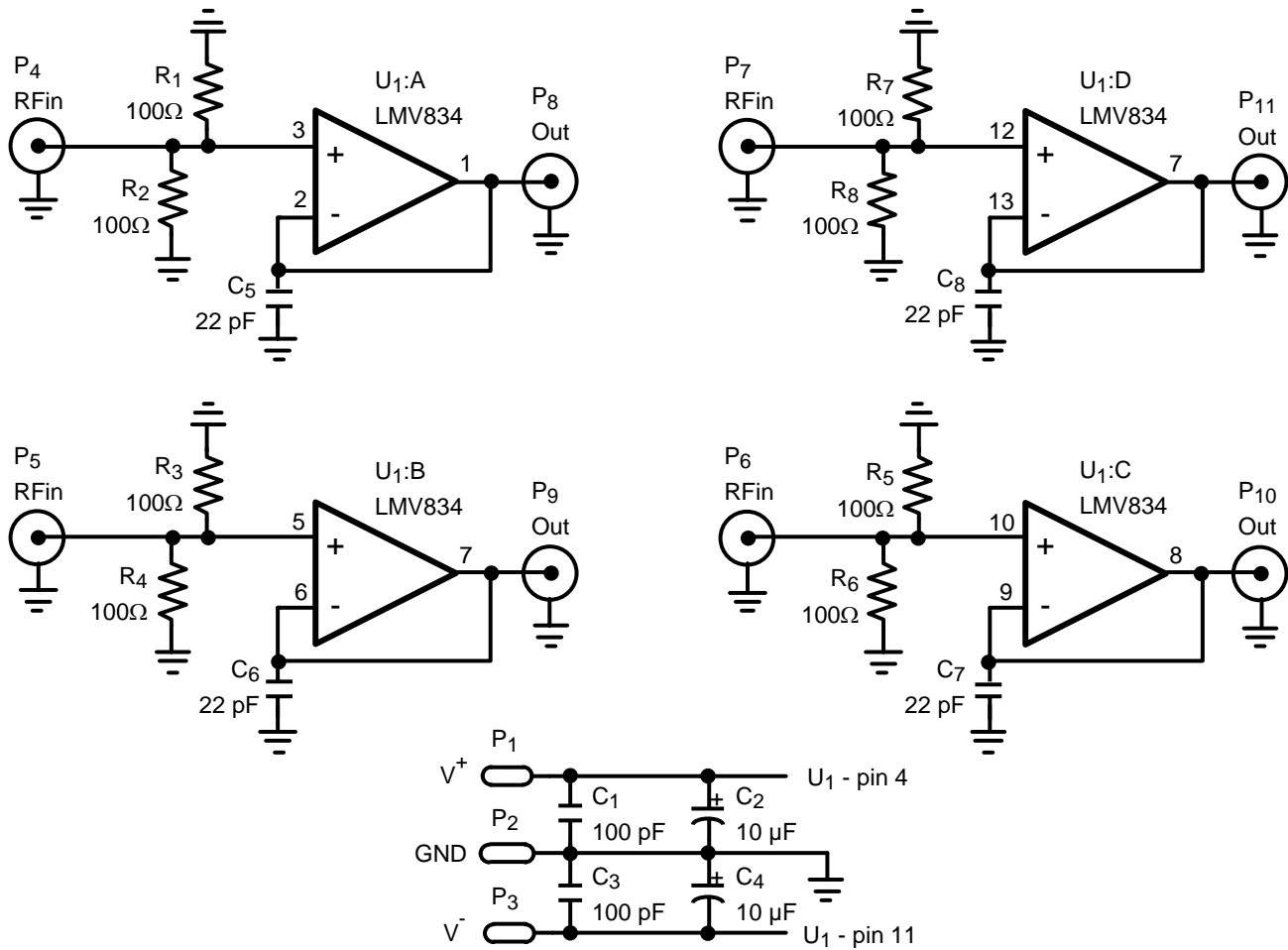


Figure 9. Schematic for LMV834, Coupling RF Signal to the IN+ Pin

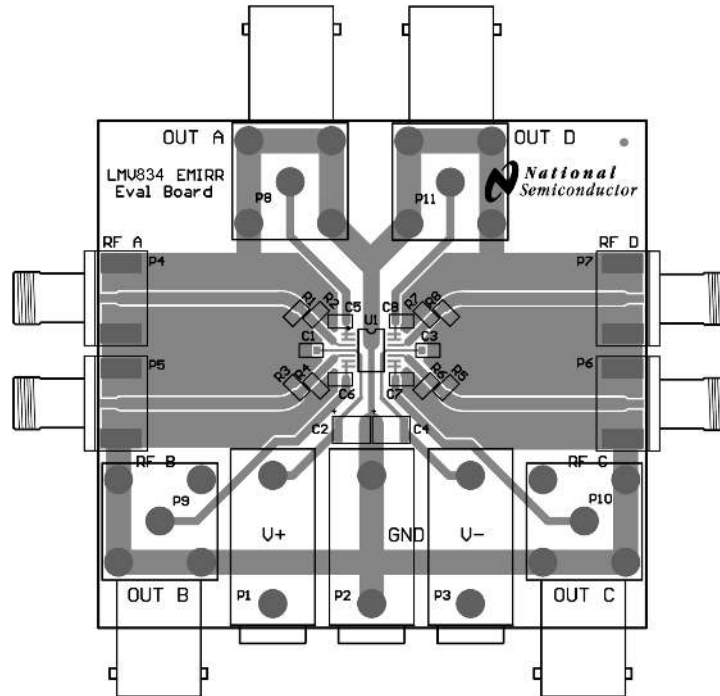


Figure 10. Layout for LMV834, All Layers

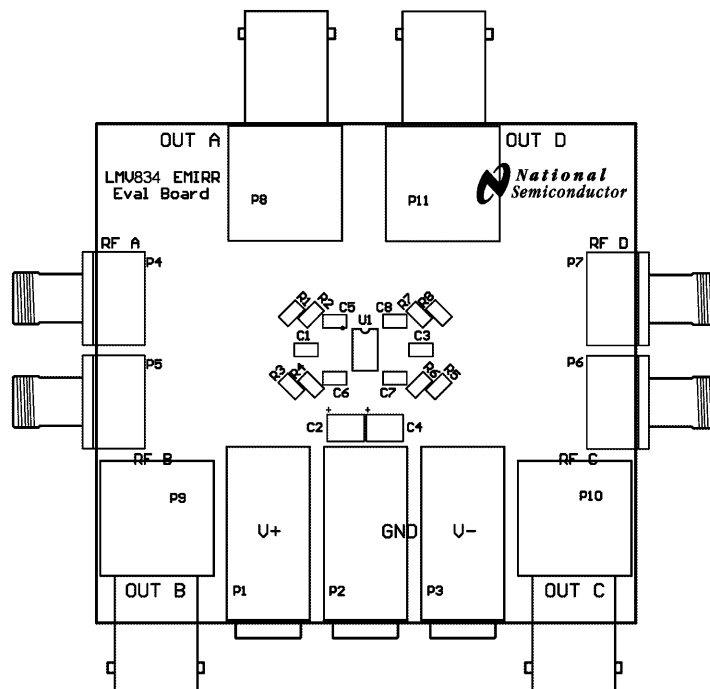


Figure 11. Layout for LMV834, Silk Screen

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com