

Reference design: wide range 200W L6599-based HB LLC resonant converter for LCD TV & flat panels

Introduction

This note describes the performances of a 200 W reference board, with wide-range mains operation and power-factor-correction (PFC). Its electrical specification is tailored to a typical high-end application for LCD TV or monitor applications.

The main features of this design are the very low no-load input consumption (<0.5 W) and the very high global efficiency, better than 87% at full load and nominal mains voltage (115 - 230 V_{ac}).

The circuit consists of three main blocks; the first is a front-end PFC pre-regulator based on the L6563 PFC controller. The second stage is a multi-resonant half-bridge converter whose control is implemented through the STMicroelectronics L6599 resonant controller. A further auxiliary flyback converter based on the VIPer12A-E off-line primary switcher completes the architecture. This third block is mainly intended for microprocessor supply and display power management operations.

Figure 1. L6599 and L6563 200W evaluation board (EVAL6599-200W)



Contents

- 1 Main characteristics and circuit description 4**
- 2 Electrical test results 9**
 - 2.1 Efficiency measurements 9
 - 2.2 Resonant stage operating waveforms 11
 - 2.3 Stand-by and no load power consumption 14
 - 2.4 Short-circuit protection 15
 - 2.5 Overvoltage protection 16
- 3 Thermal tests 17**
- 4 Conducted emission pre-compliance test 20**
- 5 Bill of materials 21**
- 6 PFC coil specification 26**
 - 6.1 Electrical characteristics 26
 - 6.2 Mechanical aspect and pin numbering 27
- 7 Resonant power transformer specification 27**
 - 7.1 Electrical characteristics and mechanical aspect 28
- 8 Auxiliary flyback power transformer 30**
 - 8.1 Electrical characteristics 30
- 9 Reference design board layout 32**
- 10 Revision history 34**

List of figures

| | | |
|------------|--|----|
| Figure 1. | L6599 and L6563 200W evaluation board (EVAL6599-200W)..... | 1 |
| Figure 2. | PFC pre-regulator electrical diagram | 6 |
| Figure 3. | Resonant converter electrical diagram | 7 |
| Figure 4. | Auxiliary converter electrical diagram | 8 |
| Figure 5. | Overall efficiency versus output power at nominal mains voltages. | 10 |
| Figure 6. | Overall efficiency versus output power at several input voltage values | 11 |
| Figure 7. | Resonant circuit primary side waveforms at full load | 12 |
| Figure 8. | Resonant circuit primary side waveforms at no-load condition. | 12 |
| Figure 9. | Resonant circuit secondary side waveforms: +24 V output | 13 |
| Figure 10. | Resonant circuit secondary side waveforms: +12 V output | 13 |
| Figure 11. | Low frequency (100 Hz) ripple voltage on the output voltages. | 13 |
| Figure 12. | Load transition (0 - 100%) on +24 V output voltage | 14 |
| Figure 13. | Load transition (0 - 100%) on +12 V output voltage | 14 |
| Figure 14. | +24 V output short-circuit waveforms | 16 |
| Figure 15. | +12 V output short-circuit waveforms | 16 |
| Figure 16. | Thermal map @115 V _{ac} - full load | 17 |
| Figure 17. | Thermal map at 230 V _{ac} - full load | 17 |
| Figure 18. | CE quasi peak measurement at 115 V _{ac} and full load | 20 |
| Figure 19. | CE quasi peak measurement at 230 V _{ac} and full load | 20 |
| Figure 20. | PFC coil electrical diagram | 26 |
| Figure 21. | PFC coil pin side view. | 27 |
| Figure 22. | Mechanical aspect and pin numbering of resonant transformer. | 28 |
| Figure 23. | Resonant transformer electrical diagram | 29 |
| Figure 24. | Resonant transformer winding position on coil former | 29 |
| Figure 25. | Auxiliary transformer electrical diagram | 30 |
| Figure 26. | Auxiliary transformer winding position on coil former | 31 |
| Figure 27. | Copper tracks | 32 |
| Figure 28. | Thru-hole component placing and top silk screen | 33 |
| Figure 29. | SMT component placing and bottom silk screen | 33 |

1 Main characteristics and circuit description

The main characteristics of the SMPS are listed below:

- Universal input mains range: 90 to 264 V_{ac} and frequencies between 45 and 65 Hz
- Output voltages:
 - 24 V@6 A continuous operation
 - 12 V@ 5 A continuous operation
 - 3.3 V@ 0.7 A continuous operation
 - 5 V@ 1 A continuous operation
- Mains harmonics: Compliance with EN61000-3-2 specifications
- St-by mains consumption: Typical 0.5 W @230 V_{ac}
- Overall efficiency: better than 88% at full load
- EMI: Compliance with EN55022-class B specifications
- Safety: Compliance with EN60950 specifications
- PCB single layer: 132x265 mm, mixed PTH/SMT technologies

The circuit consists of three stages. A front-end PFC pre-regulator implemented by the controller L6563 ([Figure 2](#)), a half-bridge resonant DC/DC converter based on the resonant controller L6599 ([Figure 3](#)) and a 7 W flyback converter intended for stand-by management ([Figure 4](#)) utilizing the VIPer12A-E off-line primary switcher.

The PFC stage delivers a stable 400 V_{DC} supply and provides for the reduction of the mains harmonics, in order to meet the requirements of the European norm EN61000-3-2 and the JEIDA-MITI norm for Japan.

The PFC controller is the L6563 (U1), working in FOT (fixed off-time) mode and integrating all functions needed to operate the PFC and interface the downstream resonant converter.

Note: The FOT control is implemented through components C15, C17, D5, Q3, R14, R17 and R29 (see AN1792 for a complete description of a FOT PFC pre-regulator).

The power stage of the PFC is a conventional boost converter, connected to the output of the rectifier bridge through a differential mode filtering cell (C5, C6 and L3) for EMI reduction. It includes a coil (L4), diode (D3) and two capacitors (C7 and C8).

The boost switch is represented by the Power MOSFET (Q2) which is directly driven by the L6563 output drive thanks to the high current capability of the IC.

The divider (R30, R31 and R32) provides the L6563 (MULT Pin 3) with the information of the instantaneous voltage that is used to modulate the boost current and to derive some further information like the average value of the AC line used by the V_{FF} (voltage feed-forward) function. This function is used to keep the output voltage almost independent of the mains one.

The first divider (R3, R6, R8, R10 and R11) is dedicated to detecting the output voltage while the second divider (R5, R7, R9, R16 and R25) is used to protect the circuit in case of voltage loop fail.

The second stage is an LLC resonant converter, with half bridge topology, working in ZVS (zero voltage switching) mode.

The controller is the L6599 integrated circuit that incorporates the necessary functions to drive properly the two half-bridge MOSFETs by a 50 percent fixed duty cycle with dead-time,

changing the frequency according to the feedback signal in order to regulate the output voltages against load and input voltage variations.

The main features of the L6599 are a non-linear soft-start, a current protection mode used to program the hiccup mode timing, a dedicated pin for sequencing or brown-out (LINE) and a stand-by pin (STBY) for burst mode operation at light loads (not used in this design).

The transformer uses the magnetic integration approach, incorporating the resonant series and shunt inductances. Thus, no additional external coils are needed for the resonance. The transformer configuration chosen for the secondary winding is center-tap, and the output rectifiers are Schottky type diodes, in order to limit the power dissipation. The feedback loop is implemented by means of a classical configuration using a TL431 (U4) to adjust the current in the optocoupler diode (U3). A weighted resistive divider (R53, R57, R58, R60 and R61) is used to detect both output voltages in order to get a better overall voltage regulation. The optocoupler transistor modulates the current from Pin 4, so the frequency will change accordingly, thus achieving the output voltage regulation. Resistors R46 and R54 set the maximum operating frequency.

In case of a short circuit, the current entering the primary winding is detected by the lossless circuit (C34, C39, D11, D12, R43, and R45) and the resulting signal is fed into Pin 6.

In case of overload, the voltage on Pin 6 will overpass an internal threshold that triggers a protection sequence via Pin 2, keeping the current flowing in the circuit at a safe level.

The third stage is a small flyback converter based on the VIPer12A-E, a current mode controller with integrated Power MOSFET, capable of delivering (approximately) 7 W output power on the output voltages (5 V and 3.3 V). The regulated output voltage is the 3.3 V output and, also in this case, the feedback loop bases on the TL431 (U7) and optocoupler (U6) to control the output voltage.

This converter is able to operate in the whole mains voltage range, even when the PFC stage is not working. From the auxiliary winding on the primary side of the flyback transformer (T2), a voltage V_s is available, intended to supply the other controllers (L6563 and L6599) in addition to the VIPer12A-E itself.

The PFC stage and the resonant converter can be switched on and off through the circuit based mainly on components Q7, Q8, D22 and U8, which, depending on the level of the signal ST-BY, supplies or removes the auxiliary voltage (V_{AUX}) necessary to start-up the controllers of the PFC and resonant stages. In this way, when the AC input voltage is applied to the power supply, the small flyback converter switches on first; then, when the ST-BY signal is low, the PFC pre-regulator becomes operative, and last the resonant converter can deliver the output power to the load.

Note that if Pin 9 of Connector J3 is left floating (no signal ST-BY present), the PFC and resonant converter will be not operating, and only +5V and +3.3V supplies are available on the output. In order to enable the +24 V and +12 V outputs, Pin 9 of Connector J3 must be pulled down to ground.

Figure 2. PFC pre-regulator electrical diagram

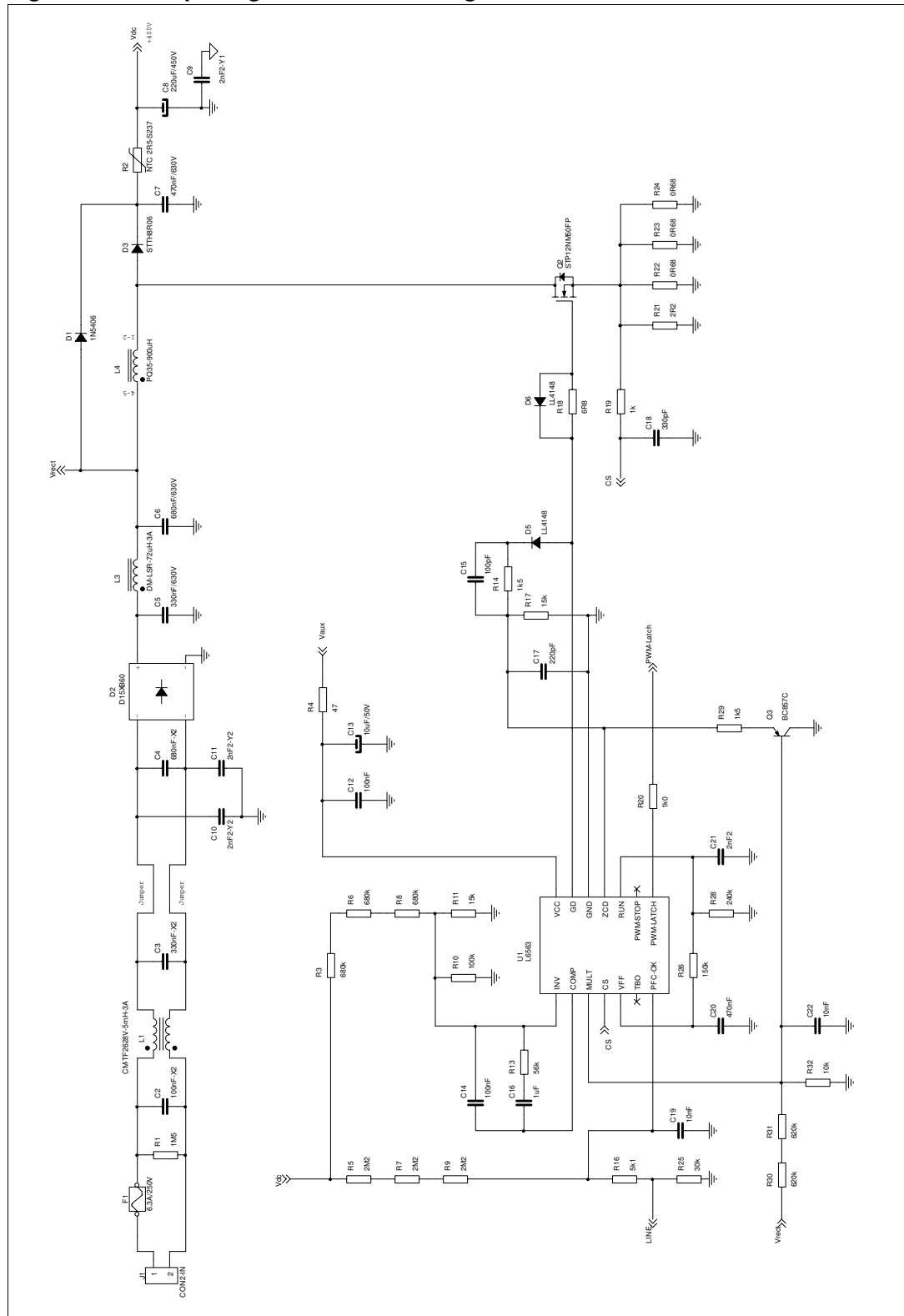


Figure 3. Resonant converter electrical diagram


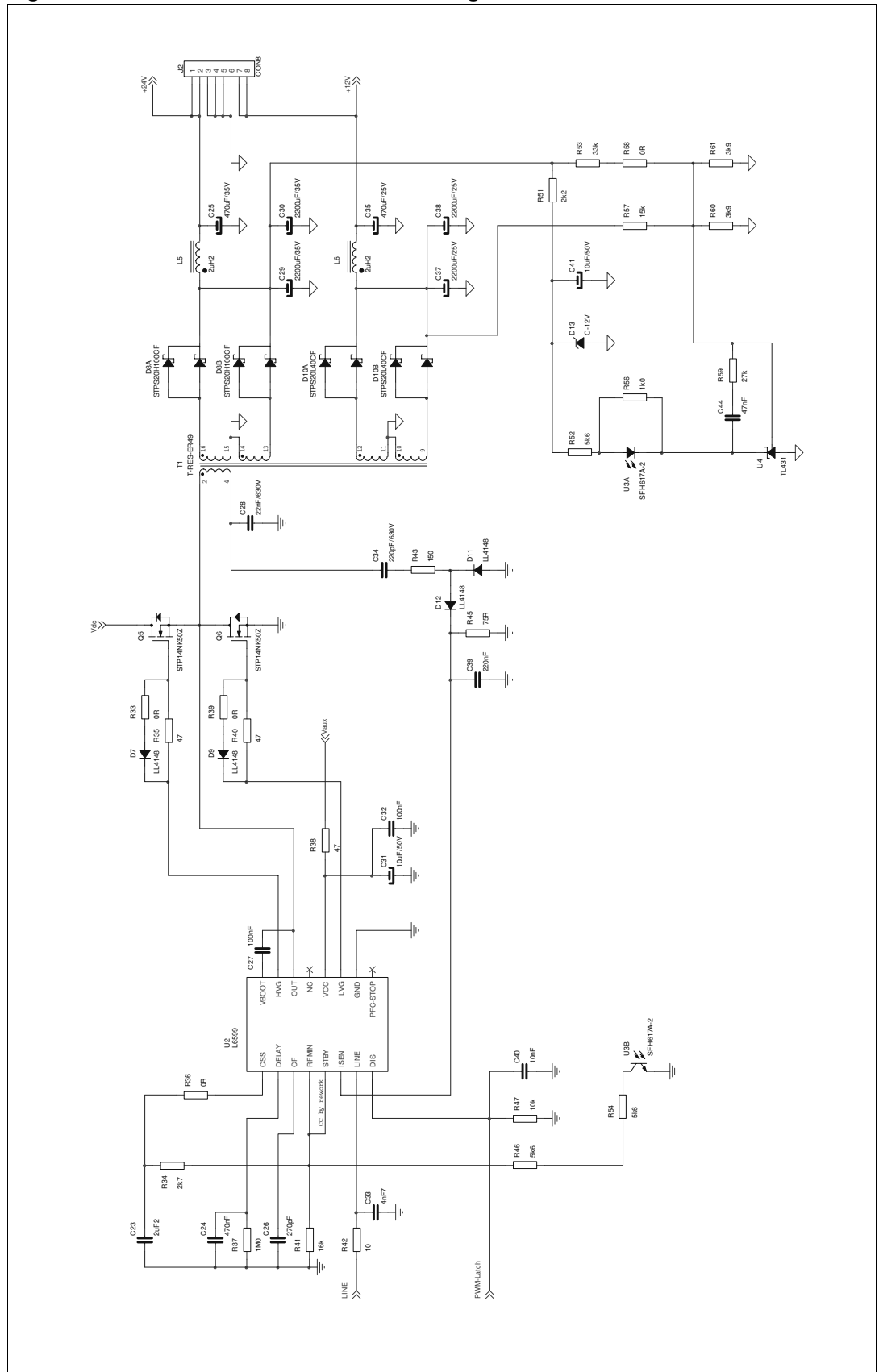


Figure 4. Auxiliary converter electrical diagram

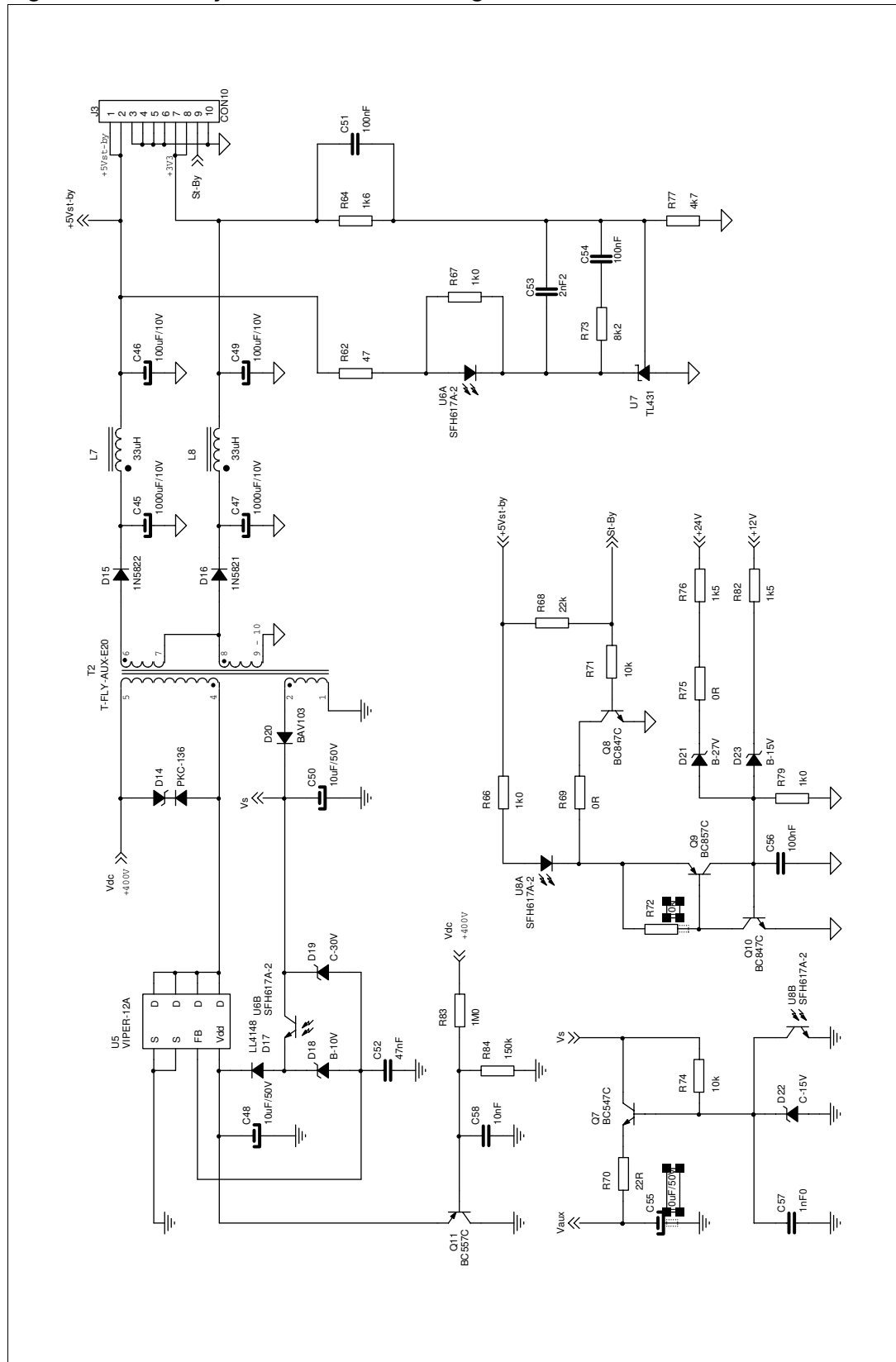

2 Electrical test results

2.1 Efficiency measurements

[Table 1](#) and [Table 2](#) show the output voltage measurements at the nominal mains voltages of 115 V_{ac} and 230 V_{ac}, with different load conditions. For all measurements, both at full load and at light load operation, the input power is measured using a Yokogawa WT-210 digital power meter.

Particular attention has to be paid when measuring input power at full load in order to avoid measurement errors due to the voltage drop on cables and connections. Therefore please connect the WT210 voltmeter termination to the board input connector. For the same reason please measure the output voltage at the output connector or use the remote sense option of your active load for a correct output voltage measurement.

Table 1. Efficiency measurements @V_{IN} = 115 V_{ac}

| +24 V(V) @load(A) | +12 V(V) @load(A) | +5 V(V) @load(A) | +3.3 V(V) @load(A) | P _{OUT} (W) | P _{IN} (W) | Efficiency |
|-------------------|-------------------|------------------|--------------------|----------------------|---------------------|------------|
| 23.81 - 6.00 | 11.86 - 4.94 | 4.93 - 0.98 | 3.35 - 0.71 | 208.66 | 235.00 | 88.79% |
| 24.04 - 3.04 | 11.80 - 4.91 | 4.93 - 0.98 | 3.35 - 0.71 | 138.23 | 155.50 | 88.89% |
| 23.84 - 3.02 | 11.91 - 1.98 | 4.93 - 0.98 | 3.35 - 0.71 | 102.79 | 115.47 | 89.02% |
| 23.79 - 2.01 | 11.96 - 0.49 | 4.96 - 0.31 | 3.35 - 0.31 | 56.25 | 63.55 | 88.52% |
| 23.94 - 0.53 | 11.92 - 0.49 | 4.97 - 0.31 | 3.35 - 0.31 | 21.11 | 25.56 | 82.58% |

Table 2. Efficiency measurements @V_{IN} = 230 V_{ac}

| +24 V(V) @load(A) | +12 V(V) @load(A) | +5 V(V) @load(A) | +3.3 V(V) @load(A) | P _{OUT} (W) | P _{IN} (W) | Efficiency |
|-------------------|-------------------|------------------|--------------------|----------------------|---------------------|------------|
| 23.82 - 6.00 | 11.86 - 4.94 | 4.94 - 0.98 | 3.35 - 0.71 | 208.73 | 229.96 | 90.77% |
| 24.05 - 3.04 | 11.80 - 4.91 | 4.94 - 0.98 | 3.35 - 0.71 | 138.27 | 152.85 | 90.46% |
| 23.85 - 3.02 | 11.91 - 1.98 | 4.94 - 0.98 | 3.35 - 0.71 | 102.83 | 114.05 | 90.16% |
| 23.80 - 2.01 | 11.96 - 0.49 | 4.96 - 0.31 | 3.35 - 0.31 | 56.27 | 63.47 | 88.66% |
| 23.94 - 0.53 | 11.92 - 0.49 | 4.96 - 0.31 | 3.35 - 0.31 | 21.11 | 26.47 | 79.73% |

In [Table 1](#), [Table 2](#) and [Figure 5](#) the overall circuit efficiency is measured at each load condition, at both nominal input mains voltages of 115 V_{ac} and 230 V_{ac}. The values were measured after 30 minutes of warm-up at maximum load. The high efficiency of the PFC pre-regulator working in FOT mode and the very high efficiency of the resonant stage working in ZVS (i.e. with negligible switching losses), provides for an overall efficiency better than 88%. This is a significant high value for a two-stage converter with two output voltages delivering an output current in excess of 5 amps, especially at low input mains voltage where the PFC conduction losses increase. Even at lower loads, the efficiency still remains high.

The global efficiency at full load has been measured even at the limits of the input voltage range, with good results:

- At V_{IN} = 90 V_{ac} - full load, the efficiency is 86.88% (P_{OUT} = 208.8 W and P_{IN} = 240.3 W)
- At V_{IN} = 264 V_{ac} - full load, the efficiency is 90.90% (P_{OUT} = 208.7 W and P_{IN} = 229.6 W)

Also at light load, at an output power of about 10% of the maximum level, the overall efficiency is very good, reaching a value better than 79% over the entire input mains voltage range.

Figure 6 shows the efficiency measured at various input voltages versus output power.

Figure 5. Overall efficiency versus output power at nominal mains voltages


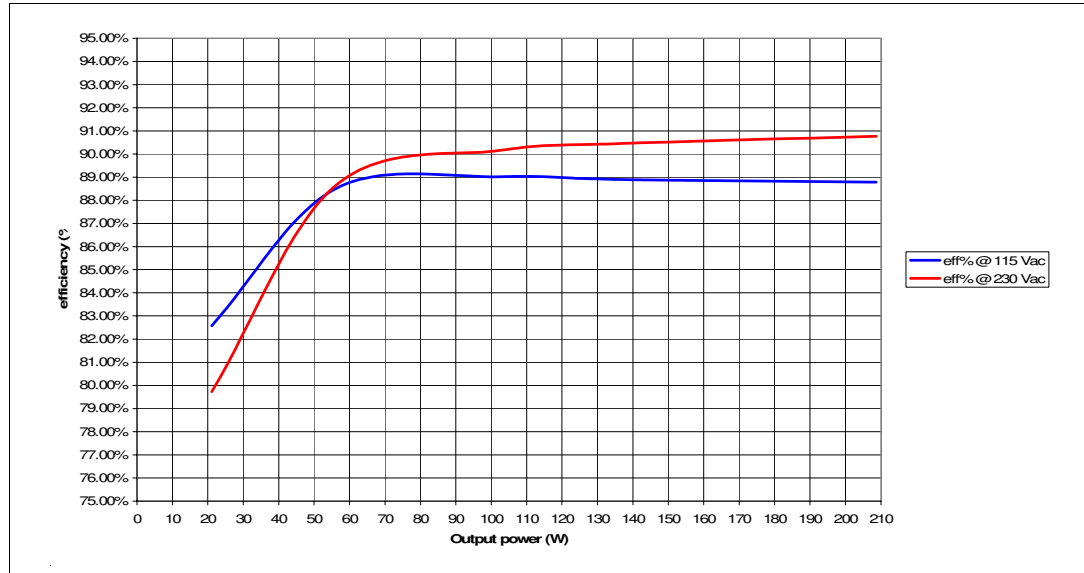


Figure 6. Overall efficiency versus output power at several input voltage values

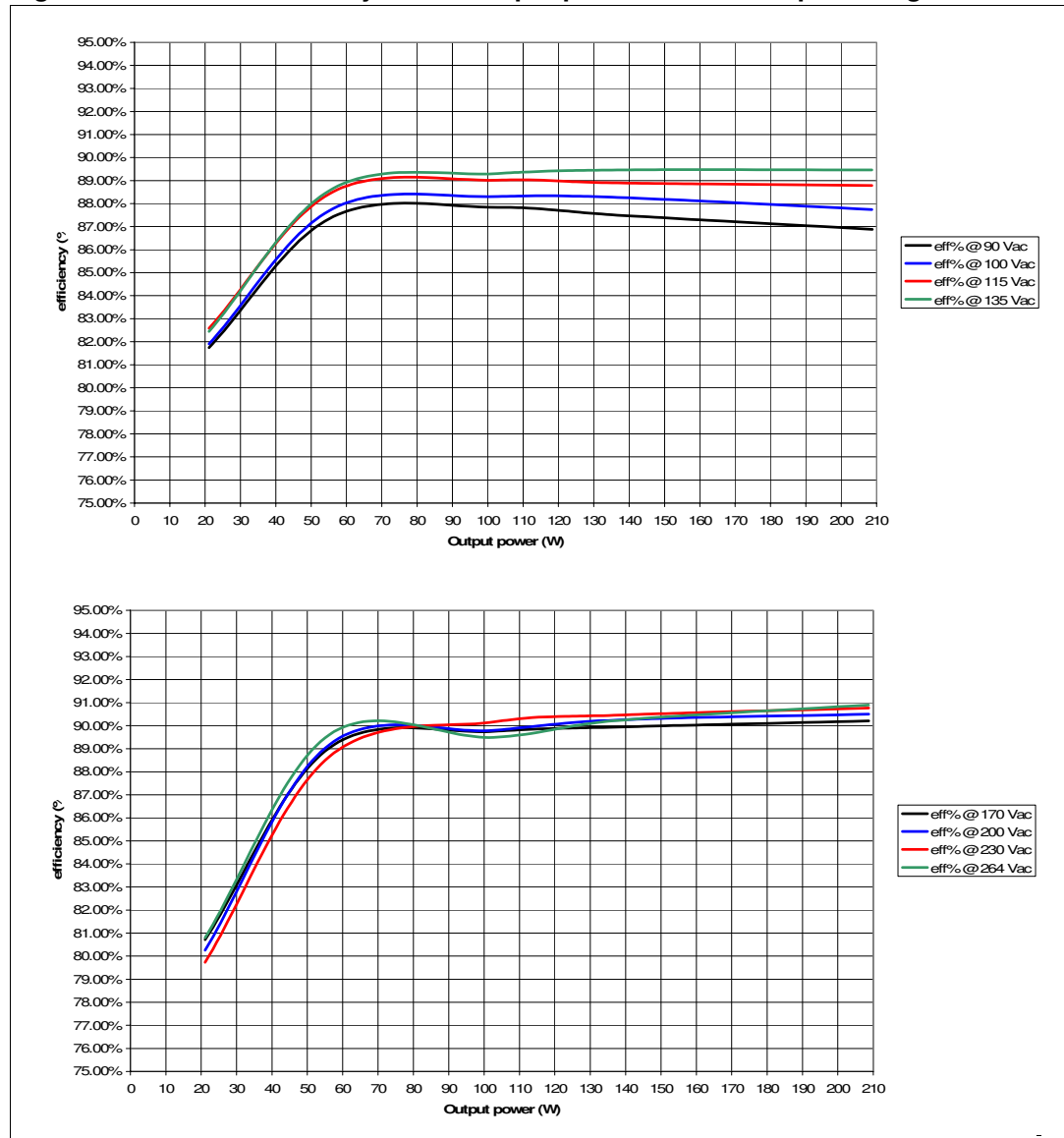

2.2 Resonant stage operating waveforms

Figure 7 shows some waveforms during steady state operation of the resonant circuit at full load. The Ch3 waveform is the half-bridge square voltage on Pin 14 of L6599, driving the resonant circuit. In the picture it is not evident, but the switching frequency is normally slightly modulated following the PFC pre-regulator 100-Hz ripple that is rejected by the resonant control circuitry. The switching frequency has been selected approximately at 95-kHz in order to have a good trade off between transformer losses and dimensions.

The Ch4 waveform represents the transformer primary current flowing into the resonant tank. As shown, it is almost sinusoidal because the operating frequency is close to the resonance of the leakage inductance of the transformer and the resonant capacitor (C28). In this condition, the circuit has a good margin for ZVS operation, providing good efficiency,

while the almost sinusoidal current waveform just allows for an extremely low EMI generation.

Figure 8 shows the same waveforms of previous figure, when both the outputs are not loaded. This picture demonstrates the ability of the converter to operate down to zero load, with the output voltages still within regulation. The resonant tank current has obviously a triangular shape and represents the magnetizing current flowing into the transformer primary side.

Figure 7. Resonant circuit primary side waveforms at full load


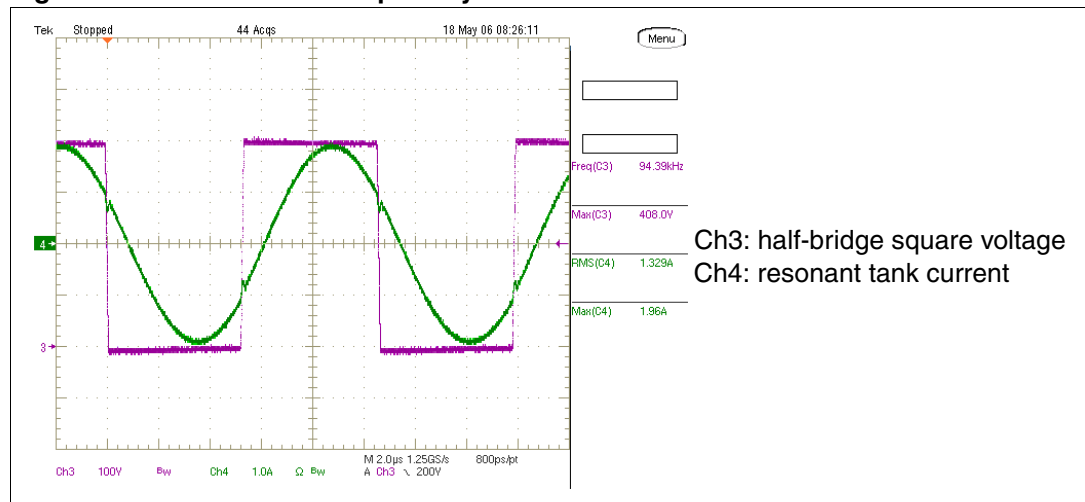


Figure 8. Resonant circuit primary side waveforms at no-load condition

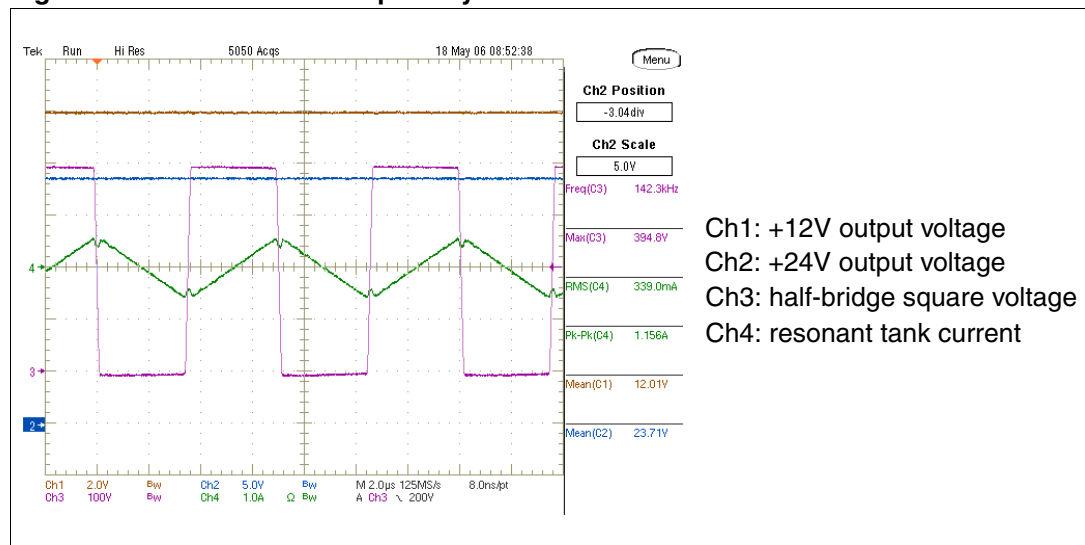


In Figure 9 and Figure 10, waveforms relevant to the secondary side are represented: the rectifiers reverse voltage is measured by CH1 (for both +24 V and +12 V outputs) and the peak to peak value is indicated on the right side of the figure. It is a bit higher than the theoretical value that would be $2(V_{OUT}+V_F)$: it is possible to observe a small ringing on the bottom side of the waveform, responsible for this difference.

Waveform CH3 shows the current flowing into one of the two output diodes for each output voltage (respectively D8A and D10A). Also this current shape is almost a sine wave, whose average value is one half the output current.


The ripple and noise on the output voltage is shown on CH2. Thanks to the advantages of the resonant converter, the high frequency noise of the output voltages is less than 50 mV, while the residual ripple at twice the mains frequency is lower than 75 mV at maximum load and any line condition, as shown in *Figure 11*.

Figure 9. Resonant circuit secondary side waveforms: +24 V output

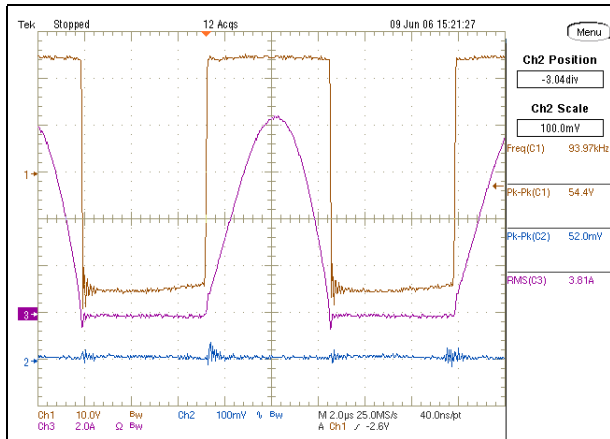


+24 V output waveforms:
 Ch1: +24 V diode reverse voltage
 Ch2: high freq. ripple on +24 V output voltage
 Ch3: diode D8A current

Figure 10. Resonant circuit secondary side waveforms: +12 V output

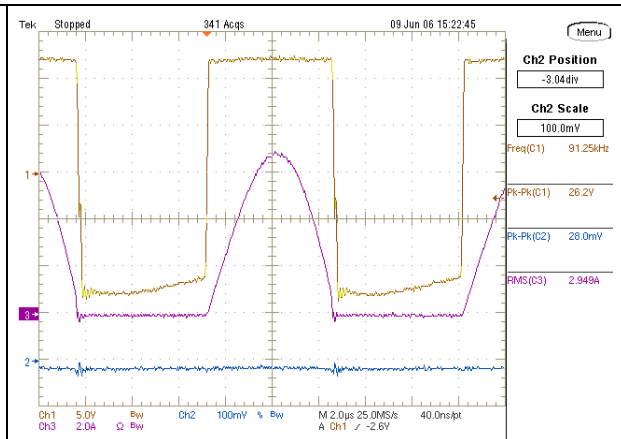

+12 V output waveforms:
 Ch1: +12V diode reverse voltage
 Ch2: high freq. ripple on +12 V output voltage
 Ch3: diode D10A current

Figure 11. Low frequency (100 Hz) ripple voltage on the output voltages

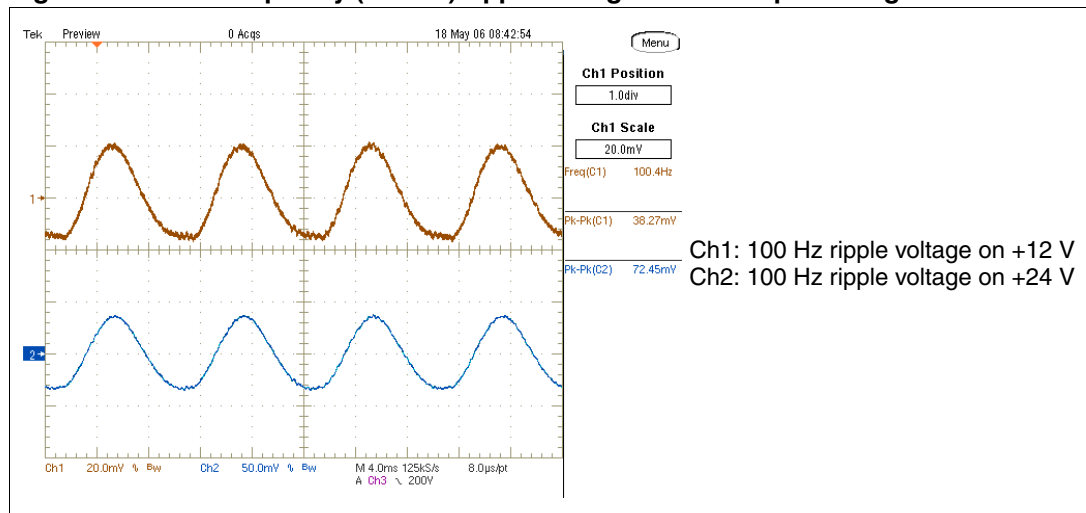


Ch1: 100 Hz ripple voltage on +12 V
 Ch2: 100 Hz ripple voltage on +24 V

Figure 12 shows the dynamic behavior of the converter during a load variation from 0 to 100% on one output, with the other output at maximum load. This figure also highlights the induced effect of this load change on the PFC pre-regulator output voltage (+400 V on Ch3 track). Both the transitions (from 0 to 100% and from 100% to 0) are clean and do not show any problem for the output voltage regulation.

Thus, it is clear that the proposed architecture is really suitable for power supplies operating with strong load variation without any problem related to the load regulation.

Figure 12. Load transition (0 - 100%) on +24 V output voltage **Figure 13. Load transition (0 - 100%) on +12 V output voltage**

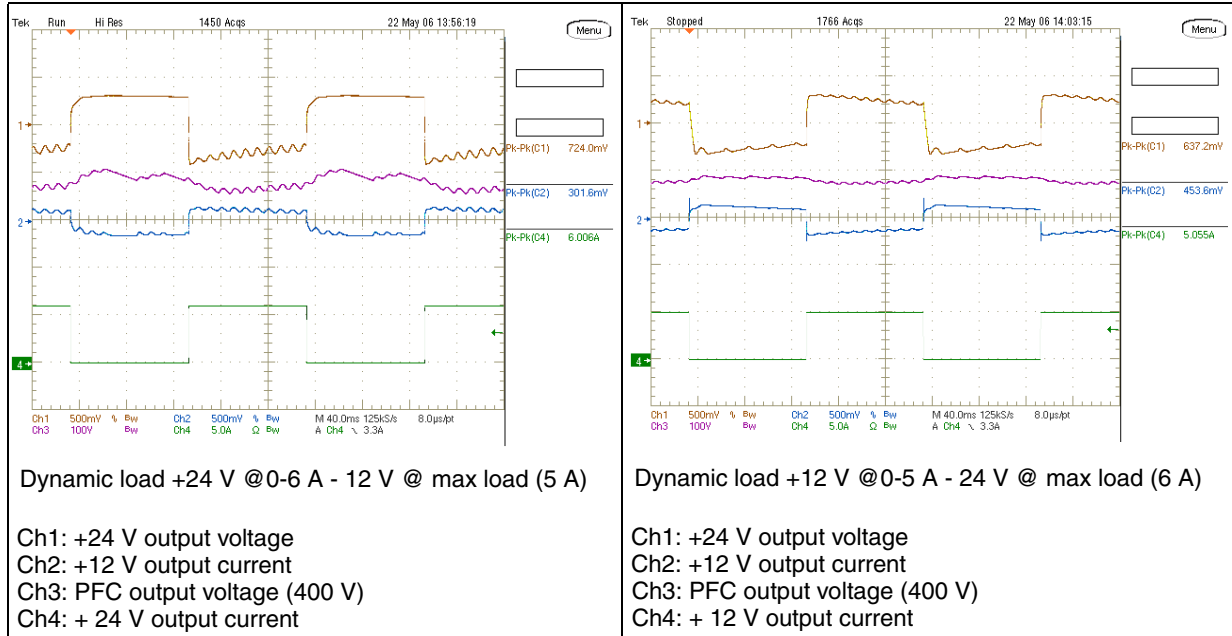

2.3 Stand-by and no load power consumption

The board is specifically designed for light load and zero load operation, as during Stand-by or Power-off operation, when no power is requested from the +24 V and +12 V outputs.

Though the resonant converter can operate down to zero load, some tricks are required to keep very low the input power drawn from the mains when the system is in this load condition. Thus, when entering this power management mode, the ST-BY signal needs to be set high (by the microcontroller of the system). This forces the PFC pre-regulator and the resonant stage to switch off (because the supply voltage of the two control ICs is no longer present (Figure 4) and only the auxiliary flyback converter continues working just to supply the microprocessor circuitry.

Table 3 and Table 4 show the measurements of the input power in several light load conditions at 115 and 230 V_{ac}.

These tables show that at no load the input power is lower than 0.5 W.

Table 3. Stand-by consumption at $V_{IN} = 115 V_{ac}$

| +5 V(V) @load(A) | +3.3 V(V) @load(A) | P_{OUT} (W) | P_{IN} (W) |
|------------------|--------------------|---------------|--------------|
| 5.08 - 0.018 | 3.35 - 0.102 | 0.43 | 0.863 |
| 5.04 - 0.018 | 3.35 - 0.079 | 0.36 | 0.751 |
| 4.98 - 0.018 | 3.35 - 0.046 | 0.24 | 0.582 |
| 4.92 - 0.018 | 3.35 - 0.023 | 0.17 | 0.445 |
| 4.47 - 0.000 | 3.35 - 0.000 | 0.00 | 0.221 |

Table 4. Stand-by consumption at $V_{IN} = 230 V_{ac}$

| +5 V(V) @load(A) | +3.3 V(V) @load(A) | P_{OUT} (W) | P_{IN} (W) |
|------------------|--------------------|---------------|--------------|
| 5.08 - 0.018 | 3.35 - 0.102 | 0.43 | 1.138 |
| 5.04 - 0.018 | 3.35 - 0.079 | 0.36 | 1.022 |
| 4.98 - 0.018 | 3.35 - 0.046 | 0.24 | 0.857 |
| 4.92 - 0.018 | 3.35 - 0.023 | 0.17 | 0.740 |
| 4.47 - 0.000 | 3.35 - 0.000 | 0.00 | 0.470 |

2.4 Short-circuit protection

The L6599 is equipped with a current sensing input (pin #6, ISEN) and a dedicated over-current management system. The current flowing in the circuit is detected (through the not dissipative sensing circuit already mentioned in [Section 1](#) and the signal is fed into the ISEN pin. It is internally connected to the input of a first comparator, referenced to 0.8 V, and to that of a second comparator referenced to 1.5 V. If the voltage externally applied to the pin exceeds 0.8 V, the first comparator is tripped causing an internal switch to be turned on discharging the soft-start capacitor CSS.

For output short-circuits, this operation results in a nearly constant peak primary current. Using the L6599, the designer can externally program the maximum time (t_{SH}) that the converter is allowed to run overloaded or under short-circuit conditions. Overloads or short-circuits lasting less than t_{SH} will not cause any other action, hence providing the system with immunity to short duration phenomena. If, instead, t_{SH} is exceeded, an overload protection (OLP) procedure is activated that shuts down the L6599 and, in case of continuous overload/short circuit, results in continuous intermittent operation with a user-defined duty cycle. This function is realized with the pin DELAY (#2), by means of a capacitor C24 and the parallel resistor R37 connected to ground. As the voltage on the ISEN pin exceeds 0.8 V, the first OCP comparator, in addition to discharging CSS, turns on an internal current generator that via the DELAY pin charges C24. As the voltage on C24 reaches 3.5 V, the L6599 stops switching and the PFC_STOP pin is pulled low. Also the internal generator is turned off, so that C24 will now be slowly discharged by R37. The IC will restart when the voltage on C24 becomes less than 0.3 V. Additionally, if the voltage on the ISEN pin reaches 1.5 V for any reason (e.g. transformer saturation), the second comparator will be triggered, the L6599 will shutdown and the operation will be resumed after an on-off cycle.

[Figure 14](#) and [Figure 15](#) illustrate the L6599 short-circuit protection sequence described above. The on-off operation is controlled by the voltage on pin #2 (DELAY), providing for the hiccup mode of the circuit. Thanks to this control pin, the designer can select the hiccup mode timing and thus keep the average output current at a safe level. Please note on the left

side of the figure the very low mean current flowing in the shorted output which is less than 0.3 A.

Figure 14. +24 V output short-circuit waveforms


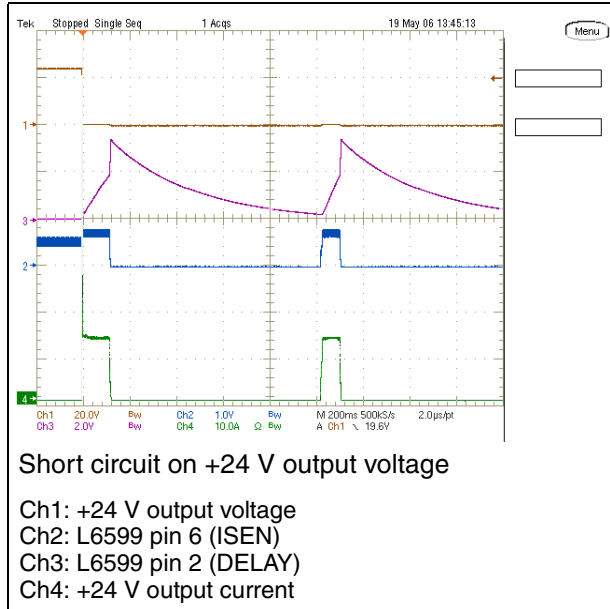


Figure 15. +12 V output short-circuit waveforms

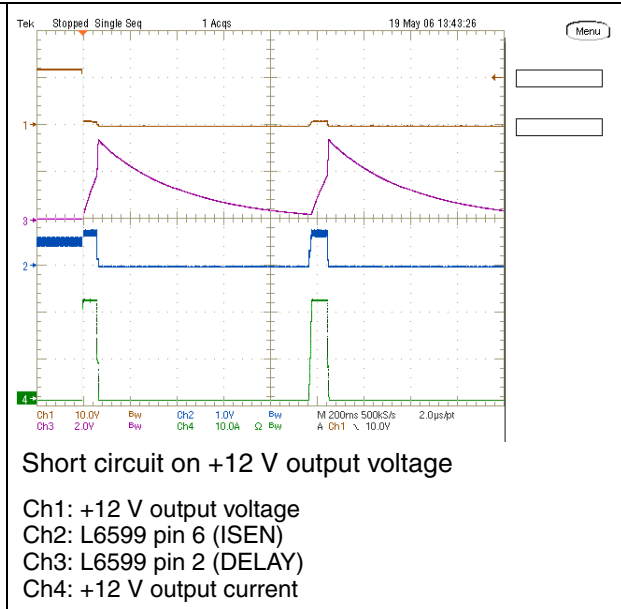

2.5 Overvoltage protection

Both the PFC pre-regulator and the resonant converter are equipped with their own overvoltage protection circuit. The PFC controller L6563 is internally equipped with a dynamic and a static overvoltage protection circuit sensing the error amplifier via the voltage divider dedicated to the feedback loop to sense the PFC output voltage. If an internal threshold is exceeded, the IC limits the PFC output voltage to a programmable, safe value.

Moreover, in the L6563 there is an additional protection against loop failures using an additional divider (R5, R7, R9, R16 and R25) connected to a dedicated pin (PFC_OK, Pin 7) protecting the circuit in case of loop failures or disconnection or deviation from the nominal value of the feedback loop divider. Hence the PFC output voltage is always under control and in case a fault condition is detected the PFC_OK circuitry will latch the L6563 operations and, by means of the PWM_LATCH pin (Pin 8) it will latch the L6599 as well via the DIS pin (Pin 8).

The OVP circuit (see [Figure 4](#)) for the output voltages of the resonant converter uses two zener diodes (D21 and D23) to sense the +24 V and +12 V. If one of the output voltages exceeds the threshold imposed by these zener diodes plus the V_{BE} of Q10, the transistor Q9 starts conducting and the optocoupler U8 opens Q7, so that the V_{AUX} supply voltage of the controller ICs L6563 and L6599 is no longer available. This state is latched until a mains voltage recycle occurs.

3 Thermal tests

In order to check the design reliability, a thermal mapping by means of an IR Camera was performed. *Figure 16* and *Figure 17* show the thermal measurements of the board, component side, at nominal input voltage. The correlation between measurement points and components is indicated for both diagrams.

Figure 16. Thermal map @115 V_{ac} - full load

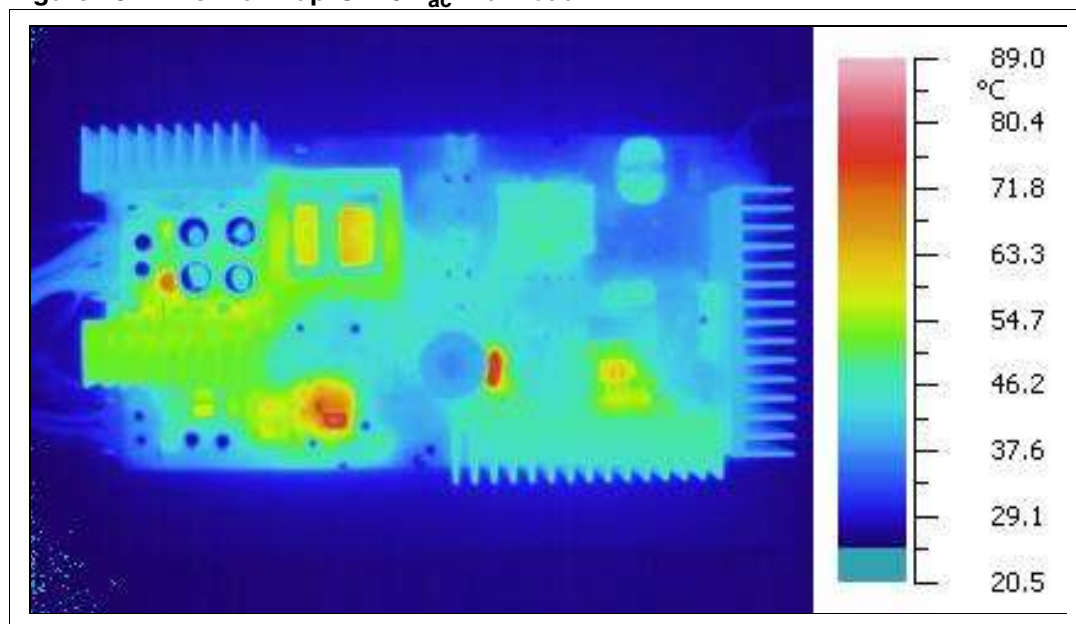


Figure 17. Thermal map at 230 V_{ac} - full load

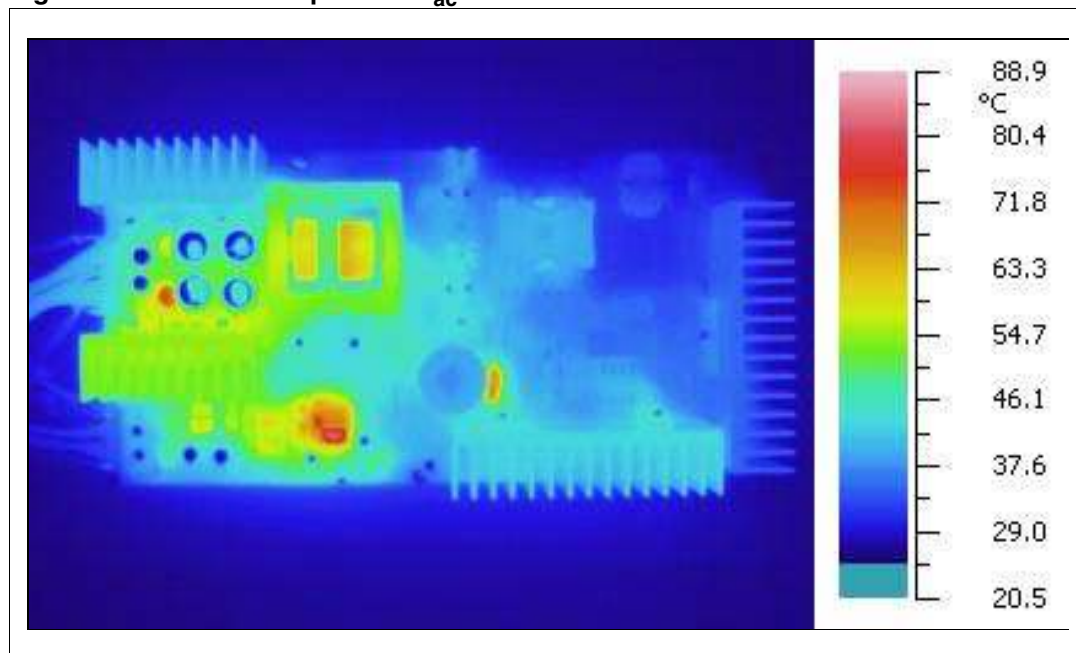


Table 5. Key components temperature at 115 V_{ac} - full load

| Ambient temperature: 25° C | |
|----------------------------|-----------|
| Item | Temp (°C) |
| D2 | 44.9 |
| Q2 | 53.7 |
| D3 | 50.3 |
| L1 | 47.0 |
| L3 | 46.0 |
| L4 (Fe) | 45.8 |
| L4 (Cu) | 49.2 |
| C8 | 37.3 |
| R2 | 78.0 |
| Q5 | 40.2 |
| Q6 | 46.7 |
| D8A | 56.2 |
| D8B | 56.7 |
| D10A | 42.1 |
| D10B | 42.7 |
| C29 | 45.1 |
| C30 | 46.1 |
| C37 | 42.0 |
| C38 | 41.6 |
| L5 | 71.2 |
| L6 | 56.0 |
| T1 | 51.7 |
| T1 | 56.8 |
| U5 | 81.4 |
| D14 | 74.2 |
| D15 | 57.6 |
| D16 | 55.3 |
| T2 | 56.4 |

Table 6. Key components temperature at 230 V_{AC} - full load

| Ambient temperature: 25° C | |
|----------------------------|-----------|
| Item | Temp (°C) |
| D2 | 37.1 |
| Q2 | 46.6 |
| D3 | 44.0 |
| L1 | 33.6 |
| L3 | 34.9 |
| L4 (Fe) | 39.1 |
| L4 (Cu) | 41.2 |
| C8 | 37.1 |
| R2 | 65.8 |
| Q5 | 38.3 |
| Q6 | 43.7 |
| D8A | 56.4 |
| D8B | 55.6 |
| D10A | 42.1 |
| D10B | 43.8 |
| C29 | 48.2 |
| C30 | 47.4 |
| C37 | 44.3 |
| C38 | 44.5 |
| L5 | 73.6 |
| L6 | 57.3 |
| T1 (Fe) | 51.3 |
| T1 (Cu) | 58.8 |
| U5 | 81.8 |
| D14 | 74.4 |
| D15 | 59.4 |
| D16 | 56.3 |
| T2 | 56.8 |

All other board components work within the temperature limits, assuring a reliable long term operation of the power supply.

Note that the temperatures of L4 and T1 have been measured both on the ferrite core (Fe) and on the copper (Cu).

4 Conducted emission pre-compliance test

The limits indicated on both diagrams at 115 V_{ac} and 230 V_{ac} comply with EN55022 Class-B specifications. The measurements have been taken in Quasi Peak detection mode.

Figure 18. CE quasi peak measurement at 115 V_{ac} and full load


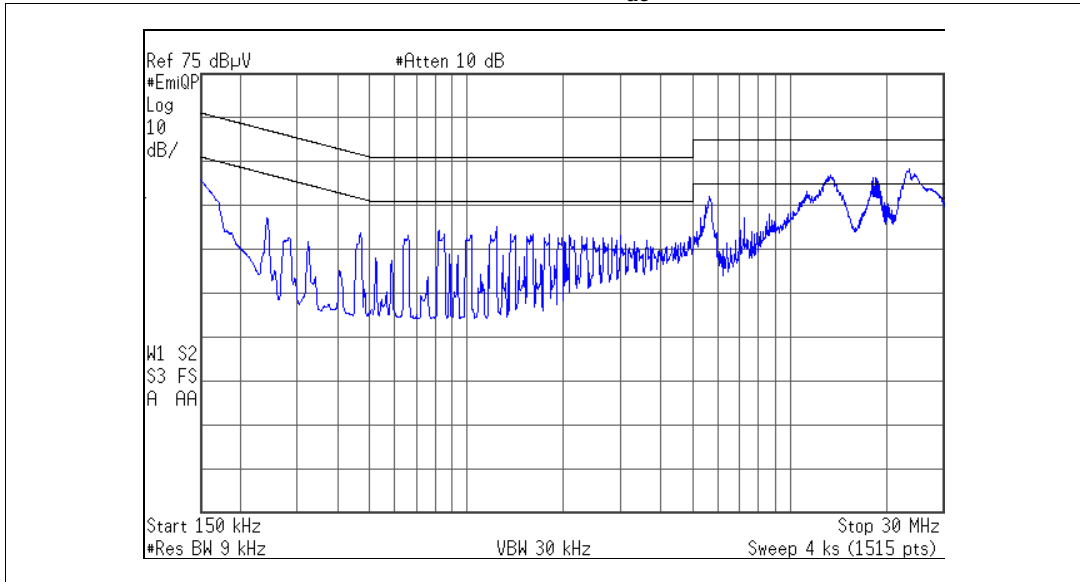


Figure 19. CE quasi peak measurement at 230 V_{ac} and full load

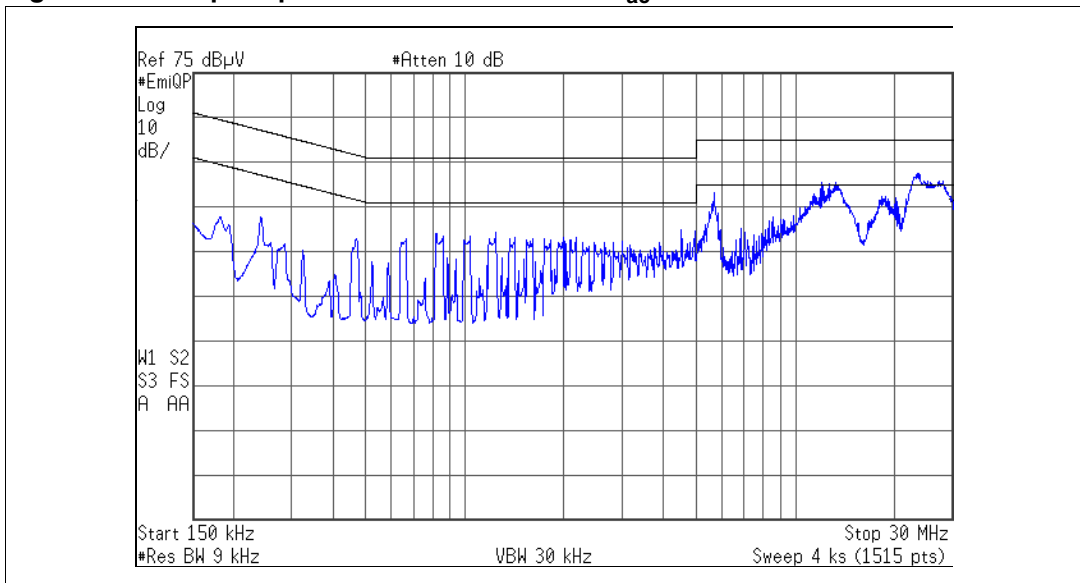

5 Bill of materials

Table 7. Bill of materials

| Item | Part type/value | Description | Supplier |
|------|---------------------------------|--|---------------------|
| C2 | 100 nF-X2 | 275 V _{ac} X2 Safety Capacitor MKP R46 | Arcotronics |
| C3 | 330 nF-X2 | 275 V _{ac} X2 Safety Capacitor MKP R46 | Arcotronics |
| C4 | 680 nF-X2 | 275 V _{ac} X2 Safety Capacitor MKP R46 | Arcotronics |
| C5 | 330 nF/630 V | Polypropylene Capacitor High Ripple MKP R71 | Arcotronics - Epcos |
| C6 | 680 nF/630 V | Polypropylene Capacitor High Ripple MKP R71 | Arcotronics - Epcos |
| C7 | 470 nF/630 V | Polypropylene Capacitor High Ripple MKP R71 | Arcotronics - Epcos |
| C8 | 220 µF/450 V | Aluminium ELCAP USC Series 85 DEG SNAP-IN | Rubycon |
| C9 | 2nF2-Y1 | 400 V _{ac} Y1 Safety Ceramic Disk Capacitor | Murata |
| C10 | 2nF2-Y1 | 250 V _{ac} Y1 Safety Ceramic Disk Capacitor | Murata |
| C11 | 2nF2-Y1 | 250 V _{ac} Y1 Safety Ceramic Disk Capacitor | Murata |
| C12 | 100 nF | 50 V 1206 SMD Cernap General Purpose | BC Components |
| C13 | 10 µF/50 V | Aluminium ELCAP General Purpose 85 DEG | Rubycon |
| C14 | 100 nF | 50 V 1206 SMD Cernap General Purpose | BC Components |
| C15 | 100 pF | 100 V 0805 SMD Cernap General Purpose | BC Components |
| C16 | 1 µF | 25 V 1206 SMD Cernap General Purpose | BC Components |
| C17 | 220 pF | 100 V 0805 SMD Cernap General Purpose | BC Components |
| C18 | 330 pF | 100 V 0805 SMD Cernap General Purpose | BC Components |
| C19 | 10 nF | 100 V 0805 SMD Cernap General Purpose | BC Components |
| C20 | 470 nF | 50 V 1206 SMD Cernap General Purpose | BC Components |
| C21 | 2nF2 | 100 V 1206 SMD Cernap General Purpose | BC Components |
| C22 | 10 nF | 100 V 0805 SMD Cernap General Purpose | BC Components |
| C23 | 2 µF2 | 25 V 1206 SMD Cernap General Purpose | BC Components |
| C24 | 470 nF | 25 V 1206 SMD Cernap General Purpose | BC Components |
| C25 | 470 µF/35 V | Aluminium ELCAP YXF Series 105 DEG | Rubycon |
| C26 | 270 pF | 100 V 0805 SMD Cernap General Purpose | BC Components |
| C27 | 100 nF | 50 V 1206 SMD Cernap General Purpose | BC Components |
| C28 | 22 nF/630 V/400 V _{ac} | Polypropylene Capacitor High Ripple PHE450 | RIFA-EVOX |
| C29 | 2200 µF/35 V | Aluminium ELCAP YXF Series 105 DEG | Rubycon |
| C30 | 2200 µF/35 V | Aluminium ELCAP YXF Series 105 DEG | Rubycon |
| C31 | 10 µF/50 V | Aluminium ELCAP General Purpose 85 DEG | Rubycon |
| C32 | 100 nF | 50 V 1206 SMD Cernap General Purpose | BC Components |
| C33 | 4 nF7 | 100 V 1206 SMD Cernap General Purpose | BC Components |

Table 7. Bill of materials (continued)

| Item | Part type/value | Description | Supplier |
|--------|-----------------|--|--------------------|
| C34 | 220 pF/630 V | Polypropylene Capacitor High Ripple PFR | RIFA-EVOX |
| C35 | 470 µF/25 V | Aluminium ELCAP YXF Series 105 DEG | Rubycon |
| C37 | 2200 µF/25 V | Aluminium ELCAP YXF Series 105 DEG | Rubycon |
| C38 | 2200 µF/25 V | Aluminium ELCAP YXF Series 105 DEG | Rubycon |
| C39 | 220 nF | 50 V 1206 SMD CerCap General Purpose | BC Components |
| C40 | 10 nF | 100 V 1206 SMD CerCap General Purpose | BC Components |
| C41 | 10 µF/50 V | Aluminium ELCAP General Purpose 85 DEG | Rubycon |
| C44 | 47 nF | 100 V 1206 SMD CerCap General Purpose | BC Components |
| C45 | 1000 µF/10 V | Aluminium ELCAP YXF Series 105 DEG | Rubycon |
| C46 | 100 µF/10 V | Aluminium ELCAP YXF Series 105 DEG | Rubycon |
| C47 | 1000 µF/10 V | Aluminium ELCAP YXF Series 105 DEG | Rubycon |
| C48 | 10 µF/50 V | Aluminium ELCAP General Purpose 85 DEG | Rubycon |
| C49 | 100 µF/10 V | Aluminium ELCAP YXF Series 105 DEG | Rubycon |
| C50 | 10 µF/50 V | Aluminium ELCAP General Purpose 85 DEG | Rubycon |
| C51 | 100 nF | 100 V 0805 SMD CerCap General Purpose | BC Components |
| C52 | 47 nF | 100 V 0805 SMD CerCap General Purpose | BC Components |
| C53 | 2 nF2 | 100 V 0805 SMD CerCap General Purpose | BC Components |
| C54 | 100 nF | 50 V 1206 SMD CerCap General Purpose | BC Components |
| C55 | 10 µF/50 V | Aluminium ELCAP General Purpose 85 DEG | Rubycon |
| C56 | 100 nF | 50 V 1206 SMD CerCap General Purpose | BC Components |
| C57 | 1nF0 | 100 V 0805 SMD CerCap General Purpose | BC Components |
| C58 | 10 nF | 50 V X7R Standard Ceramic Capacitor | BC Components |
| D1 | 1N5406 | General Purpose Rectifier | Vishay |
| D2 | D15XB60 | Single Phase Bridge Rectifier | Shindengen |
| D3 | STTH8R06 | TO220FP Ultrafast High Voltage Rectifier | STMicroelectronics |
| D5 | LL4148 | MINIMELF Fast Switching Diode | Vishay |
| D6 | LL4148 | MINIMELF Fast Switching Diode | Vishay |
| D7 | LL4148 | MINIMELF Fast Switching Diode | Vishay |
| D8A-B | STPS20H100CF | TO220FP Power Schottky Rectifier | STMicroelectronics |
| D9 | LL4148 | MINIMELF Fast Switching Diode | Vishay |
| D10A-B | STPS20L40CF | TO220FP Power Schottky Rectifier | STMicroelectronics |
| D11 | LL4148 | MINIMELF Fast Switching Diode | Vishay |
| D12 | LL4148 | MINIMELF Fast Switching Diode | Vishay |
| D13 | C-12 V | BZV55-C Series Zener Diode | Vishay |
| D14 | PKC-136 | Peak Clamp Transil | STMicroelectronics |

Table 7. Bill of materials (continued)

| Item | Part type/value | Description | Supplier |
|------|-----------------------|---|--------------------|
| D15 | 1N5822 | Power Schottky Rectifier | STMicroelectronics |
| D16 | 1N5821 | Power Schottky Rectifier | STMicroelectronics |
| D17 | LL4148 | MINIMELF Fast Switching Diode | Vishay |
| D18 | B-10 V | BZV55-B Series Zener Diode | Vishay |
| D19 | C-30 V | BZV55-C Series Zener Diode | Vishay |
| D20 | BAV103 | General Purpose Diode | Vishay |
| D21 | B-27 V | BZV55-B Series Zener Diode | Vishay |
| D22 | C-15 V | BZV55-C Series Zener Diode | Vishay |
| D23 | B-15 V | BZV55-B Series ZENER DIODE | Vishay |
| F1 | 6.3A/250 V | T Type Fuse 5 X 20 High Capability & Fuseholder | Wickmann |
| J1 | CON2-IN | 3-Pin Connector (Central Removed) P 3.96 KK Series | Molex |
| J2 | CON8 | 8-Pin Connector P 3.96 KK Series | Molex |
| J3 | CON10 | 10-Pin Connector P 2.54 MTA Series | AMP |
| L1 | CM-TF2628V-5 mH-3 A | TF2628 Series Common Mode Toroidal Inductor | TDK |
| L3 | DM-LSR-72 μ H-3 A | LSR1803-2 Differential Mode Toroidal Inductor | Delta |
| L4 | PQ35-900 μ H | 86H-5409 Boost Inductor | Delta |
| L5 | 2 μ H2 | RFB0807 Drum Core Inductor | Coilcraft |
| L6 | 2 μ H2 | RFB0807 Drum Core Inductor | Coilcraft |
| L7 | 33 μ H | RFB0807 Drum Core Inductor | Coilcraft |
| L8 | 33 μ H | RFB0807 Drum Core Inductor | Coilcraft |
| Q2 | STP12NM50FP | TO220FP N-Channel Power MOSFET | STMicroelectronics |
| Q3 | BC857C | SOT23 Small Signal PNP Transistor | STMicroelectronics |
| Q5 | STP14NK50Z | TO220FP N-Channel Power MOSFET | STMicroelectronics |
| Q6 | STP14NK50Z | TO220FP N-Channel Power MOSFET | STMicroelectronics |
| Q7 | BC547C | TO92 Small Signal PNP Transistor | STMicroelectronics |
| Q8 | BC847C | SOT23 Small Signal PNP Transistor | STMicroelectronics |
| Q9 | BC857C | SOT23 Small Signal PNP Transistor | STMicroelectronics |
| Q10 | BC847C | SOT23 Small Signal NPN Transistor | STMicroelectronics |
| Q11 | BC547C | TO92 Small Signal PNP Transistor | STMicroelectronics |
| R1 | 1M5 | VR25 Type High Voltage Resistor | BC Components |
| R2 | NTC 2R5-S237 | NTC RESISTOR 2R5 S237 Series | Epcos |
| R3 | 680 k Ω | 1206 SMD Standard Film RES 1/4 W 5% 200 ppm/ $^{\circ}$ C | BC Components |
| R4 | 47 | 0805 SMD Standard Film RES 1/8 W 5% 200 ppm/ $^{\circ}$ C | BC Components |
| R5 | 2M2 | 1206 SMD Standard Film RES 1/4 W 1% 100 ppm/ $^{\circ}$ C | BC Components |
| R6 | 680 k Ω | 1206 SMD Standard Film RES 1/4 W 5% 20 0ppm/ $^{\circ}$ C | BC Components |

Table 7. Bill of materials (continued)

| Item | Part type/value | Description | Supplier |
|------|-----------------|--|---------------|
| R7 | 2M2 | 1206 SMD Standard Film RES 1/4 W 1% 100 ppm/°C | BC Components |
| R8 | 680 kΩ | 1206 SMD Standard Film RES 1/4 W 5% 200 ppm/°C | BC Components |
| R9 | 2M2 | 1206 SMD Standard Film RES 1/4 W 1% 100 ppm/°C | BC Components |
| R10 | 100 kΩ | 0805 SMD Standard Film RES 1/8 W 5% 200 ppm/°C | BC Components |
| R11 | 15 kΩ | 0805 SMD Standard Film RES 1/8W 5% 200ppm/°C | BC Components |
| R13 | 56 kΩ | 1206 SMD Standard Film RES 1/8 W 5% 200 ppm/°C | BC Components |
| R14 | 1k5 | 0805 SMD Standard Film RES 1/8 W 1% 100 ppm/°C | BC Components |
| R16 | 5k1 | 1206 SMD Standard Film RES 1/4 W 1% 100 ppm/°C | BC Components |
| R17 | 15 kΩ | 0805 SMD Standard Film RES 1/8 W 1% 100 ppm/°C | BC Components |
| R18 | 6R8 | 0805 SMD Standard Film RES 1/8 W 5% 200 ppm/°C | BC Components |
| R19 | 1K0 | 0805 SMD Standard Film RES 1/8 W 5% 200 ppm/°C | BC Components |
| R20 | 1k0 | Standard Metal Film RES 1/4 W 5% 200 ppm/°C | BC Components |
| R21 | 2R2 | Standard Metal Film RES 1/4 W 5% 200 ppm/°C | BC Components |
| R22 | 0R68 | PR01 Power Resistor | BC Components |
| R23 | 0R68 | PR01 Power Resistor | BC Components |
| R24 | 0R68 | PR01 Power Resistor | BC Components |
| R25 | 30 kΩ | 0805 SMD Standard Film RES 1/8 W 1% 100 ppm/°C | BC Components |
| R26 | 150 kΩ | 1206 SMD Standard Film RES 1/8 W 5% 200 ppm/°C | BC Components |
| R28 | 240 kΩ | 0805 SMD Standard Film RES 1/8 W 5% 200 ppm/°C | BC Components |
| R29 | 1k5 | 0805 SMD Standard Film RES 1/8 W 5% 200 ppm/°C | BC Components |
| R30 | 620 kΩ | 1206 SMD Standard Film RES 1/4 W 5% 200 ppm/°C | BC Components |
| R31 | 620 kΩ | 1206 SMD Standard Film RES 1/4 W 5% 200 ppm/°C | BC Components |
| R32 | 10 kΩ | 0805 SMD Standard Film RES 1/8 W 5% 200 ppm/°C | BC Components |
| R33 | 0R | 0805 SMD Standard Film RES 1/8 W | BC Components |
| R34 | 2k7 | 0805 SMD Standard Film RES 1/8 W 5% 200 ppm/°C | BC Components |
| R35 | 47 | 0805 SMD Standard Film RES 1/8 W 5% 200 ppm/°C | BC Components |
| R36 | 0R | 0805 SMD Standard Film RES 1/8 W | BC Components |
| R37 | 1M0 | 0805 SMD Standard Film RES 1/8 W 5% 200 ppm/°C | BC Components |
| R38 | 47 | Standard Metal Film RES 1/4W 5% 200ppm/°C | BC Components |
| R39 | 0R | 0805 SMD Standard Film RES 1/8 W | BC Components |
| R40 | 47 | 0805 SMD Standard Film RES 1/8 W 5% 200 ppm/°C | BC Components |
| R41 | 16 kΩ | 0805 SMD Standard Film RES 1/8 W 1% 100 ppm/°C | BC Components |
| R42 | 10 | 1206 SMD Standard Film RES 1/8 W 5% 200 ppm/°C | BC Components |
| R43 | 150 | 1206 SMD Standard Film RES 1/4 W 5% 200 ppm/°C | BC Components |
| R45 | 75R | 1206 SMD Standard Film RES 1/4 W 1% 100 ppm/°C | BC Components |

Table 7. Bill of materials (continued)

| Item | Part type/value | Description | Supplier |
|------|-----------------|--|--------------------|
| R46 | 5k6 | 0805 SMD Standard Film RES 1/8 W 5% 200 ppm/°C | BC Components |
| R47 | 10 kΩ | 1206 SMD Standard Film RES 1/8 W 5% 200 ppm/°C | BC Components |
| R51 | 2k2 | 0805 SMD Standard Film RES 1/8 W 5% 200 ppm/°C | BC Components |
| R52 | 5k6 | 0805 SMD Standard Film RES 1/8 W 5% 200 ppm/°C | BC Components |
| R53 | 33 kΩ | 1206 SMD Standard Film RES 1/4 W 1% 100 ppm/°C | BC Components |
| R54 | 5k6 | 1206 SMD Standard Film RES 1/8 W 5% 200 ppm/°C | BC Components |
| R56 | 1k0 | 0805 SMD Standard Film RES 1/8 W 5% 200 ppm/°C | BC Components |
| R57 | 15 kΩ | 1206 SMD Standard Film RES 1/4 W 1% 100 ppm/°C | BC Components |
| R58 | 0R | 1206 SMD Standard Film RES 1/4 W | BC Components |
| R59 | 27 kΩ | 0805 SMD Standard Film RES 1/8 W 5% 200 ppm/°C | BC Components |
| R60 | 3k9 | 0805 SMD Standard Film RES 1/8 W 1% 100 ppm/°C | BC Components |
| R61 | 3k9 | 0805 SMD Standard Film RES 1/8 W 1% 100 ppm/°C | BC Components |
| R62 | 47 | 0805 SMD Standard Film RES 1/8 W 5% 200 ppm/°C | BC Components |
| R64 | 1k6 | 0805 SMD Standard Film RES 1/8 W 1% 100 ppm/°C | BC Components |
| R66 | 1k0 | 0805 SMD Standard Film RES 1/8 W 5% 200 ppm/°C | BC Components |
| R67 | 1k0 | 0805 SMD Standard Film RES 1/8 W 5% 200 ppm/°C | BC Components |
| R68 | 22 kΩ | 0805 SMD Standard Film RES 1/8 W 5% 200 ppm/°C | BC Components |
| R69 | 0R | 0805 SMD Standard Film RES 1/8W 5% 200ppm/°C | BC Components |
| R70 | 22R | 0805 SMD Standard Film RES 1/8 W 5% 200 ppm/°C | BC Components |
| R71 | 10 kΩ | 0805 SMD Standard Film RES 1/8 W 5% 200 ppm/°C | BC Components |
| R72 | 10 kΩ | 0805 SMD Standard Film RES 1/8 W 5% 200ppm/°C | BC Components |
| R73 | 8k2 | 0805 SMD Standard Film RES 1/8 W 5% 200 ppm/°C | BC Components |
| R74 | 10 kΩ | 0805 SMD Standard Film RES 1/8 W 5% 200 ppm/°C | BC Components |
| R75 | 0R | 1206 SMD Standard Film RES 1/4 W | BC Components |
| R76 | 1k5 | 1206 SMD Standard Film RES 1/4 W 1% 100 ppm/°C | BC Components |
| R77 | 4k7 | 0805 SMD Standard Film RES 1/8 W 1% 100 ppm/°C | BC Components |
| R79 | 1k0 | 0805 SMD Standard Film RES 1/8 W 5% 200 ppm/°C | BC Components |
| R82 | 1k5 | 1206 SMD Standard Film RES 1/4 W 1% 100 ppm/°C | BC Components |
| R83 | 1M0 | VR25 Type High Voltage Resistor | BC Components |
| R84 | 15 0kΩ | Standard Metal Film RES 1/4 W 5% 200 ppm/°C | BC Components |
| T1 | T-RES-ER49 | 86H-5411 Type Resonant Transformer ER49-27-17 | Delta |
| T2 | T-FLY-AUX-E20 | 86A-6079-R Type Flyback Transformer E20 Core | Delta |
| U1 | L6563 | Advanced Transition Mode PFC Controller | STMicroelectronics |
| U2 | L6599 | High Voltage Resonant Controller | STMicroelectronics |
| U3 | SFH617A-2 | 63-125% CTR Selection Optocoupler | Infineon |

Table 7. Bill of materials (continued)

| Item | Part type/value | Description | Supplier |
|------|-----------------|---|--------------------|
| U4 | TL431 | TO92 Programmable Shunt Voltage Regulator | STMicroelectronics |
| U5 | VIPer12A-E | Low Power Off Line SMPS Primary Switcher | STMicroelectronics |
| U6 | SFH617A-2 | 63-125% CTR Selection Optocoupler | Infineon |
| U7 | TL431 | TO92 Programmable Shunt Voltage Regulator | STMicroelectronics |
| U8 | SFH617A-2 | 63-125% CTR Selection Optocoupler | Infineon |

Note: Q9 and R72: Mounted by reworking on PCB
 Q11, R83, R84 and C58: Added by reworking on PCB

6 PFC coil specification


- Application type: Consumer, home appliance
- Transformer type: Open
- Coil former: vertical type, 6+6 pins
- Maximum temperature rise: 45° C
- Maximum operating ambient temperature: 60° C

6.1 Electrical characteristics

- Converter topology: FOT-PFC Pre-regulator
- Core type: PQ35-35 material grade PC44 or equivalent
- Maximum operating frequency: 100 kHz
- Primary inductance: 900 μH ±10% @1 kHz - 0.25 V (see [Note 1](#))
- Primary RMS current: 2.65 A

Note: 1 Measured between Pins 2 and 3 and Pins 10 and 11

Figure 20. PFC coil electrical diagram

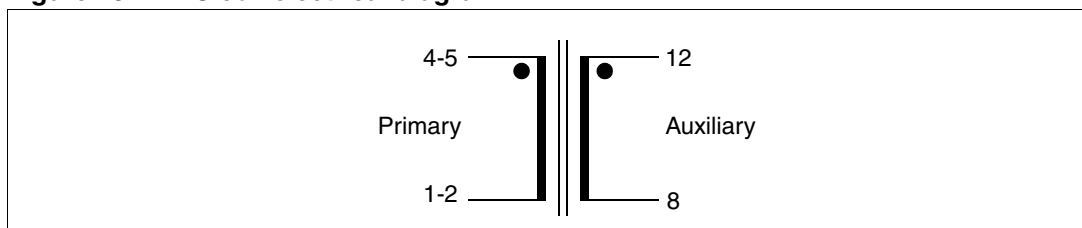

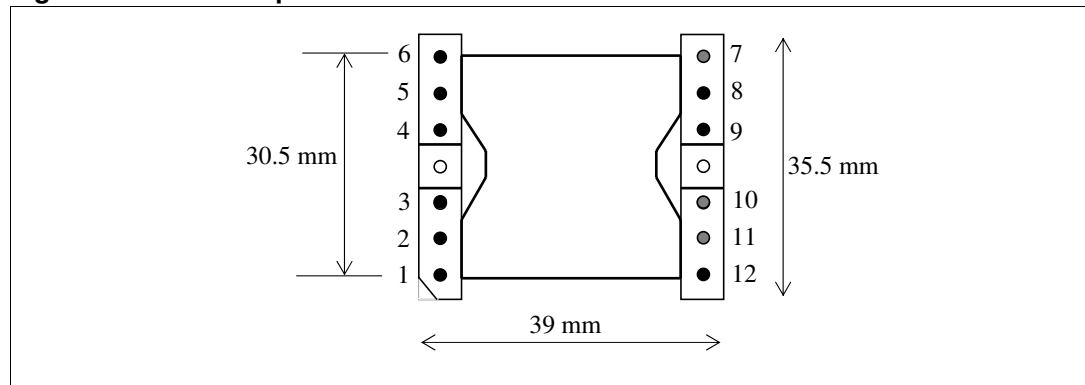
Note: The auxiliary winding is not used in this design, but is foreseen for another application

Table 8. PFC coil winding characteristics

| Start pins | End pins | Turn number | Wire type | Wire diameter (mm) | Notes |
|------------|----------|-------------|------------------|-----------------------------|--------|
| 12 | 8 | 5 (spaced) | Single | 0.28 \varnothing | Bottom |
| 4 and 5 | 1 and 2 | 70 | Multistrand - G2 | Litz 0.2 \varnothing x 20 | Top |

6.2 Mechanical aspect and pin numbering

- Maximum height from PCB: 38 mm
- Cut pins: 7, 10 and 11
- Pin distance: 5.08 mm
- Row distance: 35.5 mm

Figure 21. PFC coil pin side view

Note: External copper shield 15 x 0.05 (mm) connected to pin 12 by tinned wire
 Manufacturer: DELTA ELECTRONICS - Part number: 86H-5409

7 Resonant power transformer specification

- Application type: Consumer, home appliance
- Transformer type: Open
- Coil former: Horizontal type, 7+7 pins, 2 Slots
- Maximum temperature rise: 45° C
- Maximum operating ambient temperature: 60° C
- Mains insulation: Compliance with EN60065 specifications

7.1 Electrical characteristics and mechanical aspect

- Converter topology: half-bridge, resonant
- Core type: ER49 - PC44 or equivalent
- Typical operating frequency: 100 kHz
- Primary inductance: 585 $\mu\text{H} \pm 10\%$ @ 1 kHz - 0.25 V (see *Note 1*)
- Leakage inductance: 110 $\mu\text{H} \pm 10\%$ @ 1 kHz - 0.25 V (see *Note 1* and *Note 2*)

Note: 1 Measured between Pins 1 and 3

2 Measured between Pins 1 and 3 with ONLY a secondary winding shorted

Figure 22. Mechanical aspect and pin numbering of resonant transformer

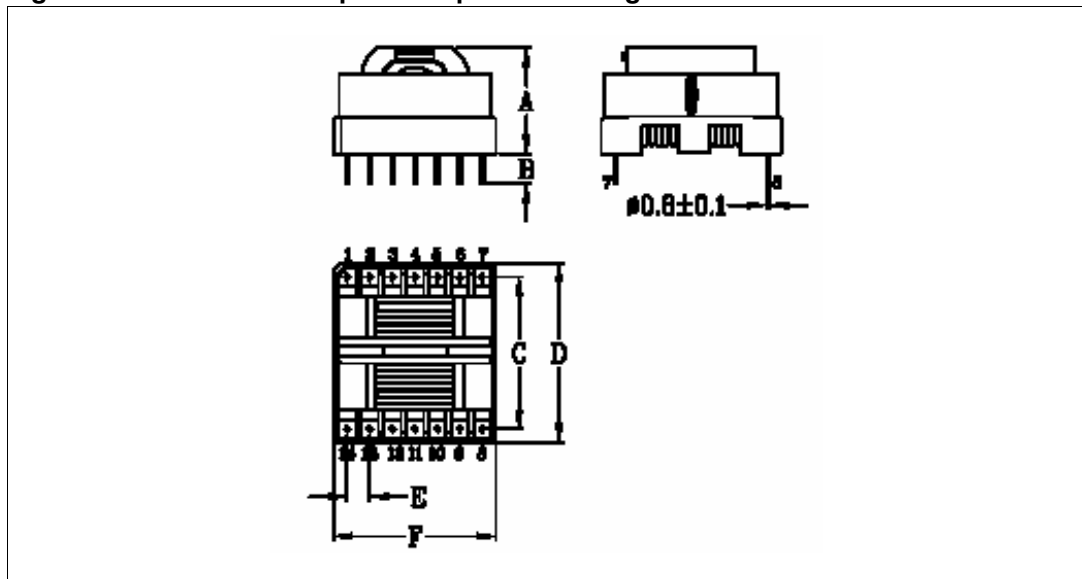


Table 9. Resonant transformer dimensions

| | A | B | C | D | E | F |
|-----------------|----------|---------------|----------------|--------|---------------|----------|
| Dimensions (mm) | 39.0 MAX | 3.5 \pm 0.5 | 41.6 \pm 0.4 | 51 MAX | 7.0 \pm 0.2 | 51.5 MAX |

Figure 23. Resonant transformer electrical diagram


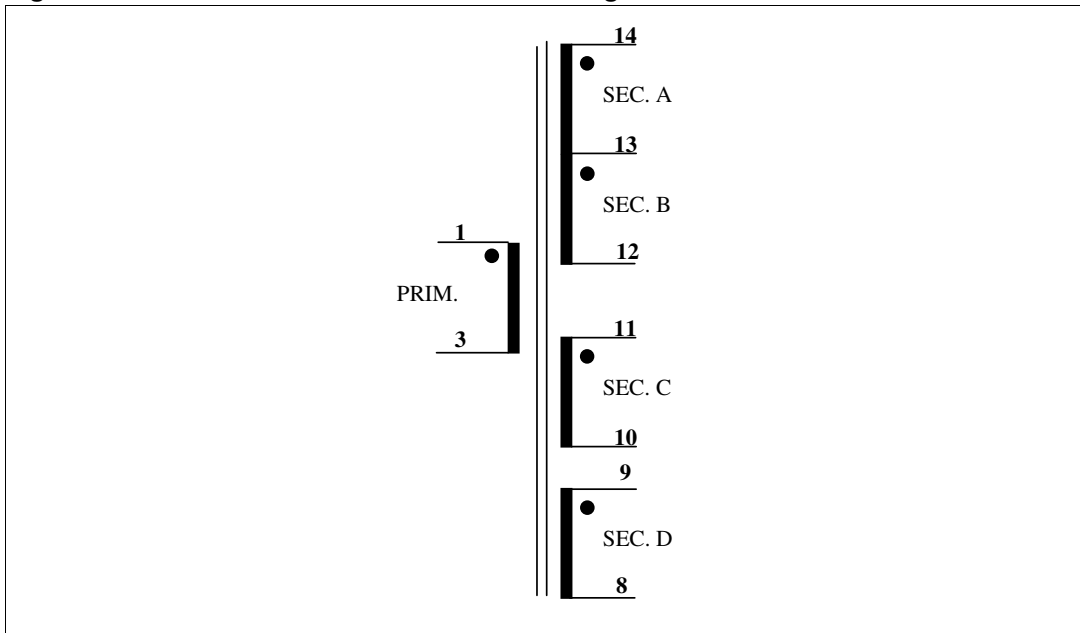


Table 10. Resonant transformer winding characteristics

| Pins | Winding | RMS current | Turn number | Wire type [mm] |
|---------|-----------------------|----------------------|-------------|---------------------|
| 1 - 3 | Primary | 1.5 A _{RMS} | 36 | LITZ - dia. 0.15x20 |
| 14 - 13 | Sec. A ⁽¹⁾ | 6.7 A _{RMS} | 4 | LITZ - dia. 0.20x30 |
| 13 - 12 | Sec. B ⁽¹⁾ | 6.7 A _{RMS} | 4 | LITZ - dia. 0.20x30 |
| 11 - 10 | Sec. C ⁽²⁾ | 5.6 A _{RMS} | 2 | LITZ - dia. 0.20x30 |
| 9 - 8 | Sec. D ⁽²⁾ | 5.6 A _{RMS} | 2 | LITZ - dia. 0.20x30 |

1. Secondary windings A and B must be wound in parallel
2. Aux winding is wound on top of primary winding

Figure 24. Resonant transformer winding position on coil former

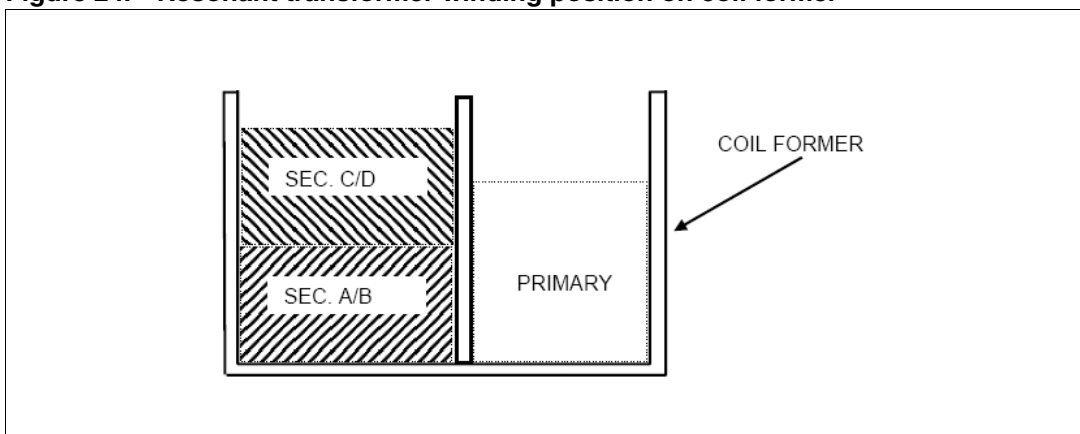

Note: Manufacturer: DELTA ELECTRONICS - Part number: 86H-5411

8 Auxiliary flyback power transformer

- Application type: Consumer, home appliance
- Transformer type: Open
- Winding type: Layer
- Coil former: Horizontal type, 4+5 pins
- Maximum temperature rise: 45° C
- Maximum operating ambient temperature: 60° C
- Mains insulation: Complies with EN60065 specifications

8.1 Electrical characteristics

- Converter topology: Flyback, DCM/CCM mode
- Core type: E20-N67 or equivalent
- Operating frequency: 60 kHz
- Primary inductance: 4.20 mH ±10% @ 1 kHz - 0.25 V (see [Note 1](#))
- Leakage inductance: 50 µH MAX @ 100 kHz - 0.25 V (see [Note 2](#))
- Maximum peak primary current: 0.38 Apk
- RMS primary current: 0.2 A_{RMS}

Note: 1 Measured between Pins 4 and 5

2 Measured between Pins 4 and 5 with all secondary windings shorted

Figure 25. Auxiliary transformer electrical diagram

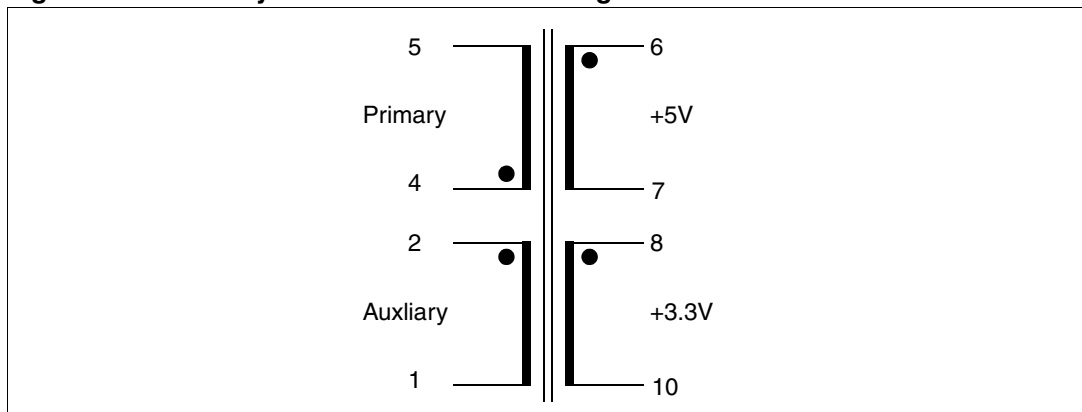


Figure 26. Auxiliary transformer winding position on coil former

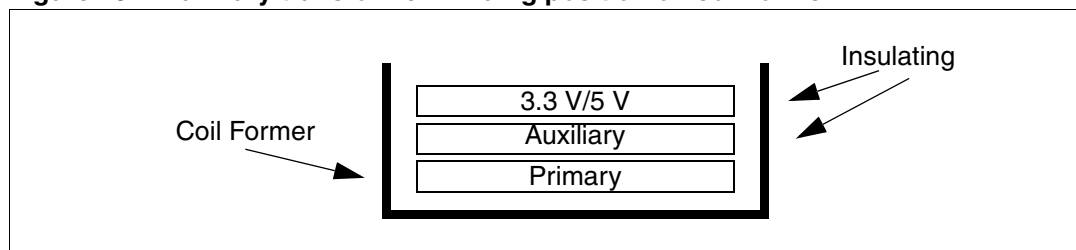


Table 11. Auxiliary transformer winding characteristics

| Pins Start - End | Winding | RMS current | Number of turns | Wire type |
|------------------|---------|-----------------------|-----------------|----------------------|
| 4-5 | PRIMARY | 0.2 A _{RMS} | 140 | G2 - ϕ 0.25 mm |
| 2-1 | AUX | 0.05 A _{RMS} | 29 | G2 - ϕ 0.25 mm |
| 8-10 | 3.3 V | 1.2 A _{RMS} | 7 | TIW - ϕ 0.75 mm |
| 6-7 | 5 V | 1 A _{RMS} | 3 | TIW - ϕ 0.75 mm |

Note: Manufacturer: DELTA ELECTRONICS - Part number: 86A-6079-R

9 Reference design board layout

Figure 27. Copper tracks

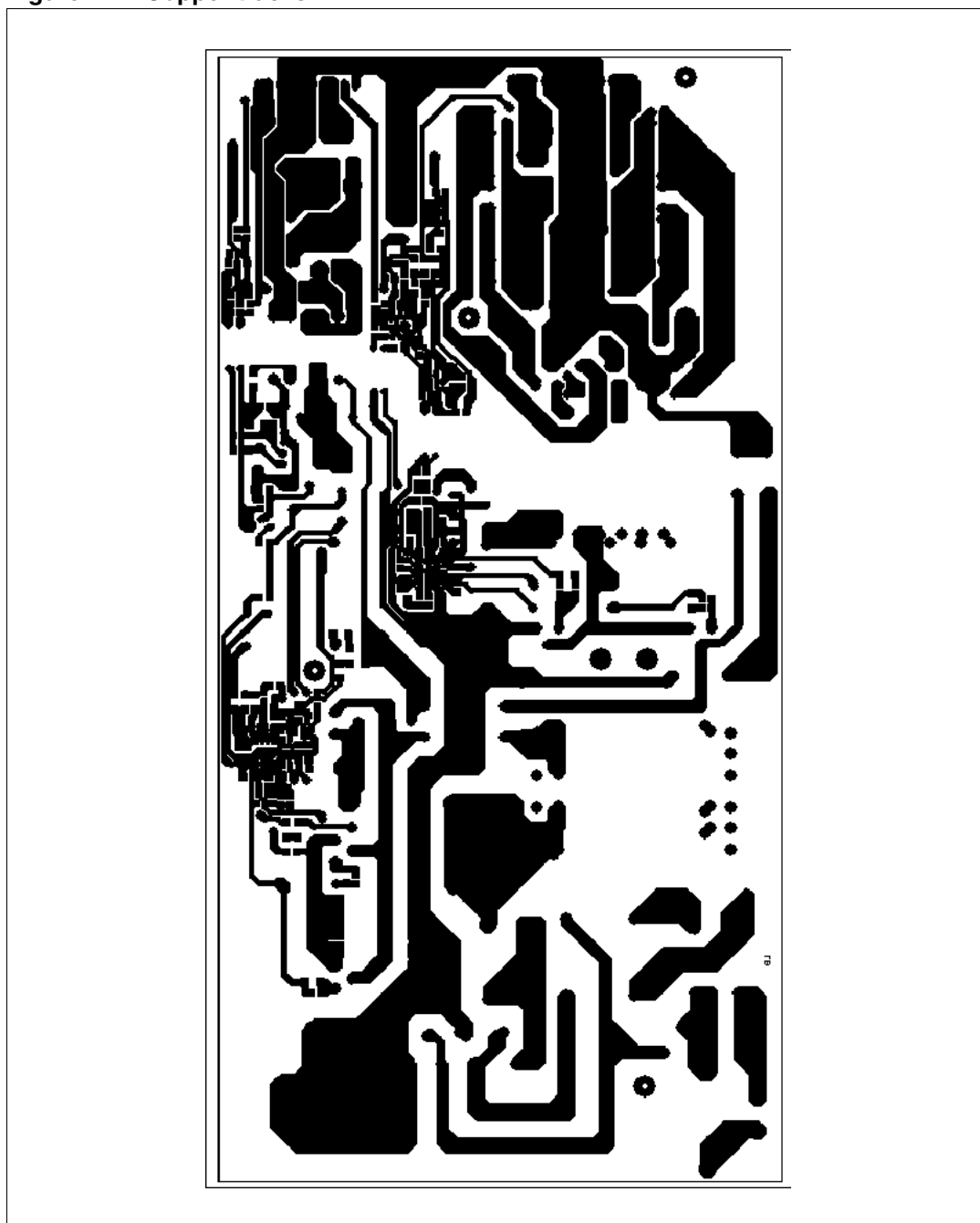


Figure 28. Thru-hole component placing and top silk screen


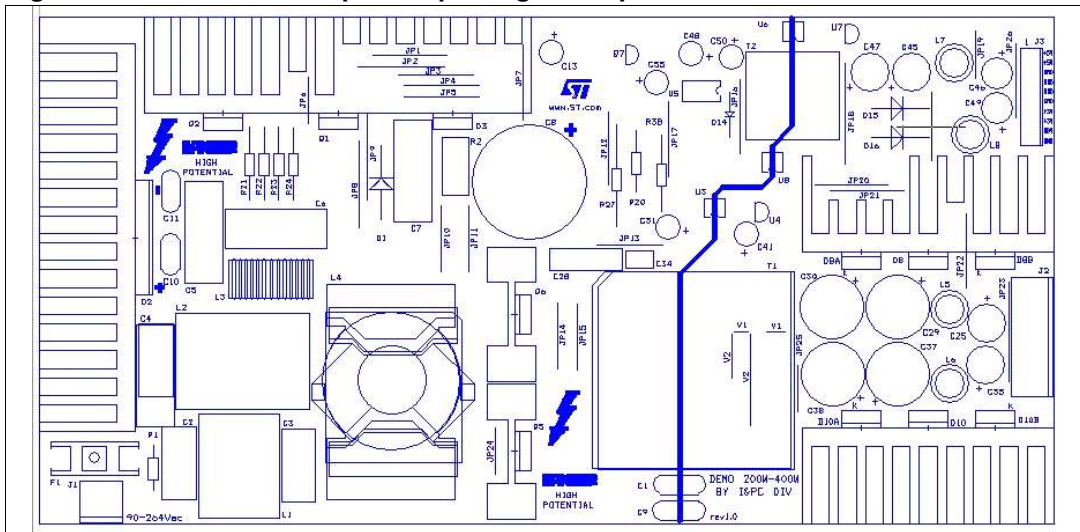


Figure 29. SMT component placing and bottom silk screen

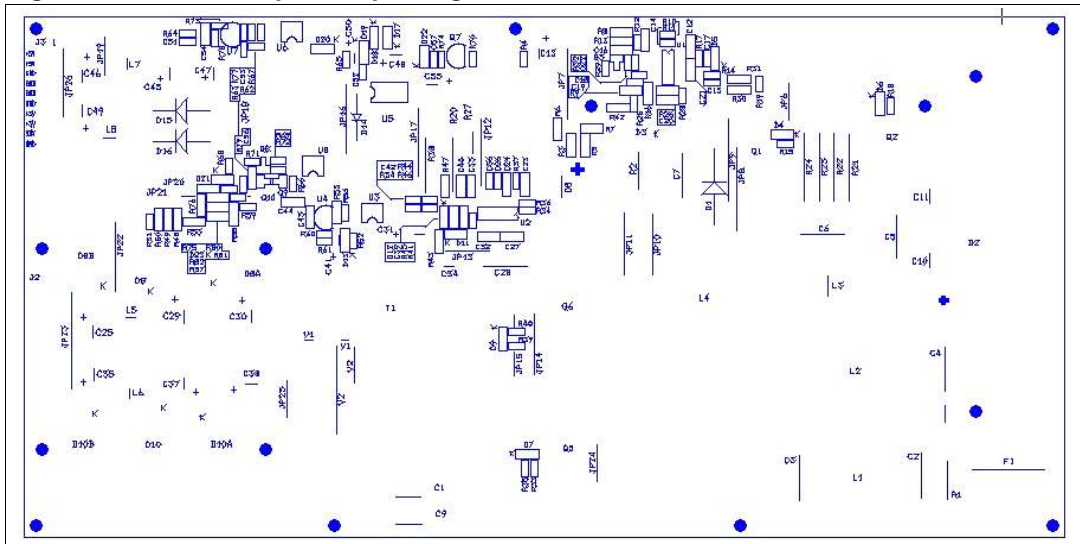

10 Revision history

Table 12. Document revision history

| Date | Revision | Changes |
|-------------|----------|---|
| 02-Aug-2006 | 1 | Initial release |
| 08-Sep-2006 | 2 | <i>Figure 2.</i> modified |
| 25-Jan-2007 | 3 | Minor text change |
| 23-Apr-2007 | 4 | – Cross references updated – <i>Table 7: Bill of materials</i> modified |
| 25-Oct-2007 | 5 | – Modified: <i>Section 8.1: Electrical characteristics</i> – VIPer12A replaced by VIPer12A-E |

Please Read Carefully:

Information in this document is provided solely in connection with ST products. STMicroelectronics NV and its subsidiaries ("ST") reserve the right to make changes, corrections, modifications or improvements, to this document, and the products and services described herein at any time, without notice.

All ST products are sold pursuant to ST's terms and conditions of sale.

Purchasers are solely responsible for the choice, selection and use of the ST products and services described herein, and ST assumes no liability whatsoever relating to the choice, selection or use of the ST products and services described herein.

No license, express or implied, by estoppel or otherwise, to any intellectual property rights is granted under this document. If any part of this document refers to any third party products or services it shall not be deemed a license grant by ST for the use of such third party products or services, or any intellectual property contained therein or considered as a warranty covering the use in any manner whatsoever of such third party products or services or any intellectual property contained therein.

UNLESS OTHERWISE SET FORTH IN ST'S TERMS AND CONDITIONS OF SALE ST DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY WITH RESPECT TO THE USE AND/OR SALE OF ST PRODUCTS INCLUDING WITHOUT LIMITATION IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE (AND THEIR EQUIVALENTS UNDER THE LAWS OF ANY JURISDICTION), OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

UNLESS EXPRESSLY APPROVED IN WRITING BY AN AUTHORIZED ST REPRESENTATIVE, ST PRODUCTS ARE NOT RECOMMENDED, AUTHORIZED OR WARRANTED FOR USE IN MILITARY, AIR CRAFT, SPACE, LIFE SAVING, OR LIFE SUSTAINING APPLICATIONS, NOR IN PRODUCTS OR SYSTEMS WHERE FAILURE OR MALFUNCTION MAY RESULT IN PERSONAL INJURY, DEATH, OR SEVERE PROPERTY OR ENVIRONMENTAL DAMAGE. ST PRODUCTS WHICH ARE NOT SPECIFIED AS "AUTOMOTIVE GRADE" MAY ONLY BE USED IN AUTOMOTIVE APPLICATIONS AT USER'S OWN RISK.

Resale of ST products with provisions different from the statements and/or technical features set forth in this document shall immediately void any warranty granted by ST for the ST product or service described herein and shall not create or extend in any manner whatsoever, any liability of ST.

ST and the ST logo are trademarks or registered trademarks of ST in various countries.

Information in this document supersedes and replaces all information previously supplied.

The ST logo is a registered trademark of STMicroelectronics. All other names are the property of their respective owners.

© 2007 STMicroelectronics - All rights reserved

STMicroelectronics group of companies

Australia - Belgium - Brazil - Canada - China - Czech Republic - Finland - France - Germany - Hong Kong - India - Israel - Italy - Japan - Malaysia - Malta - Morocco - Singapore - Spain - Sweden - Switzerland - United Kingdom - United States of America

www.st.com

