Design Guide: TIDA-050026-23881

24-Port (4 Pair) Power Sourcing Equipment Reference Design for Multi-port Applications



Description

This reference design features an evaluation module for the 24-port PSE system which contains a hardware kit, a system firmware image, and a system firmware GUI. The hardware kit consists of a motherboard (PSEMTHR24EVM-081), an MSP430 daughtercard (PSEMCUDAUEVM-082) and a PSE daughtercard (TPS23881EVM-083). To evaluate the system (both hardware and software), USB2ANY and MSP-FET adapters are also needed.

NOTE: The MSP430F5234 on PSEMCUDAUEVM-082 are programmed with pre-production firmware for EVM testing purposes. Follow the instructions in this user's guide to flash the latest firmware from Tl.com before evaluation.

Resources

TIDA-050026-23881 Design Folder
TPS23881EVM-083 Tool Folder
PSEMTHR24EVM-081 Tool Folder
PSEMCUDAUEVM-082 Tool Folder
TPS23881 Product Folder
MSP430F5234 Product Folder
CSD19538Q3A Product Folder



ASK Our E2E™ Experts


Features

- Onboard power monitoring
- 24 4-pair port system, and expandable to 48 port system
- Highly flexible system with configurable GUI and selectable host interface (I2C or UART)
- Multiport power management
- · Multiple power supplies
- Supports legacy powered devices (PDs)

Applications

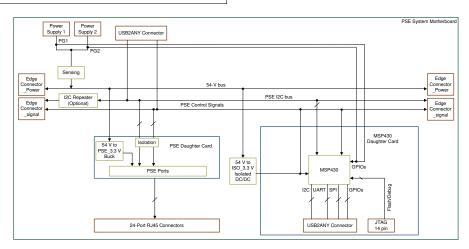- · Campus and branch switches
- Edge router
- Video recorder







System Description www.ti.com



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

1 System Description

This reference design provides a competitive and alternative solution.

In a multiport PSE system, the system-level software is the biggest challenge. The software handles complicated situations and addresses the following challenges:

- The power supply is usually not able to support all ports with a full load due to size and cost
 constraints. The system software manages the port power with priority to keep the total power
 consumption below the power budget.
- There are multiple power supplies in the system. These power supplies could be in sharing mode or backup mode. The system software shuts down low-priority ports fast enough to keep the total power consumption below the remaining power budget.
- There are some legacy PD devices that do not present the standard PoE PD signature. The system software finds a way to supply power to these devices.
- System software limits the port power based on the PD class levels or host configuration.
- When there are load-step changes on multiple ports, the system software acts quickly enough to keep the power consumption below the power budget.

1.1 Key System Specifications

PARAMETER **SPECIFICATIONS DETAILS** 44 V-57 V Input voltage Port power limit 2 W-120 W > 90 W is considered as nonstandard power IEEE 802.3bt Type 3 and Type 4 Compliance PD class level supported Class 0 to class 8 1-2 Number of power supply supported In sharing mode and redundant mode Referred to RJ45 ports Max port number supported 48

Table 1. Key System Specifications

1.2 Description

This reference design features the TPS23881 daughtercard, the octal channel, the TPS23881 device, and the IEEE802.3bt ready PoE PSE controller. When paired with the PSE motherboard PSEMTHR24-081 (sold separately) and MCU daughtercard PSEMCUDAUEVM-082 (sold separately), users can evaluate the TPS23881 device and PSE system firmware solution.

The full PoE evaluation ecosystem includes the following:

- PSEMTHR24EVM-081: motherboard for 24-port PoE PSE applications (sold separately)
- PSEMCUDAUEVM-082: MSP430 daughtercard for 24-port PoE PSE applications (sold separately)
- TPS23881EVM-083: TPS23881 daughtercard for 24 port Type 3 and Type 4 PSE applications (sold separately)
- USB2ANY interface adapter: used with the PSE system firmware GUI for I2C/UART interaction with the PSEMCUDAU-082 daughtercard (sold separately)
- · MSP-FET programmer: used with Uniflash GUI for programming the MSP430 device
- PSE system firmware code image (request access through the TIDA-050026-23881 folder or the PSEMCUDAUEVM-082 tool folder)
- PSE system firmware GUI (request access through the TIDA-050026-23881 folder or the PSEMCUDAUEVM-082 tool folder)



www.ti.com System Overview

NOTE: The MSP430F5234 on PSEMCUDAUEVM-082 is programmed with pre-production firmware for EVM testing purposes. Follow the instructions in this user's guide to flash the latest firmware from the TIDA-050026-23881 folder or the PSEMCUDAUEVM-082 tool folder before evaluation.

2 System Overview

2.1 **Block Diagram**

PSE System Motherboard Power Power Supply 2 USB2ANY Connector PG1 PG2 Sensing Edge Edge Connecto 54-V bus _Power _Power I2C Repeater PSE I2C bus Edge (Optional) PSE Control Signals Edae Connecto _signal _signal MSP430 Isolation 54 V to PSE Daughter Card PSE_3.3 V Buck 54 V to ISO 3.3 V GPIOS MSP430 PSE Ports Isolated DC/DC (see NOTE A //Debug 12C UART SPI GPIOs Flash JTAG 24-Port RJ45 Connectors USB2ANY Connector

Figure 1. TIDA-050026-23881 Block Diagram

- Α The 54-V to 3.3-V isolated DC/DC is for demonstration purposes only. It is not needed in a real system.
- Only connect a USB2ANY connector or JTAG to avoid GND loops.

2.2 Design Considerations

2.2.1 **Input Power**

2.2.1.1 **Vpwr**

DC input voltage is provided through J1 and J3. This board supports a dual power source in sharing mode and redundant mode. If the power supplies are in redundant mode, make sure the main power supply is connected to J1 and a backup power supply is connected to the J3 connector.

The minimum PSE port voltage is 44 VDC for Type 1, 50 V for Type 2 and Type 3, and 52 V for Type 4. The maximum DC voltage at VPWR is 57 V for all types. During evaluation, choose the appropriate DC power supply for the different type environment.

2.2.1.2 3.3 V

A local 3.3 V for local devices (labeled as 3.3 V) is provided by the onboard LM5017 buck converter. The LM5017 device provides a basic power-on sequence and provides a well-controlled and consistent startup to prevent erratic operation. In addition to 44 V to 57 V, the TPS238x requires 3.3 V for the digital circuitry and each TPS2388x device consumes 6-mA typical and 12-mA maximum.



System Overview www.ti.com

2.2.1.3 3.3 V ISO

The reference design kit provides galvanic isolation between PoE power side and host side using digital isolators. The host side power is provided by 3.3 V ISO.

2.2.2 Communication Interface

2.2.2.1 PSE I2C Communication

The motherboard provides two I2C interfaces communicating to PSE:

- 1. J10 on the motherboard (PSEMTHR24EVM-081) provides I2C access to all PSE devices directly. The TPS2388x GUI can communicate to PSE devices with the USB2ANY interface adapter.
- 2. J11 and J12 on the motherboard (PSEMTHR24EVM-081) provides I2C access and system control signal to the MSP430 daughtercard.

2.2.2.2 MCU - Host Communication

The MSP430 daughtercard provides I2C/UART communication port to host through J12 to J14 on MSP430 daughtercard (PSEMCUDAUEVM-082). The PSE system GUI provides host configurations to the PSE system.

Host interface protocol user's guide can be accessed from the TIDA-050026-23881 folder or the PSEMCUDAUEVM-082 tool folder.

2.2.3 MSP430F523x Hardware Design

Table 2. MSP430 GPIO Pin Assignment

TERMINAL	FUNCTION	COMMENT
P3.0	I2C SDA USCI_B0	I2C to PSEs
P3.1	I2C SCL USCI_B0	I2C to PSEs
P4.1	I2C SDA USCI_B1	I2C to host
P4.2	I2C SCL USCI_B1	I2C to host
P4.4	UART TX USCI_A1	UART to host (debug only)
P4.5	UART RX USCI_A1	UART to host (debug only)
P2.7	SPI CLK USCI_A0	SPI to host (reserved)
P3.2	SPI slave TX enable, USCI_A0	SPI to host (reserved)
P3.3	UART TX,USCI_A0 or SPI slave in, master out	UART to host TX or SPI to host (reserved)
P3.4	UART RX, USCI_A0 or SPI slave out, master in	UART to host RX or SPI to host (reserved)
	,	
P1.0	PSE INT	Connect to PSE INT pin
P1.3	OC Alert	Connect to external current sensing circuit if not used, connect to 3.3 V
P1.5	Power supply 1	Connect to power supply 1 power good signal. In RPS mode, P1.5 must be connected to main power supply. If there is only one power supply, the power good signal must be connected to P1.5.
P1.6	Power supply 2	Connect to power supply 2 power good signal, if not used, connect to GND. In RPS mode, P1.6 must be connected to backup power supply
P1.7	Disable all ports	This is for hardware disable ports (reserved)
P5.0	RESET	PSE RESET Connect to PSE RESET pin
	P3.0 P3.1 P4.1 P4.2 P4.4 P4.5 P2.7 P3.2 P3.3 P3.4 P1.0 P1.3 P1.5	P3.0



www.ti.com System Overview

Table 2. MSP430 GPIO Pin Assignment (continued)

PIN NUMBER MSP430F5234 (48RGZ)	TERMINAL	FUNCTION	COMMENT
17	P1.4	OSS	PSE OSS Connect to PSE OSS pin
46	P6.0	Interrupt pin to host	
35	P4.6	BSL mode indication to host	MCU configures as output. If MCU is in BSL mode, output high. If in normal operation mode, output low.
48	P6.2	Guard-band indication	Need an external LED
47	P6.1	Selection between I2C and SPI, UART	Need to pullup or pulldown
PROGRAM DOWNLOAD A	ND DEBUG		
44	PJ.3	TCK	JTAG clock input
43	PJ.2	TMS	JTAG state control
42	PJ.1	TDI/TCLK	JTAG data input, TCLK input
41	PJ.0	TDO	JTAG data output
40		TEST/SBWTCK	Enable JTAG pins
45		RSTDVCC/SBWTDIO	External reset
EXTERNAL CRYSTAL			
7	P5.4	XTIN	External low frequency clock (use if needed)
8	P5.5	XTOUT	External low frequency clock (use if needed)

Pre-configure the host interface protocol through hardware as Table 3 shows.

Table 3. Host Interface Protocol

	P6.1	CS (P3.2)
I2C	high	Don't care
UART	low	low
SPI (CS ActiveLow)	low	high

2.3 Highlighted Products

2.3.1 TPS23881

The TPS2388x device is the main IC to handle PoE functions to deliver power to PDs through Ethernet cable.

The TPS23881 device is an 8-channel power sourcing equipment (PSE) controller engineered to insert power onto Ethernet cables in accordance with the IEEE 802.3bt (draft) standard. The eight individual power channels can be configured in any combination of 2-pair (1-channel) or 4-pair (2-channels) PoE ports. The PSE controller can detect PDs that have a valid signature, determine the power requirements of the devices according to their classification, and apply power.

Programmable SRAM enables in field firmware upgradability over I2C to ensure IEEE compliance and interoperability with the latest PoE enabled devices.

Dedicated per-port ADCs provide continuous port current monitoring and the ability to perform parallel classification measurements for faster port turn on times. A $\pm 2.5\%$ accurate programmable port power limit provides the ability to expand the maximum power sourced to 95 W without exceeding 100 W, and for non-standard applications, the power limit may be set as high as 125 W. The 200-m Ω current sense resistor and external FET architecture allows designs to balance size, efficiency, thermal, and solution cost requirements.

Port remapping and pin-to-pin compatibility with the TPS23880 and TPS2388 devices eases migration from previous generation PSE designs and enables interchangeable 2-layer PCB designs to accommodate different system PoE power configurations.



System Overview www.ti.com

2.3.2 MSP430F523x

The TI MSP family of ultra-low-power microcontrollers consists of several devices featuring different sets of peripherals targeted for various applications. The architecture, combined with extensive low-power modes, is optimized to achieve extended battery life in portable measurement applications. The device features a powerful 16-bit RISC CPU, 16-bit registers, and constant generators that contribute to maximum code efficiency. The digitally controlled oscillator (DCO) allows the device to wake up from low-power modes to active mode in 3.5 μ s (typical). The MSP430F524x series are microcontroller configurations with four 16-bit timers, a high-performance 10-bit ADC, two USCIs, a hardware multiplier, DMA, a comparator, and an RTC module with alarm capabilities. The MSP430F523x series microcontrollers include all of the peripherals of the MSP430F524x series except for the ADC.

MSP430F523x is the main controller to control PSE devices (TPS2388x) through the I2C bus and also communicates to host CPU through I2C or UART to receive configurations and report system status.

2.3.3 ISO1541

The ISO1541 bidirectional isolator is used to isolate I2C signals between PSE devices and the MCU.

The ISO1540 and ISO1541 devices are low-power, bidirectional isolators that are compatible with I2C interfaces. These devices have logic input and output buffers that are separated by Tl's *Capacitive Isolation* technology using a silicon dioxide (SiO2) barrier. When used with isolated power supplies, these devices block high voltages, isolate grounds, and prevent noise currents from entering the local ground and interfering with or damaging sensitive circuitry.

2.3.4 ISO7731

The ISO7731 digital isolator is used to isolate control signals (OSS, RESET, INT) between MSP430 and PSE devices.

The ISO773x devices are high-performance, triple channel digital isolators with 5000 V_{RMS} (DW package) and 3000 V_{RMS} (DBQ package) isolation ratings per UL 1577.

This family of devices has reinforced insulation ratings according to VDE, CSA, TUV, and CQC.

The ISO773x family of devices provides high electromagnetic immunity and low emissions at low power consumption, while isolating CMOS or LVCMOS digital I/Os. Each isolation channel has a logic input and output buffer separated by a silicon dioxide (SiO2) insulation barrier. This device comes with enable pins which can be used to put the respective outputs in high impedance for multi-master driving applications and to reduce power consumption. The ISO7730 device has all three channels in the same direction and the ISO7731 device has two forward and one reverse-direction channel. If the input power or signal is lost, the default output is high for devices without suffix F and low for devices with suffix F. See the device Functional Modes section for further details.

Used in conjunction with isolated power supplies, this device helps prevent noise currents on a data bus or other circuits from entering the local ground and interfering with or damaging sensitive circuitry. Through innovative chip design and layout techniques, electromagnetic compatibility of the ISO773x device is significantly enhanced to ease system-level ESD, EFT, surge, and emissions compliance.

2.3.5 CSD19538

This 100-V, 49-m Ω , SON 3.3-mm × 3.3-mm NexFETTM power MOSFET is designed to minimize conduction losses and reduce the board footprint in PoE applications.



www.ti.com System Overview

2.3.6 LM5017

The LM5017 device is used to generate 3.3 V to supply PSE devices.

The LM5017 is a 100-V, 600-mA synchronous step-down regulator with integrated high-side and low-side MOSFETs. The constant on-time (COT) control scheme employed in the LM5017 device requires no loop compensation, provides excellent transient response, and enables very high step-down ratios. The on-time varies inversely with the input voltage resulting in nearly constant frequency over the input voltage range. A high-voltage startup regulator provides bias power for internal operation of the IC and for integrated gate drivers. A peak current limit circuit protects against overload conditions. The undervoltage lockout (UVLO) circuit allows the input undervoltage threshold and hysteresis to be independently programmed. Other protection features include thermal shutdown and bias supply undervoltage lockout (VCC UVLO).

2.3.7 LM5020

The LM5020 device is used to generate isolated LM5020 to supply MSP430 and isolators.

The LM5020 high-voltage pulse-width modulation (PWM) controller contains all of the features needed to implement single-ended primary power converter topologies. Output voltage regulation is based on current-mode control, which eases the design of loop compensation while providing inherent line feed-forward. The LM5020 device includes a high-voltage start-up regulator that operates over a wide-input range up to 100 V. The PWM controller is designed for high-speed capability including an oscillator frequency range to 1 MHz and total propagation delays less than 100 ns. Additional features include an error amplifier, precision reference, line undervoltage lockout, cycle-by-cycle current limit, slope compensation, soft start, oscillator synchronization capability and thermal shutdown.

2.3.8 LM5050

The LM5050 device is used to support 2 power supplies in the system to work in backup mode.

The LM5050-1 and LM5050-1-Q1 high-side ORing FET controller operates in conjunction with an external MOSFET as an ideal diode rectifier when connected in series with a power source. This ORing controller allows MOSFETs to replace diode rectifiers in power distribution networks thus reducing both power loss and voltage drops.

The LM5050-1 and LM5050-1-Q1 controllers provide charge pump MOSFET gate drive for an external N-channel MOSFET and a fast response comparator to turn off the FET when current flows in the reverse direction. The LM5050-1 and LM5050-1-Q1 devices can connect power supplies ranging from 5 V to 75 V and can withstand transients up to 100 V.

2.3.9 INA240

The INA240 amplifier is used to measure the total current from the input to support fast shutdown in an event of load step change.

The INA240 device is a voltage-output, current-sense amplifier with enhanced PWM rejection that can sense drops across shunt resistors over a wide common-mode voltage range from -4~V to 80~V, independent of the supply voltage. The negative common-mode voltage allows the device to operate below ground, accommodating the flyback period of typical solenoid applications. Enhanced PWM rejection provides high levels of suppression for large common-mode transients $(\Delta V/\Delta t)$ in systems that use PWM signals (such as motor drives and solenoid control systems). This feature allows for accurate current measurements without large transients and associated recovery ripple on the output voltage. This device operates from a single 2.7-V to 5.5-V power supply, drawing a maximum of 2.4 mA of supply current. Four fixed gains are available: 20~V/V, 50~V/V, 100~V/V, and 200~V/V. The low offset of the zero-drift architecture enables current sensing with maximum drops across the shunt as low as 10-mV full-scale.



2.3.10 REF3425

The REF3425 device is used to provide a threshold to output the INA240 and generate a signal to MCU for overcurrent alert.

The REF34xx device is a low temperature drift (6 ppm/°C), low-power, high-precision CMOS voltage reference, featuring $\pm 0.05\%$ initial accuracy, low operating current with power consumption less than 95 μ A. This device also offers very low output noise of 3.8 μ Vp-p/V, which enables its ability to maintain high signal integrity with high-resolution data converters in noise critical systems. With a small SOT-23 package, the REF34xx offers enhanced specifications and pin-to-pin replacement for MAX607x and ADR34xx. The REF34xx family is compatible to most of the ADC and DAC such as the ADS1287, ADUCM360, and ADS1112 devices. Stability and system reliability are further improved by the low output-voltage hysteresis of the device and low long-term output voltage drift. Furthermore, the small size and low operating current of the devices (95 μ A) can benefit portable and battery-powered applications.

2.3.11 TPS3890

The TPS3890 device is used to monitor the existence of the power supply and generate power good signal to MCU. The MCU can adjust the total power budget of the system.

The TPS3890 device is a precision voltage supervisor with low-quiescent current that monitors system voltages as low as 1.15 V, asserting an open-drain RESET signal when the SENSE voltage drops below a preset threshold or when the manual reset (MR) pin drops to a logic low. The RESET output remains low for the user-adjustable delay time after the SENSE voltage and manual reset (MR) return above the respective thresholds. The TPS3890 family uses a precision reference to achieve 1% threshold accuracy. The reset delay time can be user-adjusted between 40 μs and 30 s by connecting the CT pin to an external capacitor. The TPS3890 device has a very low quiescent current of 2.1 μA and is available in a small 1.5-mm \times 1.5-mm package, making the device well-suited for battery-powered and space-constrained applications.

3 Hardware, Software, Testing Requirement and Test Result

3.1 Required Hardware and Software

3.1.1 Hardware

The following hardware is required to get started with the reference design:

- PSEMTHR24EVM-081: motherboard for 24 port PoE PSE applications (sold separately)
- PSEMCUDAUEVM-082: MSP430 daughtercard for 24 Port PoE PSE applications (sold separately)
- TPS23881EVM-083: TPS23881 daughtercard for 24-port Type 3 and Type 4 PSE PoE PSE applications (sold separately)
- USB2ANY interface adapter: used with PSE system firmware GUI for I2C/UART interaction with PSEMCUDAU-082 daughtercard (sold separately)
- MSP-FET programmer: used with the Uniflash GUI for programming the MSP430 device

3.1.2 Software

- FirmPSE code image (request access to the code image through the TIDA-050026-23881 folder or the PSEMCUDAUEVM-082 tool folder)
- FirmPSE GUI (request access to the GUI through the TIDA-050026-23881 folder or the PSEMCUDAUEVM-082 tool folder)



3.2 Testing and Results

3.2.1 **Test Setup**

3.2.1.1 Hardware Setup

Figure 2 shows the hardware test setup of the ecosystem.

Figure 2. Ecosystem Setup Power supply 2 Power supply 1 J3 PSEMTHR24EVM-081 TPS23881EVM-083 PSEMCUDAUEVM-082 J15 J55 ♠ Ethernet Ethernet Ribbon Ribbon Cable Cable Type 3/4 PDs Type 3/4 PDs USB2ANY MSP-FET РС

NOTE: A 30-pin ribbon cable is required to enable the full features of PSE system firmware GUI.



3.2.1.2 LED, Test Point, Jumper and Connector Settings

3.2.1.2.1 EVM LEDs

Table 4 lists the EVM LEDs and their descriptions.

Table 4. EVM LEDs

LED	COLOR	DESCRIPTION
PSEMTHR24EVM-081		
J15, J55	Green, Yellow	There is one green and yellow LED on each RJ45 port
PSEMCUDAUEVM-082		
D1	Green	The total power consumption is within the pre-configured guardband

3.2.1.2.2 EVM Test Points

Table 5 lists the EVM test points.

Table 5. EVM Test Points

TP	LABEL	DESCRIPTION
PSEMTHR24EVM-081		
TP1	55VDC	VPWR
TP2	GND	VPWR ground
TP3	OC-ALERT	System over current alert signal
TP4	SDA	I2C data
TP5	SCL	I2C clock
TP6	PG1	Power good signal for power supply #1
TP7	PG2	Power good signal for power supply #2
TP8	PSE_3.3V	3.3 V for PSE devices
TP9	GND	PSE_3.3V ground
TP10	3.3V_ISO	Isolated 3.3 V for MSP430
TP11	3.3V	3.3 V for debug
TPS12, TP13	GND_ISO	3.3V_ISO ground
TP14	OSS	OSS signal from MCU to PSE
TPS23881EM-083		
TP1	VPWR	VPWR
TP2	PSE_3.3	3.3 V for PSE devices
TP3, TP4, TP14, TP18	GND	VPWR and PSE_3.3V ground
TP5	RESET	Reset signal from MCU
TP6	OSS	OSS signal from MCU
TP7	INT	INT signal to MCU
TP8	SCL	I2C clock from MCU
TP9	SDA	I2C data from and to MCU
TP10	3.3V_ISO	Isolated 3.3 V
TP11	PSE_RST	Reset signal to PSE
TP12	PSE_OSS	OSS signal to PSE
TP13	PSE_INT	INT signal from PSE
TP15	GND_ISO	3.3V_ISO ground
TP16	PSE_SDA	I2C data from or to PSE
TP17	PSE_SCL	I2C clock to PSE



3.2.1.2.3 **EVM Jumpers**

Table 6 lists the EVM test jumpers and their descriptions.

Table 6. EVM Test Jumpers

JUMPER	DEFAULT PIN POSITION	DESCRIPTION
PSEMTHR24EVM-081		
J13	1-2	3.3 V comes from PSE daughtercard
J14	1-2	Connect 3.3V_ISO to supply the circuit
J17, J22, J38, J43, J19, J23, J32, J28, J52, J47, J31, J26	1-2	Enable port LED
J45, J42, J24, J21, J44, J49, J53, J30, J33, J51, J54	1-2	Enable port LED
J57, J62, J78, J83, J59, J63, J72, J68, J92, J87, J71, J66	1-2	Enable port LED
J85, J82, J64, J61, J84, J80, J89, J93, J70, J91, J94	1-2	Enable port LED

3.2.1.2.4 EVM Input and Output Connectors

Table 7 lists the EVM input and output connectors.

Table 7. EVM Input and Output Connectors

CONNECTOR	DESCRIPTION		
PSEMTHR24EVM-081			
J1, J3	DC power supply input (44–57 V VDC, 41 A)		
J2, J4, J6, J7	Edge connector for DC bus when connecting 2 boards together		
J5	Power to PSE daughtercard		
J8, J9	Edge connector for PSE signals (I2C, OSS, RESET and INT) when connecting 2 boards together		
J10	Connector to USB2ANY for direct I2C access to PSE devices (for debug purpose only)		
J11	Connectors to PSE daughter for PSE signals (I2C, OSS, RESET and INT)		
J12	Connectors to MSP430 daughter for PSE signals (I2C, OSS, RESET and INT), system level signals (OC-ALERT, PG) and isolated 3.3 V		
J15, J55	PSE ports magjacks		
J34, J35, J36, J74, J75, J76	PSE port connector to PSE daughtercard		
J95, J96	For MSP430 daughtercard mechanical mounting purpose		
TPS23881EM-083			
J1	Pair with J5 on motherboard		
J4	Pair with J11 on motherboard		
J5	Pair with J34, J35, J36, J74, J75, J76 on motherboard		
PSEMCUDAUEVM-082			
J1	JTAG connector		
J3, J7, J8, J9	Extended GPIO access		
J11	Pair with J12 on motherboard		
J12, J13, J14	USB2ANY connector (30 pin)		
J17, J18	For MSP430 daughtercard mechanical mounting purpose		



3.2.1.3 System Firmware GUI Setup

3.2.1.3.1 PSE System Firmware GUI Installation

TI's PSE system firmware GUI is used with the PSE system EVM kit (PSEMTHR24EVM-081, PSEMCUDAUEVM-082, TPS23881EVM-083) to configure the system, generate the code image and flash to MSP430 device. Download the PSE system firmware GUI from the TIDA-050026-23881 folder or the PSEMCUDAUEVM-082 tool folder.

3.2.1.3.2 PSE System Firmware GUI Operation

Start the PSE system firmware GUI by double clicking the GUI icon and clicking the start button. A window similar to Figure 3 comes up. Offline mode is selected by default.


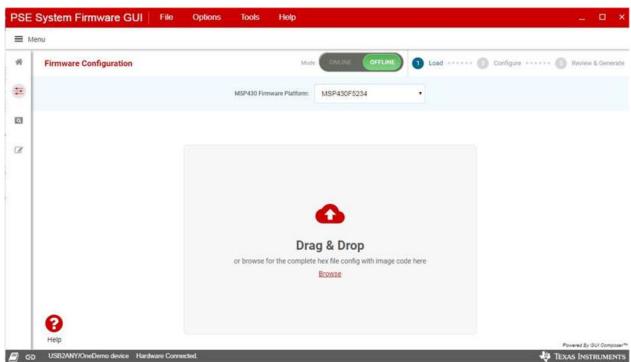


Figure 3. GUI Startup

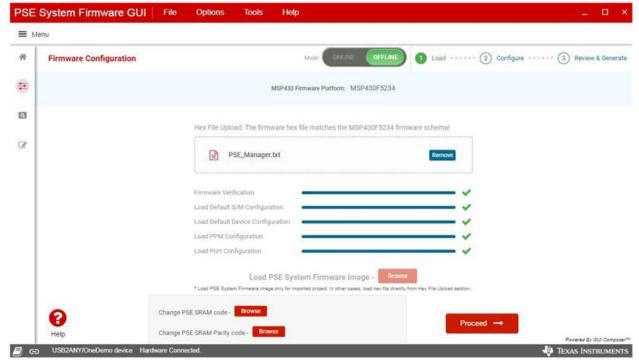

Select the MSP430 device you want to start with and then load the PSE system firmware code image (request from the TIDA-050026-23881 folder or the PSEMCUDAUEVM-082 tool folder). Once finished, click *Proceed* to go to the configuration page.

Figure 4. GUI Device Selection and Image Load



The configurations are split into 4 sections: system configuration, PPM (Port Power Management) configuration, device configuration, and port configuration.

The system configuration is applied to the whole system. This tab is always available on the right side of the GUI. The following parameters can be configured through the system configuration tab:

- Legacy detection functions
 - Legacy devices released prior to the PoE standard can be powered through the Ethernet cable. The PSE system firmware detects these legacy PDs and powers on with protection.
- Use of external sensing circuit
 - The external sensing circuit is used to measure the total power consumption of the system. Once the current exceeds the power budget, the MCU shuts down low priority ports. This increases the system response to the load step change.
- System boot-up setting
 - 1. Turn on the PSE port as soon as the power is up.
 - 2. Turn on the PSE port after the PoE enable command is sent from the host
- · Port overload retry mode
 - 1. Re-enable immediately: after overload happens, the port is re-enabled immediately. If the overload still presents, it will try at most 5 times and shuts down the port if the overload is not removed within 5 retries. The port is re-enabled after the PD is removed from the port and reconnects to the port.
 - 2. Re-enable after PD is disconnected and connected: after overload happens, the port is disabled immediately and is re-enabled after the PD is removed from the port and reconnects to the port.
 - 3. Timer controlled: the port is re-enabled immediately after overload happens. The port keeps retrying for a period (controller by timer) and is disabled after the timer expires. The port is reenabled after the PD is removed from the port and reconnects to the port.




- OSS signal source (from MCU or CPLD):In a multi-power supply system, when one power supply has
 faults and the remaining power supply is not able to supply the current power consumption, turn off low
 priority ports to protect the remaining power supply. The OSS function of the PSE is used to fast
 shutdown the low priority ports. There are 2 sources to generate the OSS signal:
 - 1. MSP430 generates the OSS signal
 - 2. CPLD generates the OSS signal
- Interrupt mask

The interrupt mask in Figure 5 can be configured to enable interrupt events to notify the host through the MSP430 P6.0.

Figure 5. GUI System Configuration and PPM Configuration

GUI | File Options Tools Help

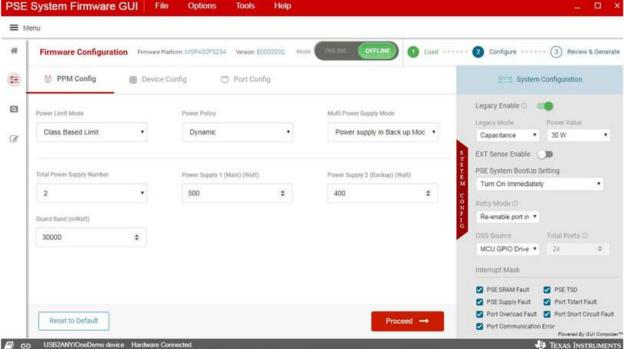

PPM configuration is applied to the port power management mechanism. The following parameters can be configured through the PPM configuration tab:

- Power limit mode: class limit mode and port limit mode
 - Class limit mode: in class limit mode, the port power is limited by the class level of the PD. For example, if the PD is class 8, the port power limit (PCUT) is set to 90 W.
 - Port limit mode: in port limit mode, the port power is limited by the host. The host should set port power limit before the port is powered on.
- Power policy:static and dynamic mode
 - Static mode: in static mode, the port power allocation is set to port power limit. So in class limit mode, port power allocation is class level power of the PD and in port limit mode, the port power allocation is the port power limit configured from the host.
 - Dynamic mode: in dynamic mode, the port power allocation equals to the actual consumed power of the port. It allocates the unused power of the port to other ports.



- Multi-power supply mode: RPS and sharing mode:
 - Redundant power supply (RPS) mode: in RPS mode, the total power budget equals to the power budget of the main power supply when both main power supply and backup power supply are connected. The total power budget equals to backup the power budget of the power supply when the main power supply is disconnected.
 - Sharing power supply mode: in sharing mode, the total power budget equals to the sum of the
 power budget of the two power supplies when both power supplies are connected. The total power
 budget equals to the remaining power budget of the power supply if one of the power supplies is
 disconnected.
- Total number of power supplies and the power budget of each power supply. If there is only one
 power supply, the power good signal must be connected to P1.5.
- Power guard band: when the total allocated power < total power budget guard band, there is no more low priority ports to be turned on and the guard band LED will turn on.

Device configuration is mainly used to configure the mapping between the PSE device channels and the logical RJ45 ports. When mapping a 4-pair port, only channels within the same quad (channel 1–4 or channel 5–8) can be mapped to one 4-pair port.

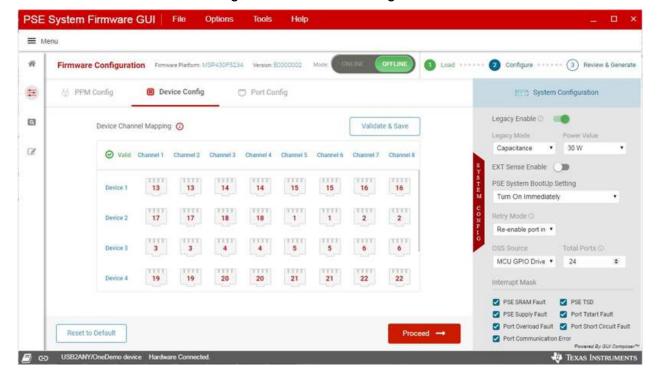


Figure 6. GUI Device Configuration

Reset to Default

USB2ANY/OneDemo device Hardware Connect



The Port Configuration is applied to the port by port settings, such as port PoE enable and disable, port priority, and port power limit (only in port limit mode).

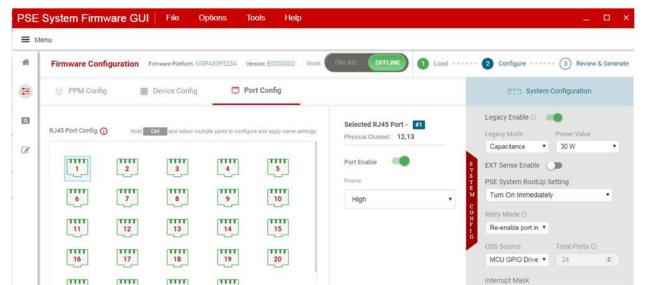


Figure 7. GUI Port Configuration

Once everything is configured, click the Proceed button. The summary page shows all the configurations being set compared to the factory default configurations. Once everything is verified, you can generate the hex file or flash the code to the MSP430 device directly.

Proceed -

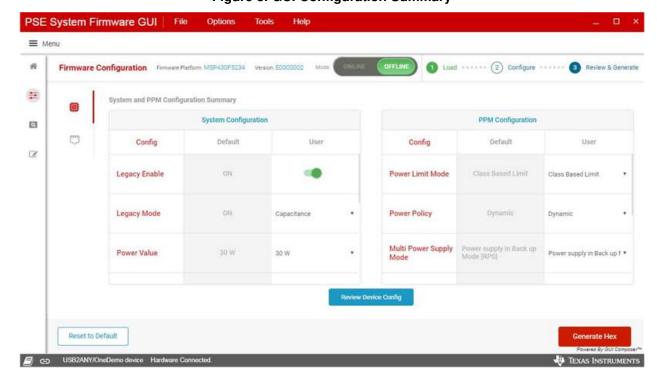


Figure 8. GUI Configuration Summary

PSE SRAM Fault PSE TSD PSE Supply Fault

Port Overload Fault Port Short Circuit Fault

Port Communication Error
Powered By GUI Com

Port Tstart Fault

TEXAS INSTRUMENTS



Once configurations are reviewed, the GUI can generate the default code image and program the device directly through **MSP-FET**.

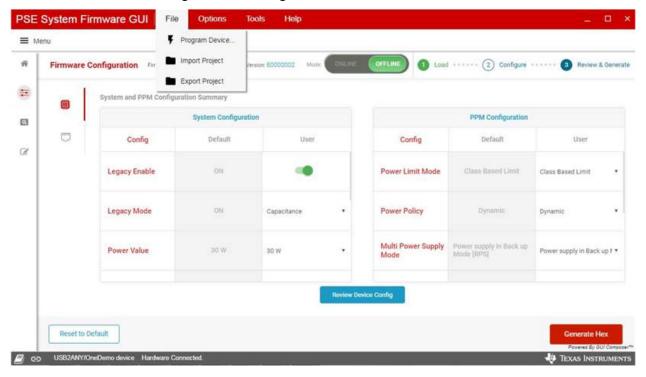


Figure 9. GUI Program Device and Generate Hex

Once the code is successfully flashed to the MSP430 MCU, the system is up and running. The MSP-FET can be disconnected from the laptop or PC. Connect the USB2ANY (with 30-pin ribbon cable) to a laptop or PC and the GUI is in online mode after selecting the host interface protocol.

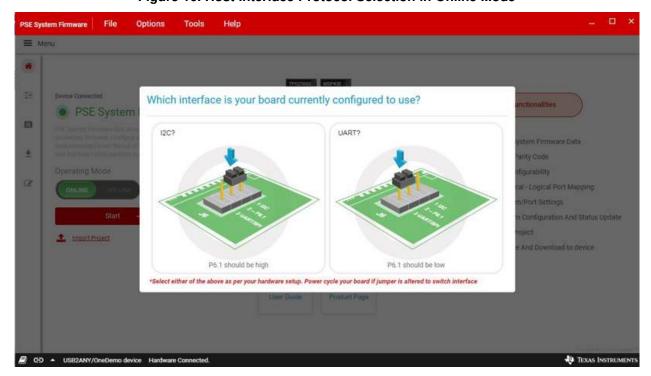


Figure 10. Host Interface Protocol Selection in Online Mode



Once the device is connected to the GUI, real time changes can be made on the configuration page and status page shows the real time system status. The status page shows the system, device, and port real-time status. The user can also change the system configuration in the configuration page: each change is converted to a host command to the MSP430 MCU. The user can also press the *Save Configuration* button to save the current configuration as the default setting.

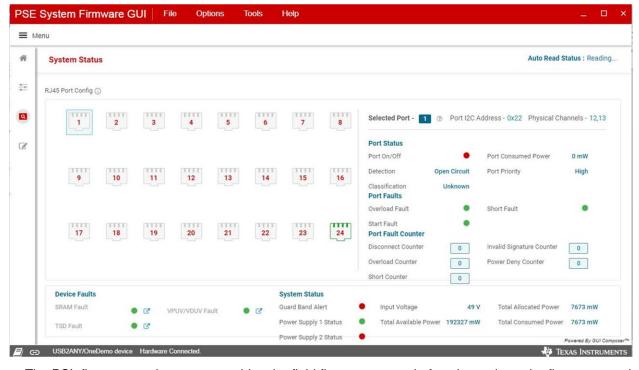


Figure 11. GUI Status Page

The BSL firmware update page provides the field firmware upgrade functions where the firmware can be upgraded through the same I2C or UART port as the normal communication. This is beneficial to firmware upgrade after the product is released to customers.



Tools Options Help PSE System Firmware ■ Menu 4 **BSL Firmware Update** ① Upload the Firmware File and Click 'Update System Software' Q * (i) Please uncheck if you want to exclude any of the below two steps ✓ Enable BSL Mode(Step 1) 8 ✓ Verify Loaded Program(Step 5) Drag & Drop or browse for the complete hex file config with image code here Browse Entered BSL Password Mass Erase

Figure 12. BSL Firmware Update Page


Before using the BSL page to update the MSP430 firmware, BSL code must be flashed to the MSP430 MCU if it is not flashed. Download Uniflash from ti.com and use it to flash the BSL code with the following steps:

1. Select the MCU device to MSP430F5234

USB2ANY/OneDemo device Hardware Conn

Verified

Figure 13. MCU Device Selection Page

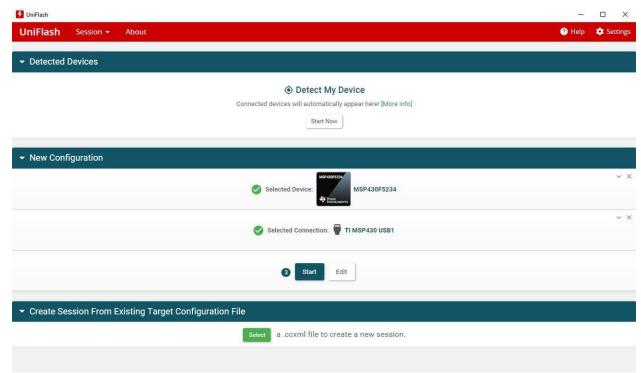


₩ TEXAS INSTRUMENTS




2. Configure the flash section.

Figure 14. Configure Settings and Utilities Page

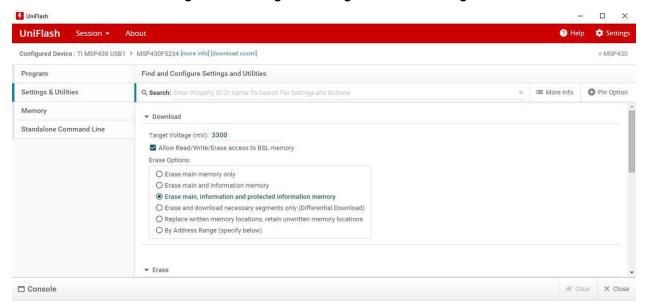

3. Load BSL code and flash to the MSP430 MCU.

Figure 15. Select and Load Images Page

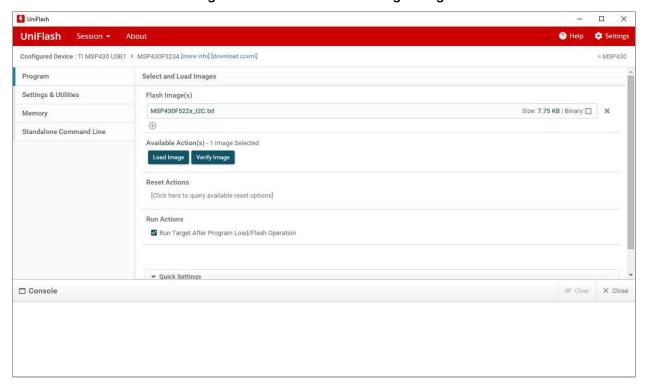



4. In the debug page, user can read and write raw data to MSP430 following host interface protocol and to each PSE device's registers by providing I2C address and register number. The password is "C430".

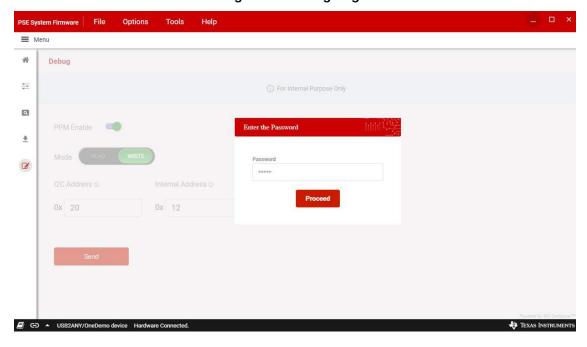


Figure 16. Debug Page

3.2.2 Test Results

The IEEE 802.3bt compliance test suite is not available now. The test report will be added once available.



Design Files www.ti.com

4 Design Files

4.1 Schematic

To download the schematics, see the design files at TIDA-050026-23881.

4.2 Bill of Materials

To download the bill of materials (BOM), see the design files at TIDA-050026-23881.

4.3 PCB Layout Recommendations

KSENSA is shared between SEN1 and SEN2, KSENSB is shared between SEN3 and SEN4, KSENSEC is shared between SEN5 and SEN6, KSENSED is shared between SEN7 and SEN8. To optimize the accuracy of the measurement, the PCB layout must be done carefully to minimize the impact of PCB trace resistance. For an example, see the *Layout* section of the *TPS23881 Type-4 4-Pair 8-Channel PoE PSE Controller With SRAM and 200 m* Ω R_{SENSE} data sheet.

4.3.1 Layout Prints

To download the layer plots, see the design files at TIDA-050026-23881.

4.4 Altium Project

To download the Altium project files, see the design files at TIDA-050026-23881.

4.5 Gerber Files

To download the Gerber files, see the design files at TIDA-050026-23881.

4.6 Assembly Drawings

To download the assembly drawings, see the design files at TIDA-050026-23881.

5 Software Files

To download the software files, see the design files at TIDA-050026-23881.

6 Related Documentation

- 1. Texas Instruments, TPS23881 High-Power, 8-Channel, Power-Over-Ethernet PSE With 200-mΩ R_{SENSE} Data Sheet
- 2. Texas Instruments, TPS23882 Type-3, 30W, 2-pair, PSE daughter card for 24-port PSE systems

6.1 Trademarks

E2E, NexFET are trademarks of Texas Instruments.

All other trademarks are the property of their respective owners.



www.ti.com Revision History

Revision History

Cł	nanges from Original (May 2019) to A Revision	Page	ļ
•	The SLVUBN3 is completely reworked in revision A.	1	•

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2019, Texas Instruments Incorporated