

# ISL81601DEMO1Z User's Manual: Demonstration Board

User's Manual

Industrial Analog and Power

Rev.0.00 Oct 2018

# RENESAS

# **USER'S MANUAL**

ISL81601DEMO1Z

Demonstration Board

UG176 Rev.0.00 Oct 12, 2018

# 1. Overview

The ISL81601DEMO1Z demonstration board (shown in Figure 8 on page 9) features the <u>ISL81601</u>, a 60V high voltage synchronous buck-boost controller that offers external soft-start, independent enable functions, and integrates UV/OV/OC/OT protection. Programmable switching frequency ranging from 100kHz to 600kHz helps to optimize inductor size while the strong gate driver delivers up to 20A for the buck-boost output.

## 1.1 Key Features

- Wide input range: 32V to 60V
- Bidirectional operation
- High light-load efficiency in pulse skipping DEM operation
- Programmable soft-start
- Optional DEM/PWM operation
- Optional CC/HICCUP OCP protection
- Supports prebias output with soft-start
- PGOOD indicator
- OVP, OTP, and UVP protection
- Parallelable operation

# 1.2 Specifications

The ISL81601DEMO1Z demonstration board is designed for high current applications. The current rating of the ISL81601DEMO1Z is limited by the FETs and inductor selected. The ISL81601DEMO1Z electrical ratings are shown in <u>Table 1</u>.

Parameter	Rating
Input Voltage	32V to 60V
Switching Frequency	200kHz
Output Voltage	48V
Output Current	10A
OCP Set Point	Minimum 11A at ambient room temperature

Table 1. Electrical Rating

# 1.3 Ordering Information

Part Number	Description
ISL81601DEMO1Z	Parallelable high voltage buck-boost controller demonstration board

### 1.4 Related Literature

For a full list of related documents, visit our website:

• ISL81601 product page









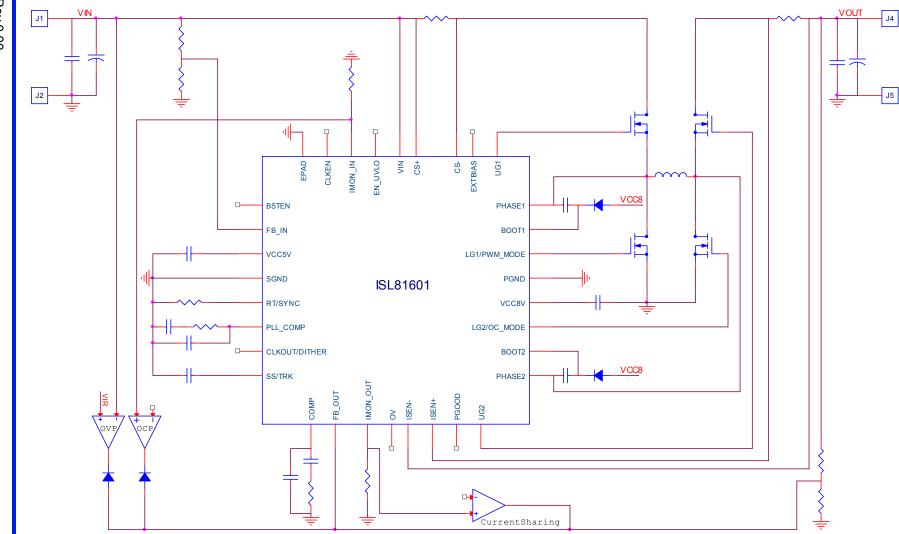


Figure 1. ISL81601DEMO1Z Block Diagram

UG176 Rev.0.00 Oct 12, 2018

RENESAS

# 2. Functional Description

The ISL81601DEMO1Z is used to evaluate the performance of the ISL81601 QFN IC. The board provides an easy and complete demonstration of all the IC and board functions.

As shown in <u>Figure 7 on page 7</u>, 32V to 60V  $V_{IN}$  is supplied to  $J_1$  (+) and  $J_2$  (-). The regulated 48V output on  $J_4$  (+) and  $J_5$  (-) can supply up to 10A to the load. Due to the high power efficiency, the demonstration board can run at 5A continuously without airflow at room temperature ambient conditions.

Test points TP<sub>1</sub> through TP<sub>28</sub> provide easy access to the IC pin and external signal injection terminals.

As shown in <u>Table 3 on page 7</u>, connector  $J_8$  provides selection of either Forced PWM mode (shorting Pin 1 and Pin 2) or DEM mode (shorting Pin 2 and Pin 3). Connector  $J_9$  provides selection of either constant current limit (shorting Pin 1 and Pin 2) or HICCUP OCP (shorting Pin 2 and Pin 3). Connector  $J_3$  provides an option to disable the converter by shorting its Pin 1 and Pin 2.

## 2.1 Recommended Testing Equipment

The following materials are recommended for testing:

- 0V to 60V power supply with at least 15A source current capability
- Electronic loads capable of sinking current up to 15A
- Digital Multimeters (DMMs)
- 100MHz quad-trace oscilloscope

## 2.2 Operating Range

The input voltage range is from 32V to 60V for an output voltage of 48V. If the output voltage is set to a lower value, the minimum  $V_{IN}$  can be reset to a lower value by changing the ratio of  $R_2$  and  $R_3$ . The minimum EN threshold that  $V_{IN}$  can be set to is 4.5V.

The rated load current is 10A with the OCP point set at minimum 11A at ambient room temperature conditions. The operating temperature range of this board is from -40°C to +85°C. Note that airflow is needed for higher temperature ambient conditions.



### 2.3 Parallel Operation

The ISL81601DEMO1Z demonstration board can operate in parallel, in a daisy chain setup.

<u>Figure 2</u> shows the wiring of two units in parallel and <u>Figure 3</u> shows three units in parallel. The phase shift between the units can be set by  $J_6$  and  $J_7$ . <u>Table 2</u> shows the combination.

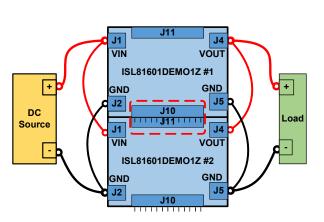


Figure 2. Setup for Two Units in Parallel

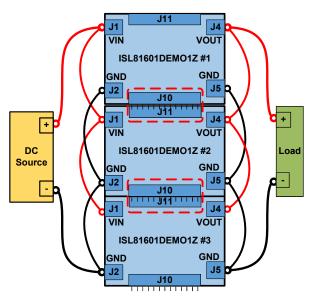


Figure 3. Setup for Three Units in Parallel

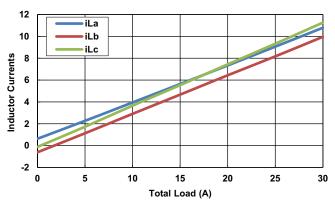


Figure 4. Current Sharing Among Three Units

Table 2. Set Phase Shift for Interleaving					
	CLK Lag RT by (°)	90	60	180	120
J <sub>7</sub>	FBI	VC5 (1)	VC5 (1)	GND (Active)	GND (Active)
J <sub>6</sub>	IIN_B	Open (Active)	Shorted (1)	Open (Active)	Shorted (1)



### 2.4 Bidirectional Operation

Refer to Figure 5 for proper setup. Float the FBI pin  $(J_7)$  and set the mode to PWM before powering on the board. The rated voltage of the super capacitor must be higher than 48V.

- (1) Adjust the input voltage higher than 36V. Switch on the input power source.
- (2) Switch off the input power source after the super capacitor is fully charged.

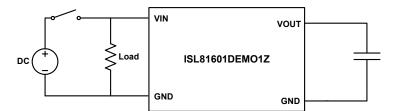


Figure 5. Proper Set-Up for Bidirectional Operation



### 2.5 Quick Test Guide

- (1) Jumper J<sub>8</sub> provides the option to select PWM or DEM. Jumper J<sub>9</sub> provides the option to select Constant current limit or HICCUP. Refer to <u>Table 3</u> for the operating options. Ensure that the circuit is correctly connected to the supply and electronic loads prior to applying any power. Refer to <u>Figure 7</u> for proper setup.
- (2) Turn on the power supply.
- (3) Adjust input voltage  $V_{IN}$  within the specified range and observe the output voltage. The output voltage variation should be within 3%.
- (4) Adjust the load current within the specified range and observe the output voltage. The output voltage variation should be within 3%.
- (5) Use an oscilloscope to observe output voltage ripple and phase node ringing. For accurate measurement, refer to Figure 6 for proper test setup.

Jumper	Position	Function
3	3 EN-GND Disable output	
	EN Floating	Enable output
6	I <sub>IN</sub> Floating	Enable input current limit
	I <sub>IN</sub> -VCC5	Disable input current limit
7	FBI-GND	Disable V <sub>IN</sub> limit
	FBI Floating	Enable V <sub>IN</sub> limit
8	Pin 1-2	PWM
	Pin 2-3	DEM
9	Pin 1-2	Constant current limit
	Pin 2-3	HICCUP

#### Table 3. Operating Options

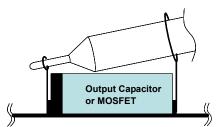


Figure 6. Proper Probe Set-Up to Measure Output Ripple and Phase Node Ringing

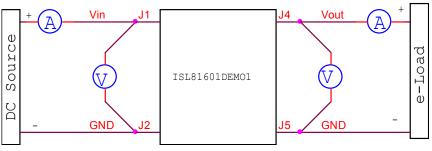


Figure 7. Proper Test Setup



# 3. PCB Layout Guidelines

Careful attention to layout requirements is necessary for successful implementation of an ISL81601 based DC/DC converter. The ISL81601 switches at a very high frequency; therefore the switching times are very short. At these switching frequencies, even the shortest trace has significant impedance. The peak gate drive current also rises significantly in an extremely short time. Transition speed of the current from one device to another causes voltage spikes across the interconnecting impedances and parasitic circuit elements. These voltage spikes can degrade efficiency, generate EMI, and increase device voltage stress and ringing. Careful component selection and proper PC board layout minimizes the magnitude of these voltage spikes.

Three sets of components are critical when using the ISL81601 DC/DC converter:

- Controller
- Switching power components
- Small signal components

The switching power components are the most critical to the layout because they switch a large amount of energy, which tends to generate a large amount of noise. The critical small signal components are those connected to sensitive nodes or those supplying critical bias currents. A multilayer printed circuit board is recommended.

Complete the following steps to optimize the PCB layout.

- (1) The input capacitors, buck FETs, inductor, boost FETs, and output capacitor should be placed first. Isolate these power components on dedicated areas of the board with their ground terminals adjacent to one another. Place the input and output high frequency decoupling ceramic capacitors very close to the MOSFETs.
- (2) If signal components and the IC are placed separately from the power train, it is recommended to use full ground planes in the internal layers with shared SGND and PGND to simplify the layout design. Otherwise, use separate ground planes for the power ground and the small signal ground. Connect the SGND and PGND together close to the IC. DO NOT connect them together anywhere else.
- (3) The loop formed by the input capacitor, the buck top FET, and the buck bottom FET must be kept as small as possible. Also, the loop formed by the output capacitor, the boost top FET, and the boost bottom FET must also be kept as small as possible.
- (4) Ensure the current paths from the input capacitor to the buck FETs, the power inductor, the boost FETs, and the output capacitor are as short as possible with maximum allowable trace widths.
- (5) Place the PWM controller IC close to the lower FETs. The low-side FETs gate drive connections should be short and wide. The IC should be placed over a quiet ground area. Avoid switching ground loop currents in this area.
- (6) Place the VDD bypass capacitor very close to the VDD pin of the IC and connect its ground end to the PGND pin. Connect the PGND pin to the ground plane by a via. Do not connect the PGND pin directly to the SGND EPAD.
- (7) Place the gate drive components (BOOT diodes and BOOT capacitors) together near the controller IC.
- (8) Place the output capacitors as close to the load as possible. Use short, wide copper regions to connect output capacitors to the load to avoid inductance and resistance.
- (9) Use copper filled polygons or wide, short traces to connect the junction of the buck or boost upper FET, buck or boost lower FET, and output inductor. Keep the buck and boost PHASE nodes connection to the IC short. DO NOT unnecessarily oversize the copper islands for the PHASE nodes. Because the phase nodes are subjected to very high dv/dt voltages, the stray capacitor formed between these islands and the surrounding circuitry tend to couple switching noise.
- (10) Route all high speed switching nodes away from the control circuitry.
- (11) Create a separate small analog ground plane near the IC. Connect the SGND pin to this plane. All small signal grounding paths including feedback resistors, current monitoring resistors and capacitors, soft-starting capacitors, loop compensation capacitors and resistors, and EN pull-down resistors should be connected to this SGND plane.
- (12) Use a pair of traces with minimum loop for the input or output current sensing connection.
- (13) Ensure the feedback connection to the output capacitor is short and direct.



# 3.1 ISL81601DEMO1Z Demonstration Board



Figure 8. ISL81601DEMO1Z Demonstration Board (Top)


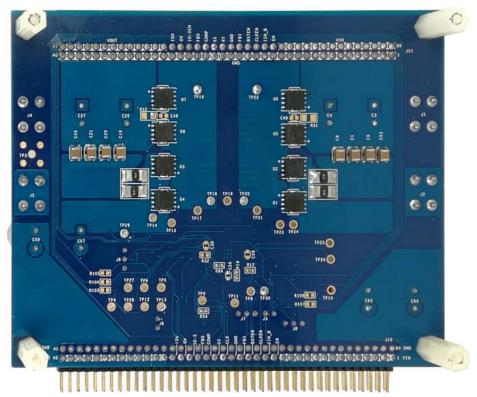


Figure 9. ISL81601DEMO1Z Demonstration Board (Bottom)

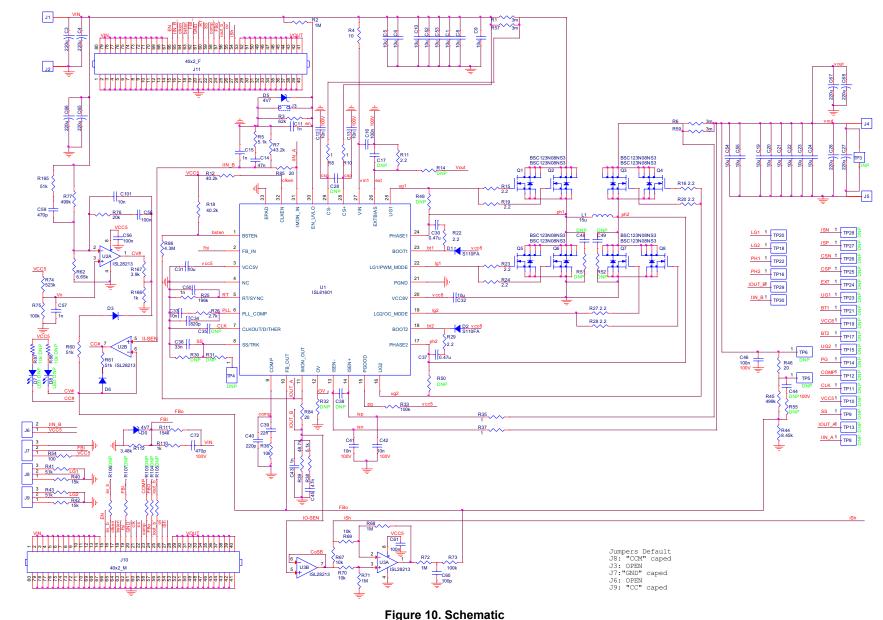





ω

ISL81601DEMO1Z

UG176 Rev.0.00 Oct 12, 2018

# 3.3 Bill of Materials

Qty	Reference Designator	Description	Manufacturer	Manufacturer Part
2	C31, C32	CAP, SMD, 0805, 10µF, 16V, 10%, X7S	MURATA	GRM21BC71C106KE11L
16	C1, C5, C6, C8-C10, C19-C24, C52-C55	CAP, SMD, 1210, 10µF, 100V, 10%, X7S	MURATA	GRM32EC72A106KE05L
1	C60	CAP, SMD, 0603, 100pF, 50V, 10%, X7R	KEMET	C0603C101K5RACTU
3	C11, C15, C43	CAP, SMD, 0603, 1000pF, 50V, 10%, X7R	AVX	06035C102KAT2A
2	C50, C57	CAP, SMD, 0603, 1000pF, 50V, 10%, X7R	AVX	06035C102KAT2A
5	C12, C13, C41, C42, C101	CAP, SMD, 0603, 0.01µF, 100V, 10%, X7R	KEMET	C0603C103K1RECAUTO
1	C33	CAP, SMD, 0603, 0.01µF, 50V, 10%, X7R	AVX	06035C103KAT2A
2	C16, C46	CAP, SMD, 0603, 0.1µF, 100V, 10%, X7R	VENKEL	C0603X7R101-104KNE
3	C56, C58, C61	CAP, SMD, 0603, 0.1µF, 50V, 10%, X7R	AVX	06035C104KAT2A
1	C40	CAP, SMD, 0603, 220pF, 50V, 10%, X7R	MURATA	GRM188R71H221KA01D
1	C39	CAP, SMD, 0603, 0.022µF, 25V, 10%, X7R	MURATA	GRM188R71E223KA01J
1	C36	CAP, SMD, 0603, 33000pF, 25V, 10%, X7R	PANASONIC	ECJ-1VB1E333K
2	C59, C72	CAP, SMD, 0603, 470pF, 100V, 10%, X7R	VISHAY	VJ0603Y471KXBA
2	C14, C45	CAP, SMD, 0603, .047µF, 25V, 10%, X7R	MURATA	GRM188R71E473KA01D
2	C30, C37	CAP, SMD, 0603, 0.47µF, 25V, 10%, X7R	MURATA	GRM188R71E474KA12D
1	C34	CAP, SMD, 0603, 820pF, 50V, 10%, X7R	KEMET	C0603C821K5RACTU
0	C17, C28, C35, C38, C44, C48, C49	CAP, SMD, 0603, DNP-PLACE HOLDER		
1	L1	COIL-PWR INDUCTOR, 15μH, 14A, 9mΩ, SMD, 18.3, x9.1, WW	WURTH ELEKTRONIK	74435571500 or 74439370150
8	C3, C4, C26, C27, C65, C66, C67, C68	CAP, RADIAL, 12.5x26.5, 220µF, 100V, 20%, ALUM.ELEC., 5mm	UNITED CHEMI-CON PANASONIC	EKZN101ELL221MK25S EEUFS2A221
6	TP16, TP18, TP20, TP22, TP29, TP30	CONN-COMPACT TEST PT, VERTICAL, WHT	KEYSTONE	5007
1	J10	CONN-HEADER, TH, 2X40, R/A, 2.54mmPITCH, 11x5mm	WURTH ELEKTRONIK	61308021021 (or two 40 pin)
2	J3, J6	CONN-HEADER, 1x2, BRKAWY 1X36, 2.54mm	BERG/FCI	68000-236HLF
3	J7, J8, J9	CONN-HEADER, 1x3, BREAKAWY 1X36, 2.54mm	BERG/FCI	68000-236HLF
1	D3	DIODE-SCHOTTKY, AEC-Q101, SMD, 2P, SOD-123, 30V, 200mA	NEXPERIA USA, INC	BAT54GWJ
2	D5, D0	DIODE-ZENER, SMD, SOD-323, 4.7V, 6%, 200mW	MICRO COMMERCIAL COMPONENTS	BZT52C4V7S-TP
2	D1, D2	DIODE-SCHOTTKY, AEC-Q101, SMD, SOD-123FA, 100V, 1A	ON SEMICONDUCTOR	S110FA
2	U2, U3	IC-DUAL OP AMP, RRIO, 8P, MSOP	RENESAS ELECTRONICS AMERICA	ISL28213FUZ
1	U1	IC-60V 4-SWITCH PWM CONTROLLER, 32P, QFN, 5x5	RENESAS ELECTRONICS AMERICA	ISL81601FRZ
8	Q1, Q2, Q3, Q4, Q5, Q6, Q7, Q8	TRANSIST-MOS, N-CHANNEL, SMD, 8P, PG-TDSON, 80V, 55A	INFINEON TECHNOLOGY	BSC123N08NS3GATMA1



Qty	Reference Designator	Description	Manufacturer	Manufacturer Part
4	R8, R10, R35, R37	RES, SMD, 0603, 1Ω, 1/10W, 1%, TF	PANASONIC	ERJ-3RQF1R0V
1	R4	RES, SMD, 0603, 10Ω, 1/10W, 1%, TF	KOA	RK73H1JT10R0F
3	R46, R84, R85	RES, SMD, 0603, 20Ω, 1/10W, 1%, TF	PANASONIC	ERJ-3EKF20R0V
11	R11, R15, R16, R19, R20, R22-R24, R27-R29	RES, SMD, 0603, 2.2Ω, 1/10W, 1%, TF	PANASONIC	ERJ-3RQF2R2V
1	R54	RES, SMD, 0603, 100Ω, 1/10W, 1%, TF	VENKEL	CR0603-10W-1000FT
2	R110, R166	RES, SMD, 0603, 1k, 1/10W, 1%, TF	PANASONIC	ERJ-3EKF1001V
4	R36, R67, R69, R70	RES, SMD, 0603, 10k, 1/10W, 1%, TF	VENKEL	CR0603-10W-1002FT
3	R33, R73, R75	RES, SMD, 0603, 100k, 1/10W, 1%, TF	VENKEL	CR0603-10W-1003FT
3	R68, R71, R72	RES, SMD, 0603, 1M, 1/10W, 1%, TF	PANASONIC	ERJ-3EKF1004V
2	R40, R42	RES, SMD, 0603, 15k, 1/10W, 1%, TF	PANASONIC	ERJ-3EKF1502V
1	R25	RES, SMD, 0603, 196k, 1/10W, 1%, TF	PANASONIC	ERJ-3EKF1963V
1	R76	RES, SMD, 0603, 20k, 1/10W, 1%, TF	VENKEL	CR0603-10W-2002FT
1	R26	RES, SMD, 0603, 2.7k, 1/10W, 1%, TF	VENKEL	CR0603-10W-2701FT
1	R112	RES, SMD, 0603, 3.48k, 1/10W, 1%, TF	PANASONIC	ERJ-3EKF3481V
1	R167	RES, SMD, 0603, 3.9k, 1/10W, 1%, TF	PANASONIC	ERJ-3EKF3901V
2	R12, R18	RES, SMD, 0603, 40.2k, 1/10W, 1%, TF	YAGEO	RC0603FR-0740K2L
1	R86	RES, SMD, 0603, 4.3M, 1/10W, 1%, TF	STACKPOLE	RMCF0603FT4M30
1	R7	RES, SMD, 0603, 43.2k, 1/10W, 1%, TF	YAGEO	RC0603FR-0743K2L
1	R39	RES, SMD, 0603, 48.7k, 1/10W, 1%, TF	PANASONIC	ERJ-3EKF4872V
2	R5, R38	RES, SMD, 0603, 5.1k, 1/10W, 1%, TF	VENKEL	CR0603-10W-5101FT
5	R41, R43, R60, R61, R165	RES, SMD, 0603, 51k, 1/10W, 1%, TF	YAGEO	RC0603FR-0751KL
1	R74	RES, SMD, 0603, 523k, 1/10W, 1%, TF	YAGEO	RC0603FR-07523KL
1	R3	RES, SMD, 0603, 62k, 1/10W, 1%, TF	YAGEO	RC0603FR-0762KL
1	R62	RES, SMD, 0603, 6.65k, 1/10W, 1%, TF	YAGEO	RC0603FR-076K65L
1	R44	RES, SMD, 0603, 8.45k, 1/10W, 1%, TF	PANASONIC	ERJ-3EKF8451V
0	a) R14, R30, R31, R32, R49, R50, R55, R87, R88 b) R103, R104, R105, R106, R107	RES, SMD, 0603, DNP-PLACE HOLDER		
1	R2	RES, SMD, 1206, 1M, 1/4W, 1%, TF	VENKEL	CR1206-4W-1004FT
1	R111	RES, SMD, 1206, 154k, 1/4W, 1%, TF	YAGEO	RC1206FR-07154KL
2	R45, R77	RES, SMD, 1206, 499k, 1/4W, 1%, TF	VENKEL	CR1206-4W-4993FT
0	R51, R52	RES, SMD, 1206, DNP, DNP, DNP, TF		
4	R1, R6, R57, R59	RES-AEC-Q200, SMD, 2512, 0.003Ω, 1W, 1%, CURR.SENSE, MF	VISHAY/DALE	WSL25123L000FEA
4	J1, J2, J4, J5	HDWARE, TERMINAL, M4 METRIC SCREW, TH, 4P, SNAP-FIT	KEYSTONE	7795
1	J11	CONN-SOCKET HEADER, TH, 2X40, R/A, 2.54mmPITCH, 12.6x5mm	WURTH ELEKTRONIK	61308024312 (or 2 x 613040243121)
0	D6, D7, D8, TP3 a) TP4-TP6, TP8-TP10, TP11-TP15, TP17, TP19, b) TP21, TP23-TP28	DO NOT POPULATE OR PURCHASE		

## 3.4 Board Layout

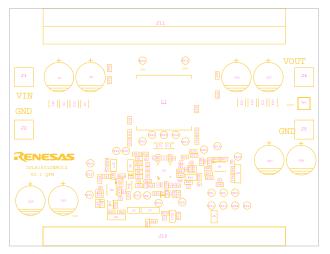


Figure 11. Assembly Top



0

C

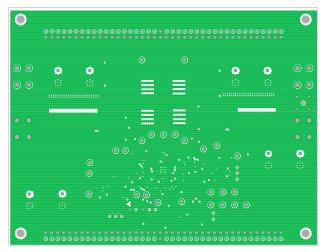


Figure 13. Layers 2 and 3 (Solid Ground), Identical


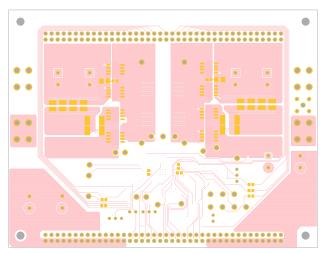


Figure 14. Bottom Layer

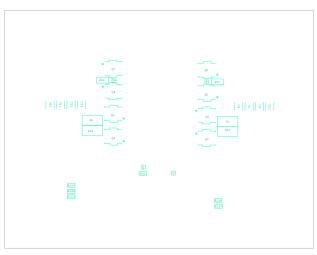

••

Figure 15. Assembly Bottom



# 4. Typical Performance Curves

 $V_{IN}$  = 48V,  $R_{62}$  = 6.65k, unless otherwise noted.


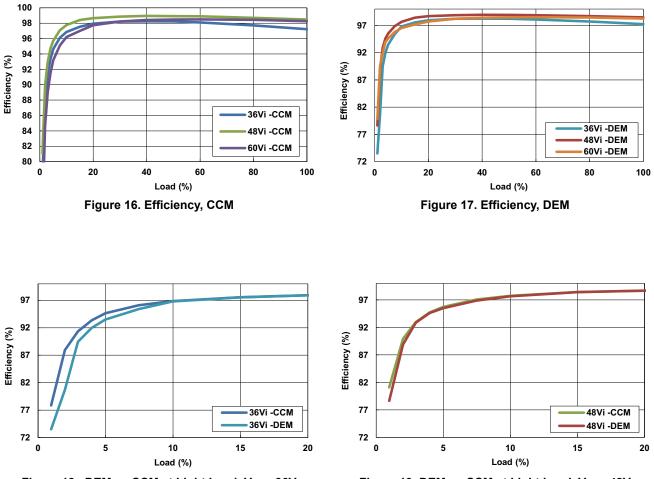


Figure 18. DEM vs CCM at Light Load, V<sub>IN</sub> = 36V

 



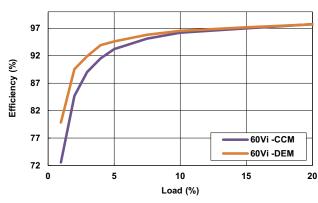


Figure 20. DEM vs CCM at Light Load,  $V_{IN}$  = 60V

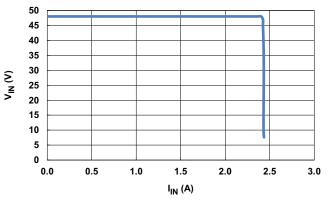


### ISL81601DEMO1Z

 





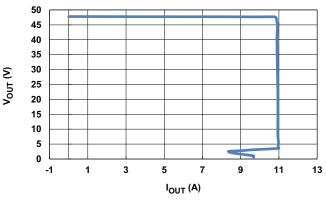



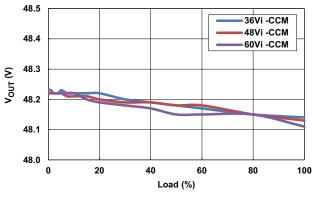


Figure 23. Load Regulation, CCM

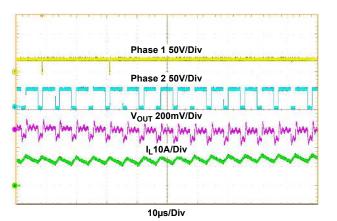


Figure 25. Phase 1, Phase 2,  $V_{OUT}$  and Inductor Current,  $V_{\rm IN}$  = 36V,  $I_{OUT}$  = 5A

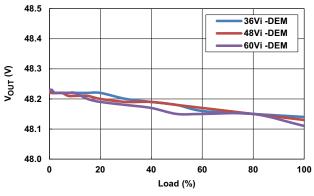


Figure 24. Load Regulation, DEM


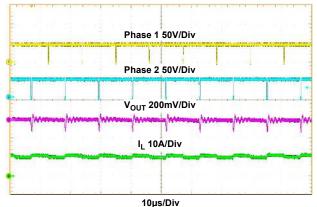


Figure 26. Phase 1, Phase 2,  $V_{OUT}$  and Inductor Current,  $V_{\rm IN}$  = 48V,  $I_{OUT}$  = 5A

 

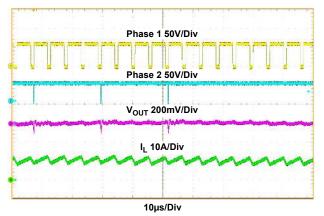


Figure 27. Phase 1, Phase 2, V<sub>OUT</sub> and Inductor Current,  $V_{IN}$  = 60V, I<sub>OUT</sub> = 5A

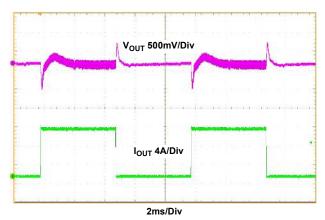


Figure 28. Load Transient,  $V_{IN}$  = 36V,  $I_{OUT}$  = 0A to 5A 2.5A/µs, CCM


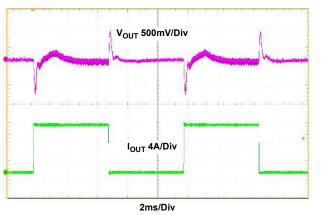


Figure 29. Load Transient, V<sub>IN</sub> = 48V, I<sub>OUT</sub> = 0A to 5A 2.5A/µs, CCM

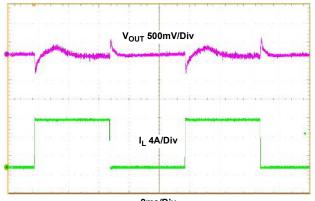

2ms/Div

Figure 30. Load Transient, V<sub>IN</sub> = 60V, I<sub>OUT</sub> = 0A to 5A 2.5A/µs, CCM

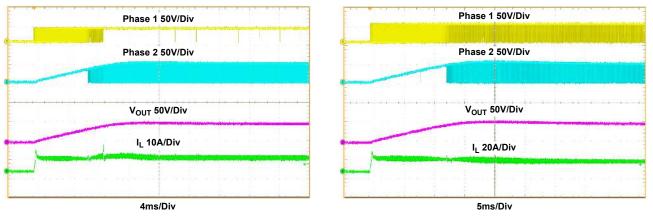


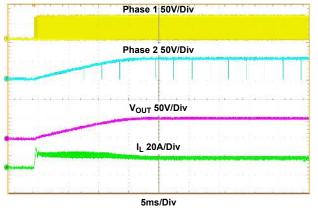


Figure 32. Start-Up Waveform,  $V_{IN}$  = 48V,  $I_{OUT}$  = 5A, CCM




### ISL81601DEMO1Z

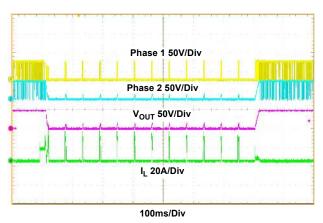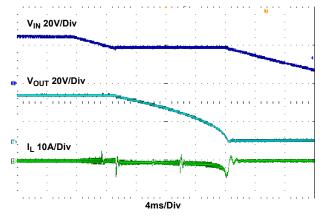
#### $V_{IN}$ = 48V, $R_{62}$ = 6.65k, unless otherwise noted. (Continued)

 


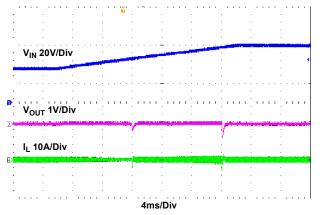


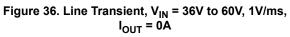












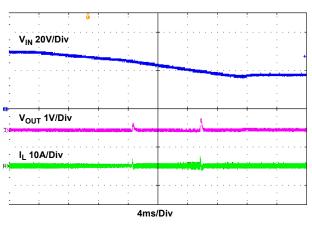


Figure 37. Line Transient,  $V_{IN}$  = 60V to 36V, 1V/ms,  $I_{OUT}$  = 0A

# 5. Revision History

Rev.	Date	Description
0.00	Oct 12, 2018	Initial release



#### Notice

- Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for
  the incorporation or any other use of the circuits, software, and information in the design of your product or system. Renesas Electronics disclaims any and all liability for any losses and damages incurred by
  you or third parties arising from the use of these circuits, software, or information.
- Renesas Electronics hereby expressly disclaims any warranties against and liability for infringement or any other claims involving patents, copyrights, or other intellectual property rights of third parties, by or arising from the use of Renesas Electronics products or technical information described in this document, including but not limited to, the product data, drawings, charts, programs, algorithms, and application examples.
- 3. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
- 4. You shall not alter, modify, copy, or reverse engineer any Renesas Electronics product, whether in whole or in part. Renesas Electronics disclaims any and all liability for any losses or damages incurred by you or third parties arising from such alteration, modification, copying or reverse engineering.
- 5. Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The intended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.
  - "Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; industrial robots; etc.

"High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control (traffic lights); large-scale communication equipment; key financial terminal systems; safety control equipment; etc. Unless expressly designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not intended or authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems; surgical implantations; etc.), or may cause serious property damage (space system; undersea repeaters; nuclear power control systems; aircraft control systems; key plant systems; military equipment; etc.). Renesas Electronics data sheet, user's manual or other Renesas Electronics document.

- 6. When using Renesas Electronics products, refer to the latest product information (data sheets, user's manuals, application notes, "General Notes for Handling and Using Semiconductor Devices" in the reliability handbook, etc.), and ensure that usage conditions are within the ranges specified by Renesas Electronics with respect to maximum ratings, operating power supply voltage range, heat dissipation characteristics, installation, etc. Renesas Electronics disclaims any and all liability for any malfunctions, failure or accident arising out of the use of Renesas Electronics products outside of such specified ranges.
- 7. Although Renesas Electronics endeavors to improve the quality and reliability of Renesas Electronics products, semiconductor products have specific characteristics, such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Unless designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not subject to radiation resistance design. You are responsible for implementing safety measures to guard against the possibility of bodily injury, injury or damage caused by fire, and/or danger to the public in the event of a failure or malfunction or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult and impractical, you are responsible for evaluating the safety of the final products or systems manufactured by you.
- 8. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. You are responsible for carefully and sufficiently investigating applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive, and using Renesas Electronics products in compliance with all these applicable laws and regulations. Renesas Electronics disclaims any and all liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
- Renesas Electronics products and technologies shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws
  or regulations. You shall comply with any applicable export control laws and regulations promulgated and administered by the governments of any countries asserting jurisdiction over the parties or
  transactions.
- 10. It is the responsibility of the buyer or distributor of Renesas Electronics products, or any other party who distributes, disposes of, or otherwise sells or transfers the product to a third party, to notify such third party in advance of the contents and conditions set forth in this document.
- 11. This document shall not be reprinted, reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics.
- 12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products
- (Note 1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its directly or indirectly controlled subsidiaries.

(Note 2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.

Refer to "http://www.renesas.com/" for the latest and detailed information.

(Rev.4.0-1 November 2017)



#### SALES OFFICES

### **Renesas Electronics Corporation**

http://www.renesas.com

Renesas Electronics Corporation TOYOSU FORESIA, 3-2-24 Toyosu, Koto-ku, Tokyo 135-0061, Japan Renesas Electronics America Inc. 1001 Murphy Ranch Road, Milpitas, CA 95035, U.S.A. Tel: +1-408-432-8888, Fax: +1-408-434-5351 Renesas Electronics Canada Limited 9251 Yonge Street, Suite 8309 Richmond Hill, Ontario Canada L4C 9T3 9251 Yonge Street, SL Tel: +1-905-237-2004 Renesas Electronics Europe Limited Dukes Meadow, Millboard Road, Bourne End, Buckinghamshire, SL8 5FH, U.K Tel: +44-1628-651-700 Renesas Electronics Europe GmbH Arcadiastrasse 10, 40472 Düsseldorf, German Tel: +49-211-6503-0, Fax: +49-211-6503-1327 Renesas Electronics (China) Co., Ltd. Room 1709 Quantum Plaza, No.27 ZhichunLu, Haidian District, Beijing, 100191 P. R. China Tel: +86-10-8235-1155, Fax: +86-10-8235-7679 Renesas Electronics (Shanghai) Co., Ltd. Unit 301, Tower A, Central Towers, 555 Langao Road, Putuo District, Shanghai, 200333 P. R. China Tel: +86-21-2226-0888, Fax: +86-21-2226-0999 Renesas Electronics Hong Kong Limited Unit 1601-1611, 16/F, Tower 2, Grand Century Place, 193 Prince Edward Road West, Mongkok, Kowloon, Hong Kong Tel: +852-2265-6688, Fax: +852 2886-9022 Renesas Electronics Taiwan Co., Ltd. 13F, No. 363, Fu Shing North Road, Taipei 10543, Taiwan Tel: +886-2-8175-9600, Fax: +886 2-8175-9670 Renesas Electronics Singapore Pte. Ltd. 80 Bendemeer Road, Unit #06-02 Hyflux Innovation Centre, Singapore 339949 Tel: +65-6213-0200, Fax: +65-6213-0300 Renesas Electronics Malaysia Sdn.Bhd. Unit 1207, Block B, Menara Amcorp, Amcorp Trade Centre, No. 18, Jln Persiaran Barat, 46050 Petaling Jaya, Selangor Darul Ehsan, Malaysia Tei: +60-3-7955-9309, Fax: +60-3-7955-9510 Renesas Electronics India Pvt. Ltd. No.777C, 100 Feet Road, HAL 2nd Stage, Indiranagar, Bangalore 560 038, India Tel: +91-80-67208700, Fax: +91-80-67208777 Renesas Electronics Korea Co., Ltd. 17F, KAMCO Yangjae Tower, 262, Gangnam-daero, Gangnam-gu, Seoul, 06265 Korea Tel: +82-2-558-3737, Fax: +82-2-558-5338

# ISL81601DEMO1Z

